

(Summary) Combinational Logic Design

Honam University

Documentation Standard

- Documentation of a digital system should provide the necessary information for building, testing, operating, and maintaining the system.
- Documentation include:
 1. Block Diagram : showing the inputs, outputs, the main building blocks (modules) of the system and how they are connected.
 2. Schematic Diagram : showing all the components, their types, and all interconnections.
 3. Timing Diagram : showing the logic signals as a function of time.
 4. Structured Logic Description : the operation of the Structure.
 - Example
 - Function Table of multiplexer, Program Listing of PLD (Programmable Logic Device).
 5. Circuit Description : explaining of the operation of the logic circuit.

2 Embedded System Lab..

Honam University

Outline


- Documentation Standard for Digital System.
- Digital Circuit Timing and Propagation Delay
- Combinational Logic Design Structure :
 - Decoder
 - Encoder
 - Three-State Buffer
 - Multiplexer
 - Demultiplexer
 - Exclusive-OR Gates
 - Parity Circuit
 - Comparator
 - Adder/ Subtractor
 - Arithmetic Logic Unit (ALU)

1 Embedded System Lab..

Honam University

Drawing Layout

- Inputs to the left, outputs to the right.
- Signals flow from left to right.
- Signal paths should be connected.
- Broken signal paths should be flagged to indicate the source or destination and direction.
- Crossing Lines/Connected Lines (T-type connection)
- Buses should be named : DATA[0-7], CONTROL
- A signal extracted from a bus should be named
- Bus Flags : - Unidirection
- Bidirection
- Multiple Pages Schematic:
 - Flat Structure.
 - Hierarchical Structure.

 


3 Embedded System Lab..

Honam University

Decoder

 
- Multiple-input/Multiple-output device.
- Converts input code into output code.
- Input Codes :
 - Binary Code
 - Gray Code
 - BCD Code
 - Your Code ..



Logic Diagram of 2-to-4 Decoder

1 of 4 Decoder

 
- $Y0 = I0'I1'EN$
- $Y1 = I0 I1'EN$
- $Y2 = I0'I1 EN$
- $Y3 = I0 I1 EN$



Binary Decoder

- n-to- 2^n Decoder : n inputs and 2^n outputs.
- Input code : Binary Code.
- Output code : 1-out-of- 2^n , One output is asserted for each input code.
- Example : n=2, 2-to-4 Decoder

Inputs			Outputs			
EN	I1	I0	Y3	Y2	Y1	Y0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

 

- Logic Diagram


74x139 : 1 of 4 Decoder

- Active Low Enable, Active Low Outputs

- Truth Table

Inputs			Outputs			
$\overline{/G}$	B	A	Y3	Y2	Y1	Y0
1	x	x	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

Logic Symbol

 


74x138 1 of 8 Decoder

Inputs						Outputs							
G1	/G2A	/G2B	C	B	A	/Y7	/Y6	/Y5	/Y4	/Y3	/Y2	/Y1	/Y0
0	x	x	x	x	x	1	1	1	1	1	1	1	1
x	1	x	x	x	x	1	1	1	1	1	1	1	1
x	x	1	x	x	x	1	1	1	1	1	1	1	1
1	0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	0	1	1	1	1	1	1	0	1	1
1	0	0	0	1	0	1	1	1	1	0	1	1	1
1	0	0	0	1	1	1	1	1	0	1	1	1	1
1	0	0	1	0	0	1	1	1	0	1	1	1	1
1	0	0	1	0	1	1	1	0	1	1	1	1	1
1	0	0	1	1	0	1	0	1	1	1	1	1	1
1	0	0	1	1	1	1	0	1	1	1	1	1	1
1	0	0	1	1	1	0	1	1	1	1	1	1	1

7-Segment Decoder/Driver



- Input Code : BCD Code
Output Code : 7-Segment Code
- Truth Table for Active High 7-Segment Decoder/Driver

Input				Output						
D	C	B	A	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	0	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0	1	1	1	1	1	1	1
1	0	1	1	1	1	1	0	0	1	1

 

7-Segment Display

  
- Displays decimal numbers and some characters
- LED (Light Emitting Diode) or LCD (Liquid Crystal Display)
- LED type
 - Common Anode(CA) /Common Cathode(CC) type



- CA : requires Active Low inputs (a driver with Active Low outputs)
- CC : requires Active High inputs (a driver with Active High outputs)


74x47 7-Segment Decoder/Driver

- Driving CC 7-Segment Display

 

Encoder

 - Multiple-input/multiple-output device.
- Performs the inverse function of a Decoder.
- Outputs (m) are less than inputs (n).
- Converts input code words into output code words.




Priority Encoder

- Assign priorities to the inputs
- When more than one input are asserted, the output generates the code of the input with the highest priority
- Priority Encoder :

$H7=I7$
 $H6=I6.I7'$
 $H5=I5.I6'.I7'$
 $H4=I4.I5'.I6'.I7'$
 $H3=I3.I4'.I5'.I6'.I7'$
 $H2=I2.I3'.I4'.I5'.I6'.I7'$
 $H1=I1. I2'.I3'.I4'.I5'.I6'.I7'$
 $H0=I0.I1'. I2'.I3'.I4'.I5'.I6'.I7'$
 $IDLE= I0'.I1'. I2'.I3'.I4'.I5'.I6'.I7'$

- Encoder

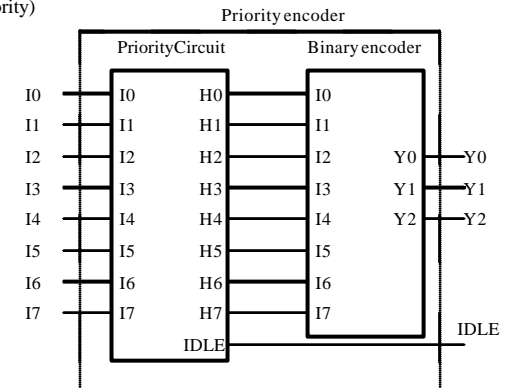
$Y0 = I1 + I3 + I5 + I7$
 $Y1 = I2 + I3 + I6 + I7$
 $Y2 = I4 + I5 + I6 + I7$




Binary Encoder

- 2^n -to- n Encoder : 2^n Inputs and n Outputs
- Input code : 1-out-of- 2^n
- Output code : Binary Code
- Example : $n=3$, 8-to-3 encoder


Inputs								Outputs		
I0	I1	I2	I3	I4	I5	I6	I7	Y0	Y1	Y2
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

BCD Encoder (Application)

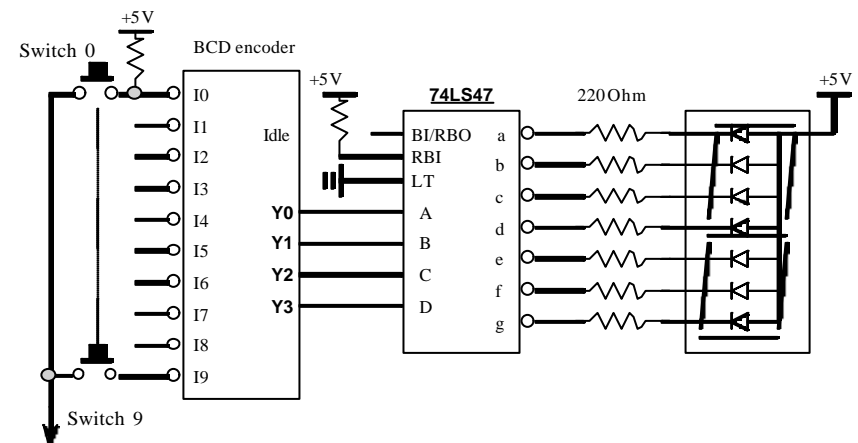


Logic Diagram of 4-to-1 Multiplexer

 

Exclusive OR & Exclusive NOR Gate

- XOR : $X \oplus Y = X'Y + X \cdot Y'$
- XNOR : $(X \oplus Y)' = X \cdot Y + X'Y'$
- Truth Table :

X	Y	XOR	XNOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

 


1-to-4 DMUX


1-to-4 DEMUX

Function Table

IN	S1	S0	D0	D1	D2	D3
x	0	0	IN	0	0	0
x	0	1	0	IN	0	0
x	1	0	0	0	IN	0
x	1	1	0	0	0	IN

 


Logic Diagram

 

Half Adder

- Truth table :

X	Y	S=(X+Y)	Co
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 


Full Adder

- Truth Table


X	Y	C _i	S	C _o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 - $S = X'Y'Ci + X'YCi' + XY'Ci' + XYCi$
 $S = X \oplus Y \oplus Ci$
- $Co = XY + XCi + Y Ci$




Full Adder vs. Carry Lookahead Adder

- Full Adder

 


- Carry Lookahead Adder

 


Adder/Subtractor Circuit

 - M=0 : Ripple Adder
- M=1 : Ripple Subtractor



Networks for Binary Addition

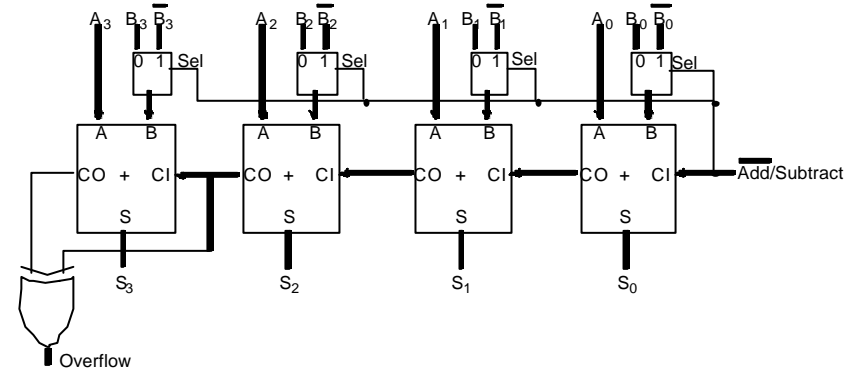Adder/Subtractor - assumes 2's complement representation



$$A - B = A + (-B) = A + \overline{B} + 1$$