

Truth Table for Code Converter Example

Decimal Digit	Input BCD				Output Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

Truth Table for BCD-to-Seven-Segment Decoder

BCD Input				Seven-Segment Decoder						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
All other inputs				0	0	0	0	0	0	0

Truth Table for 3-to-8-Line Decoder

Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Truth Table for Octal-to-Binary Encoder


Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Truth Table of Priority Encoder


Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

Signed Binary Numbers


Decimal	Signed 2's Complement	Signed 1's Complement	Signed Magnitude
+7	0111	0111	0111
+6	0110	0110	0110
+5	0101	0101	0101
+4	0100	0100	0100
+3	0011	0011	0011
+2	0010	0010	0010
+1	0001	0001	0001
+0	0000	0000	0000
-0	—	1111	1000
-1	1111	1110	1001
-2	1110	1101	1010
-3	1101	1100	1011
-4	1100	1011	1100
-5	1011	1010	1101
-6	1010	1001	1110
-7	1001	1000	1111
-8	1000	—	—

 


(a) Symbol for circuit

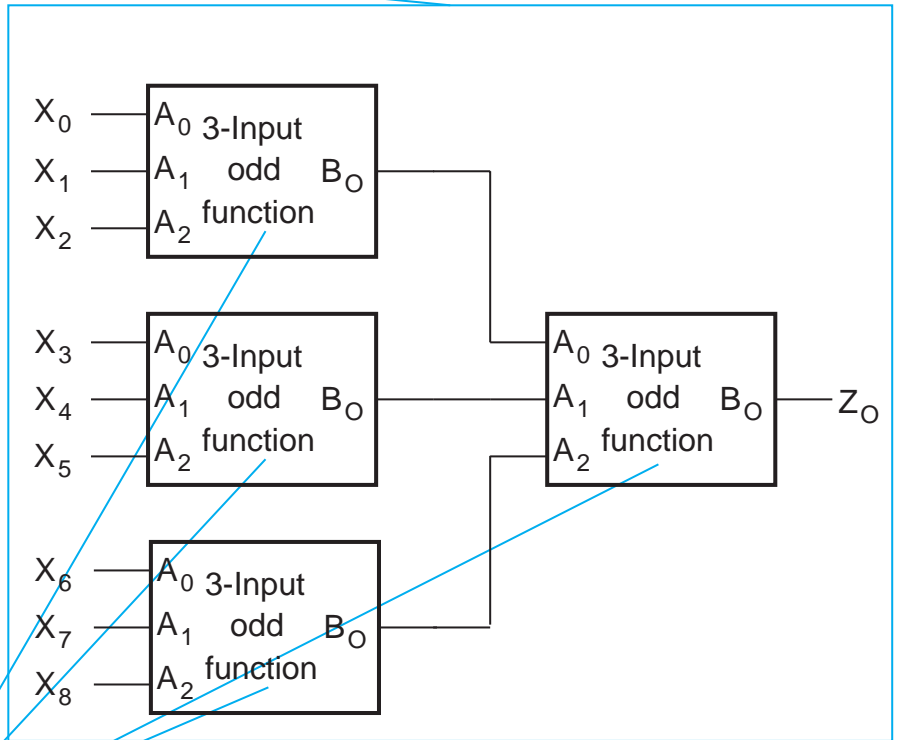

 (b) Circuit as interconnected 3-input odd function blocks




 (c) 3-input odd function circuit as interconnected exclusive-OR blocks



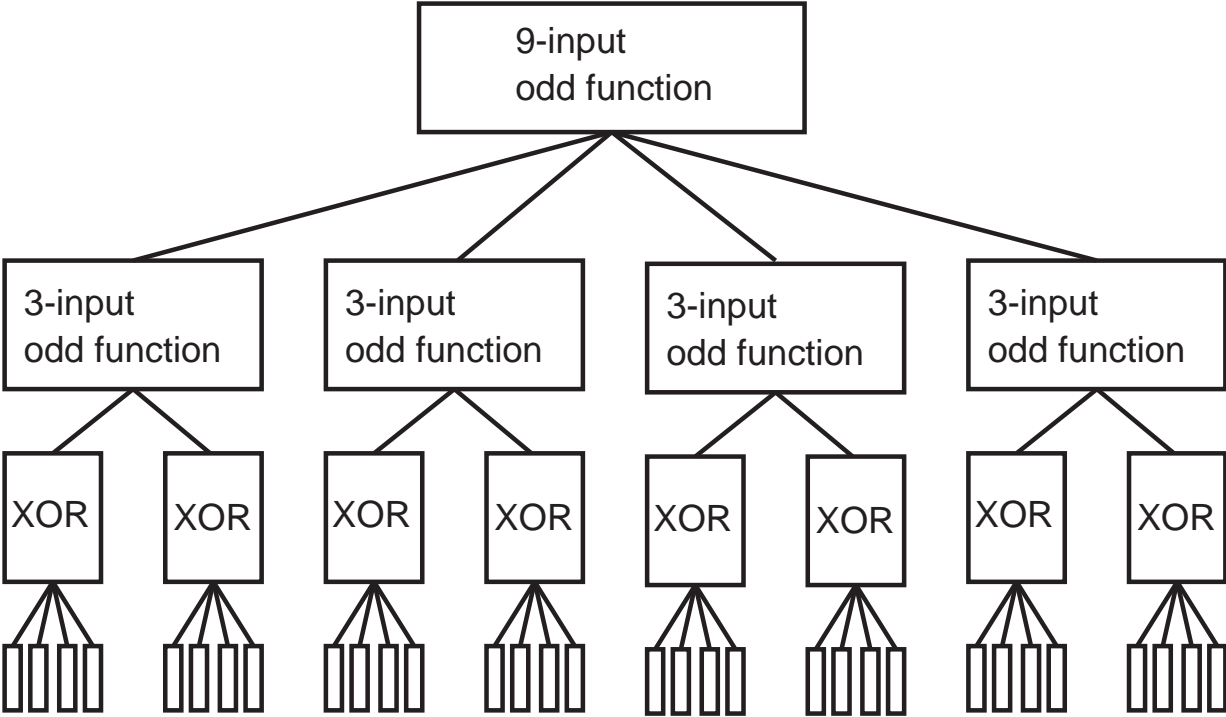
(d) Exclusive-OR block as interconnected NANDs

Diagrams Representing the Hierarchy for Figure 3-2




-NAND

(a)

 


(b)


Logic Diagram for Analysis Example

 


Logic Diagram for Binary Adder

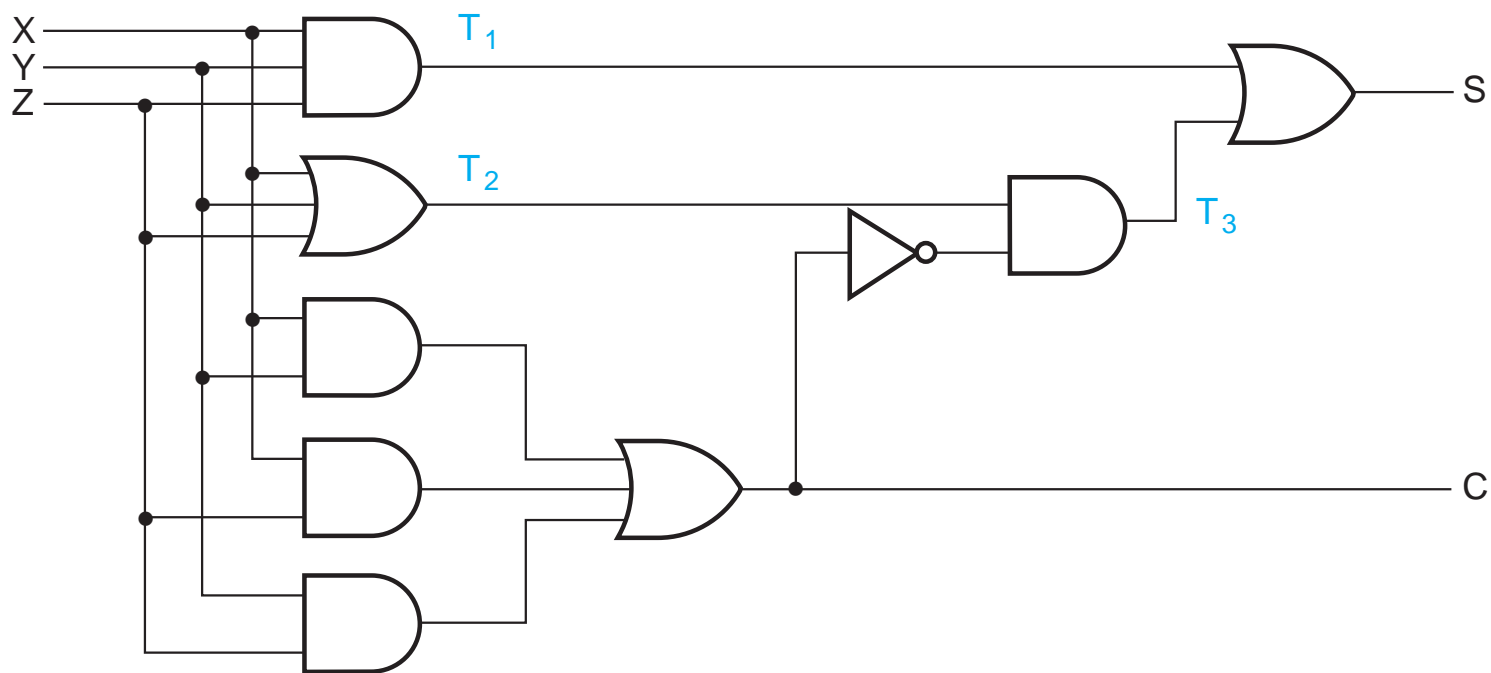

 
ViewDraw® Schematic for Binary Adder in Figure 3-5



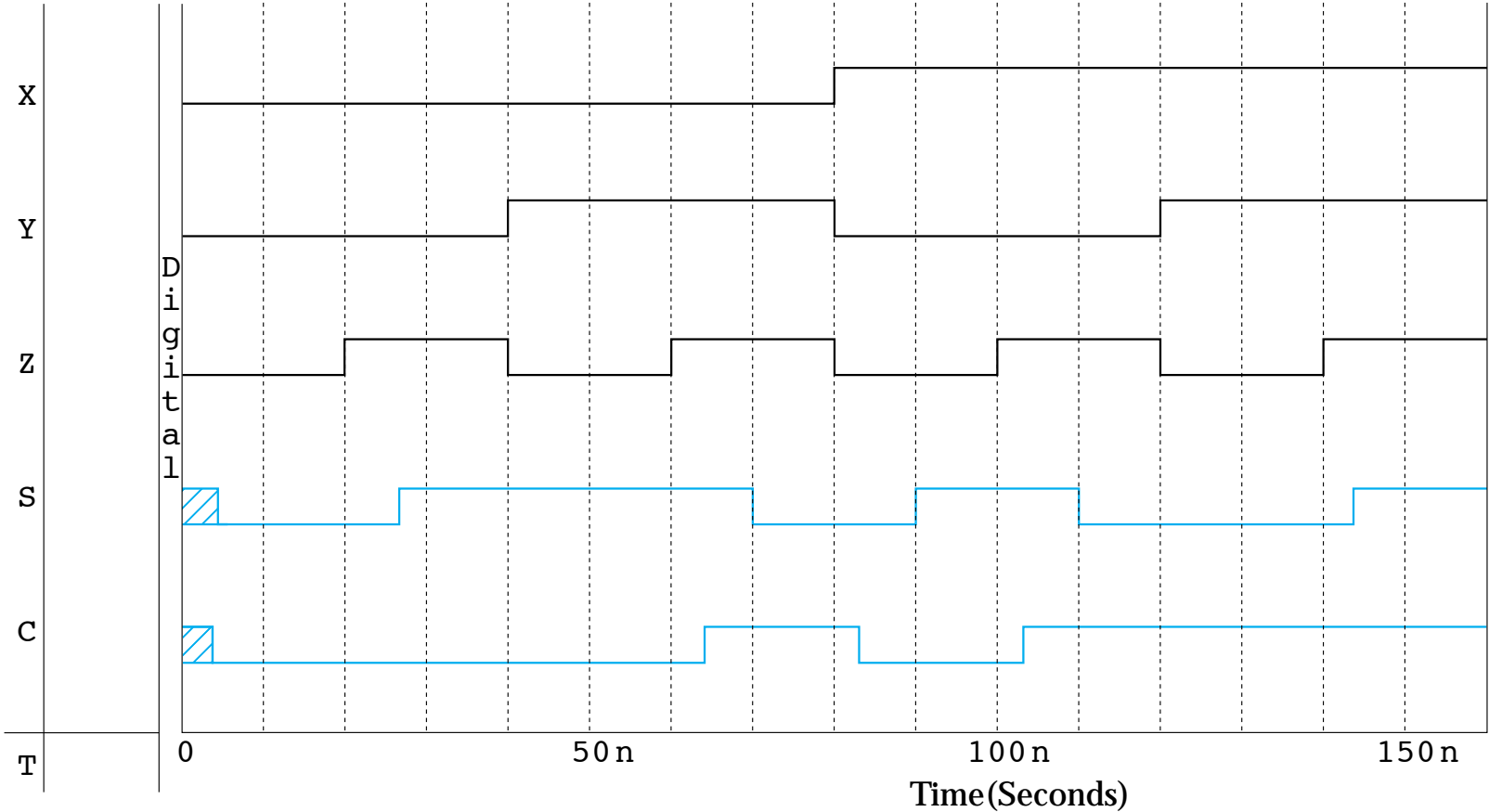
ViewTrace® Input and Output Waveforms for the Binary Adder Schematic in Figure 3-6




Maps for BCD-to-Excess-3 Code Converter

 


$$W = A + BC + BD$$

 

$$X = \bar{B}C + BD + B\bar{C}\bar{D}$$

 


$$Y = CD + \bar{C}\bar{D}$$

 


$$Z = \bar{D}$$

 Logic Diagram of BCD-to-Excess-3 Code Converter




Seven-Segment Display

 


(a) Segment designation



(b) Numeric designation for display

 

A 2-to-4-Line Decoder with Enable Input

 


(a) Logic diagram


E	A_1	A_0	D_0	D_1	D_2	D_3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

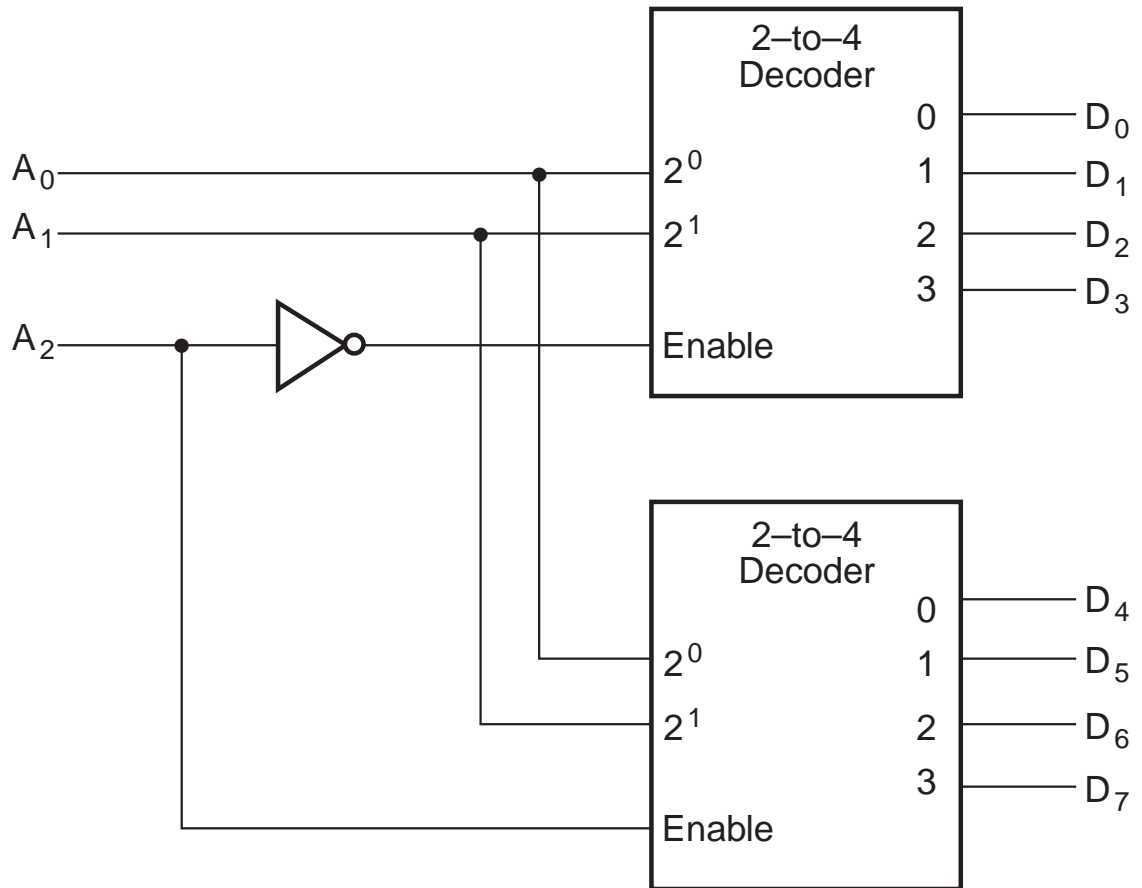(b) Truth table


T-45 A 3-to-8 Decoder Constructed with Two 2-to-4 Decoders



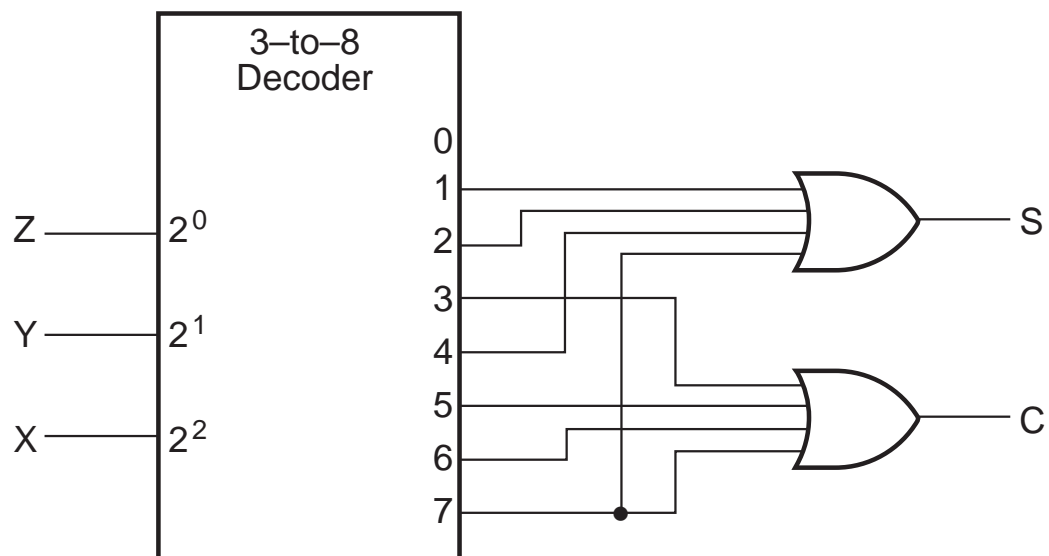
Implementing a Binary Adder Using a Decoder



 Logic Diagram of a 4-Input Priority Encoder




4-to-1-Line Multiplexer

 


Function table

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

4-to-1-Line Multiplexer with Transmission Gates

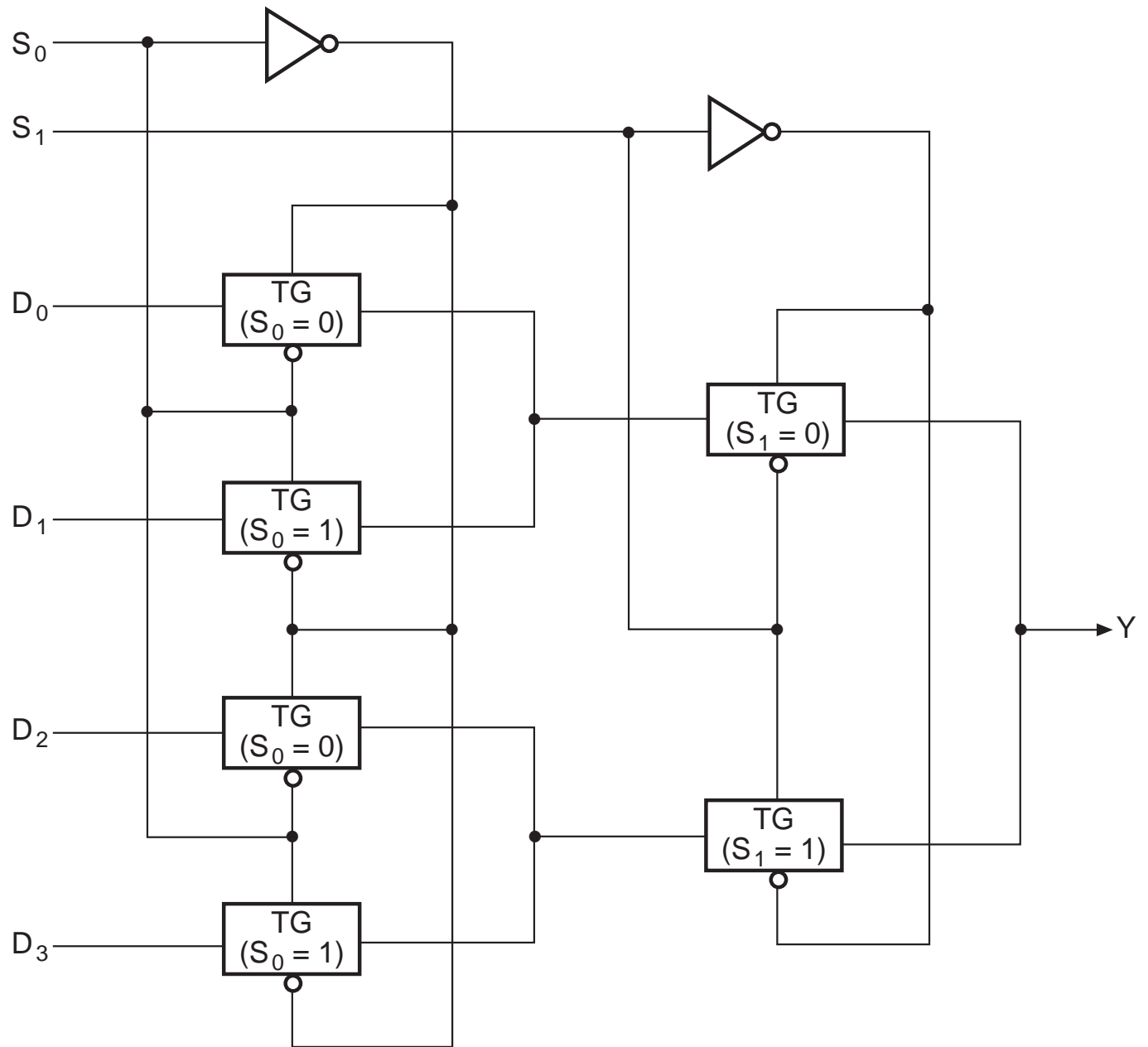

Quadruple 2-to-1-Line Multiplexer

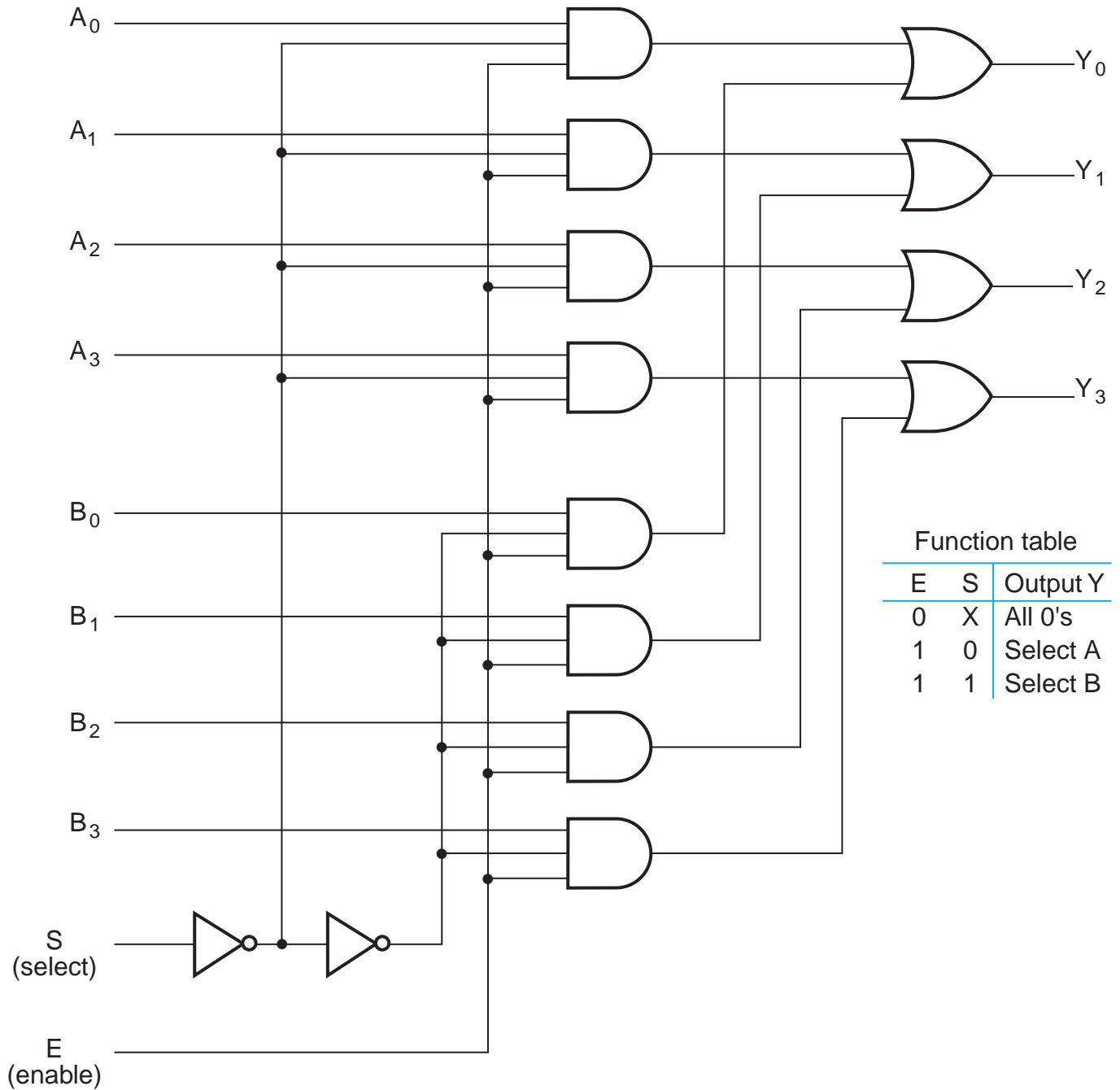


Function table

E	S	Output Y
0	X	All 0's
1	0	Select A
1	1	Select B

Implementing a Boolean Function with a Multiplexer

X	Y	Z	F	
0	0	0	0	$F = Z$
0	0	1	1	
0	1	0	1	$F = \bar{Z}$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	


(a) Truth table

 


(b) Multiplexer implementation

Implementing a Four-Input Function with a Multiplexer


A	B	C	D	F	
0	0	0	0	0	F = D
0	0	0	1	1	
0	0	1	0	0	F = D
0	0	1	1	1	
0	1	0	0	1	F = \bar{D}
0	1	0	1	0	
0	1	1	0	0	F = 0
0	1	1	1	0	
1	0	0	0	0	F = 0
1	0	0	1	0	
1	0	1	0	0	F = D
1	0	1	1	1	
1	1	0	0	1	F = 1
1	1	0	1	1	
1	1	1	0	1	F = 1
1	1	1	1	1	

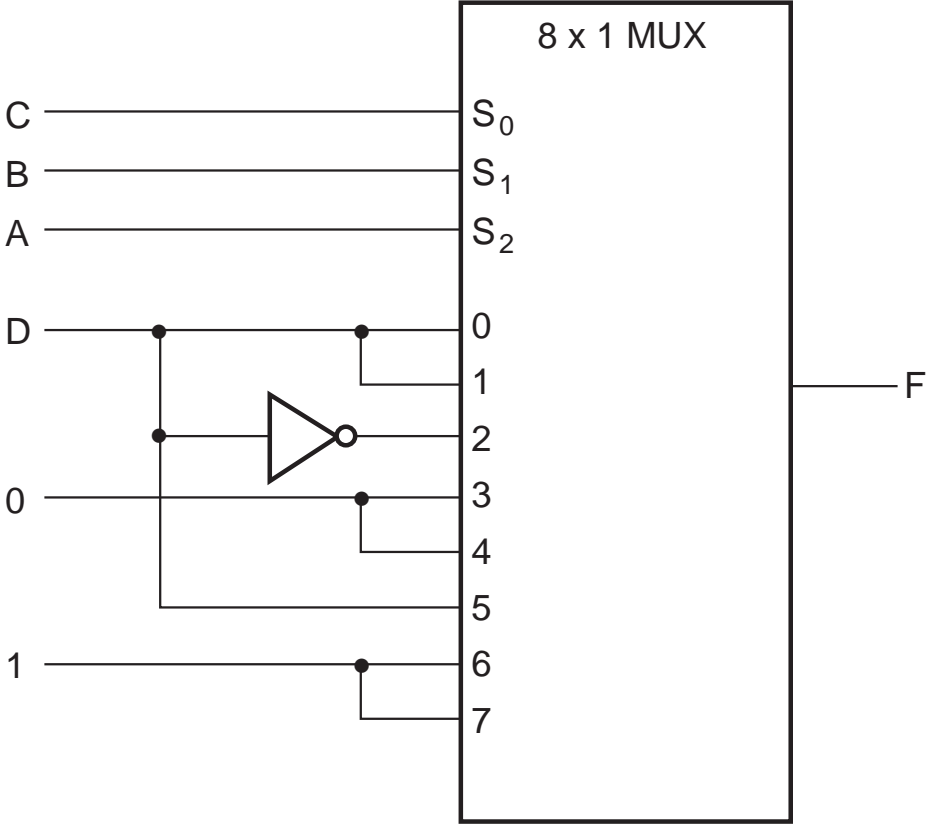


1-to-4-Line Demultiplexer

 


Logic Diagram of Full Adder

 


4-Bit Ripple Carry Adder

 

Development of a Carry Lookahead Adder

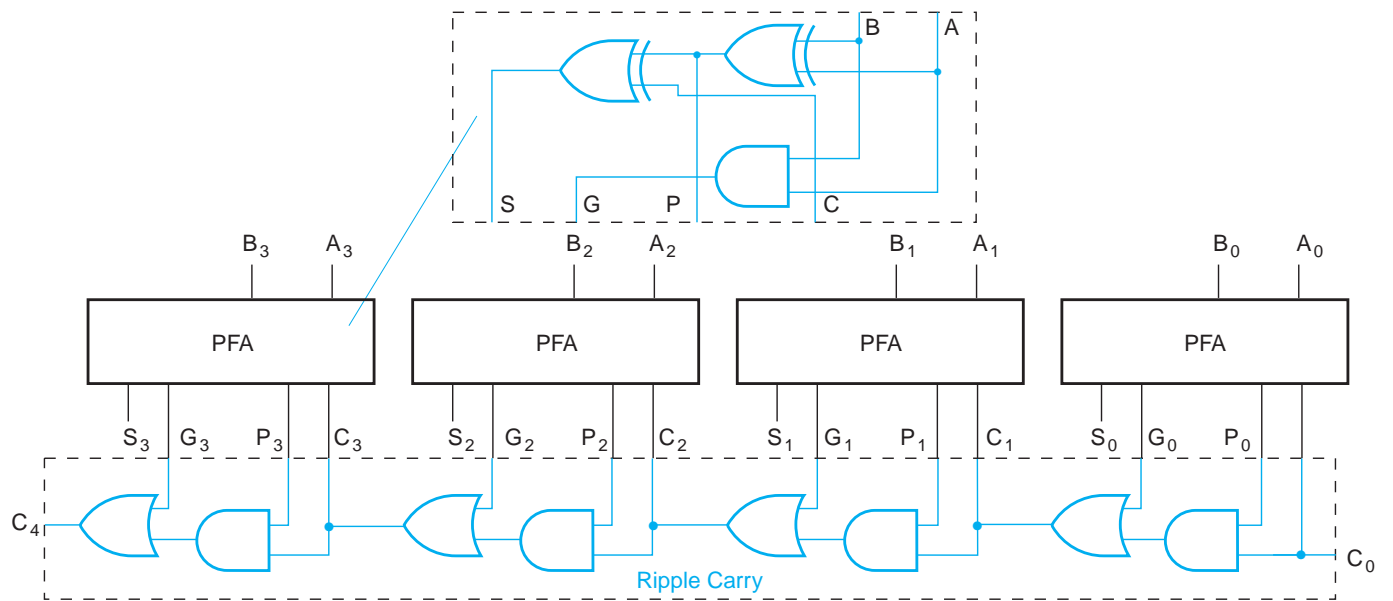


(a)

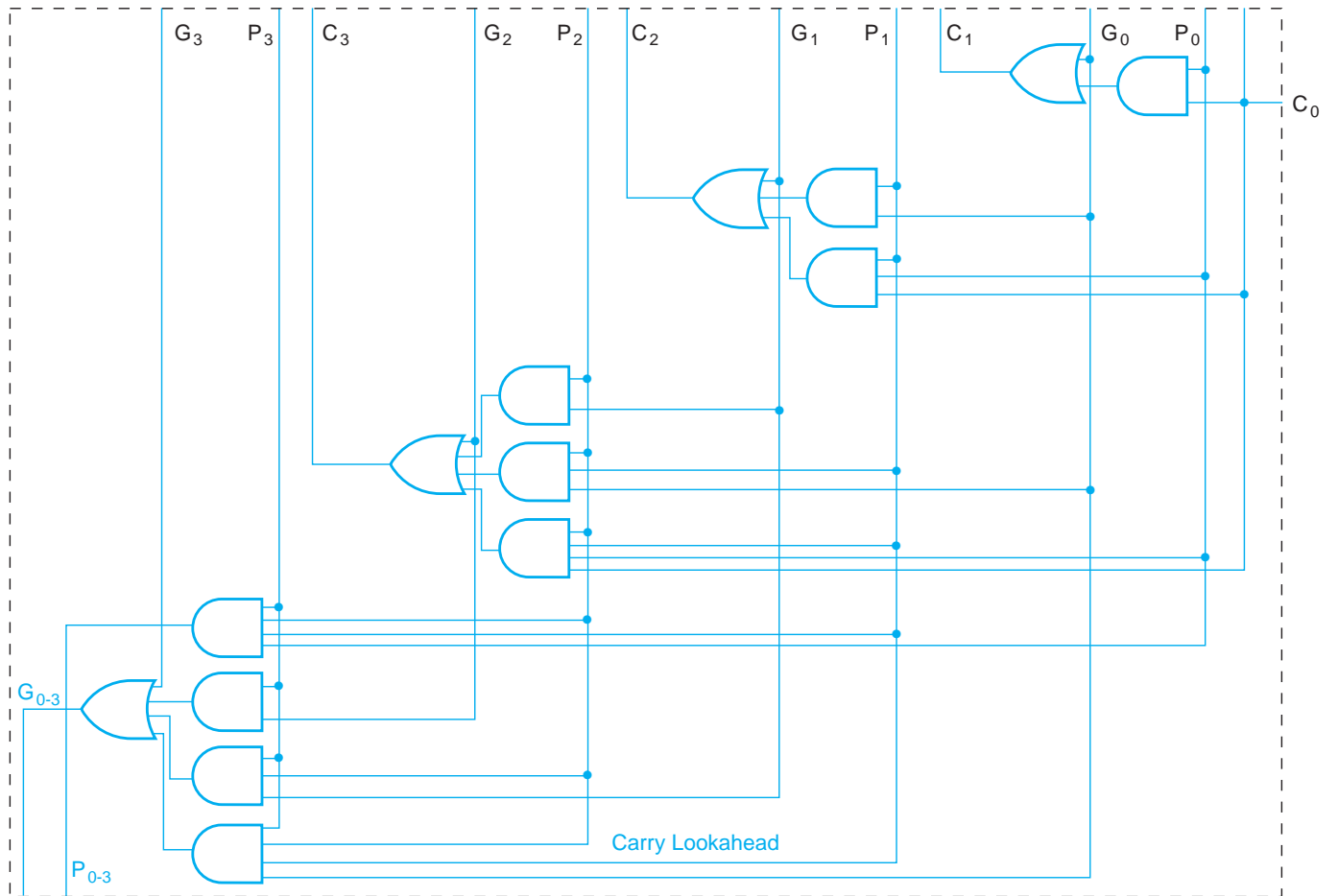


(b)

Block Diagram of Binary Adder-Subtractor

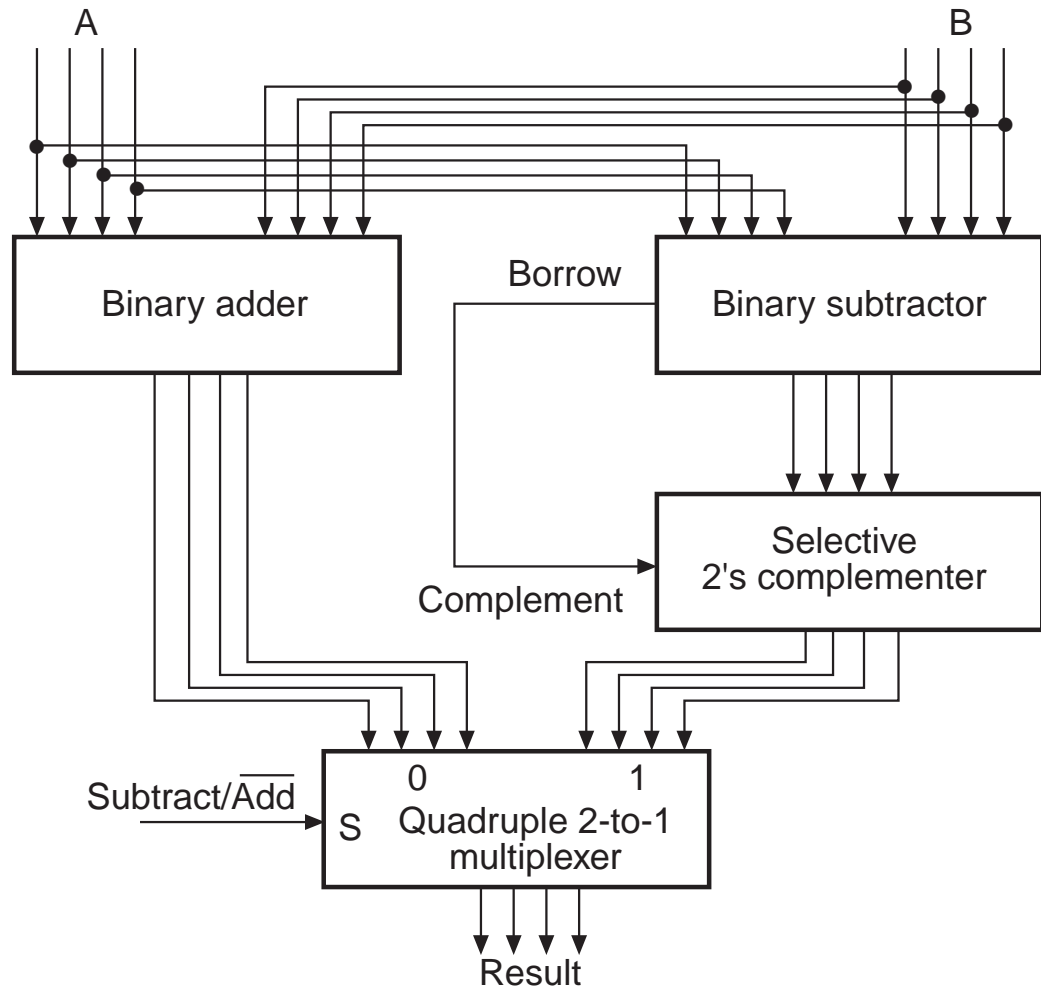


Adder-Subtractor Circuit

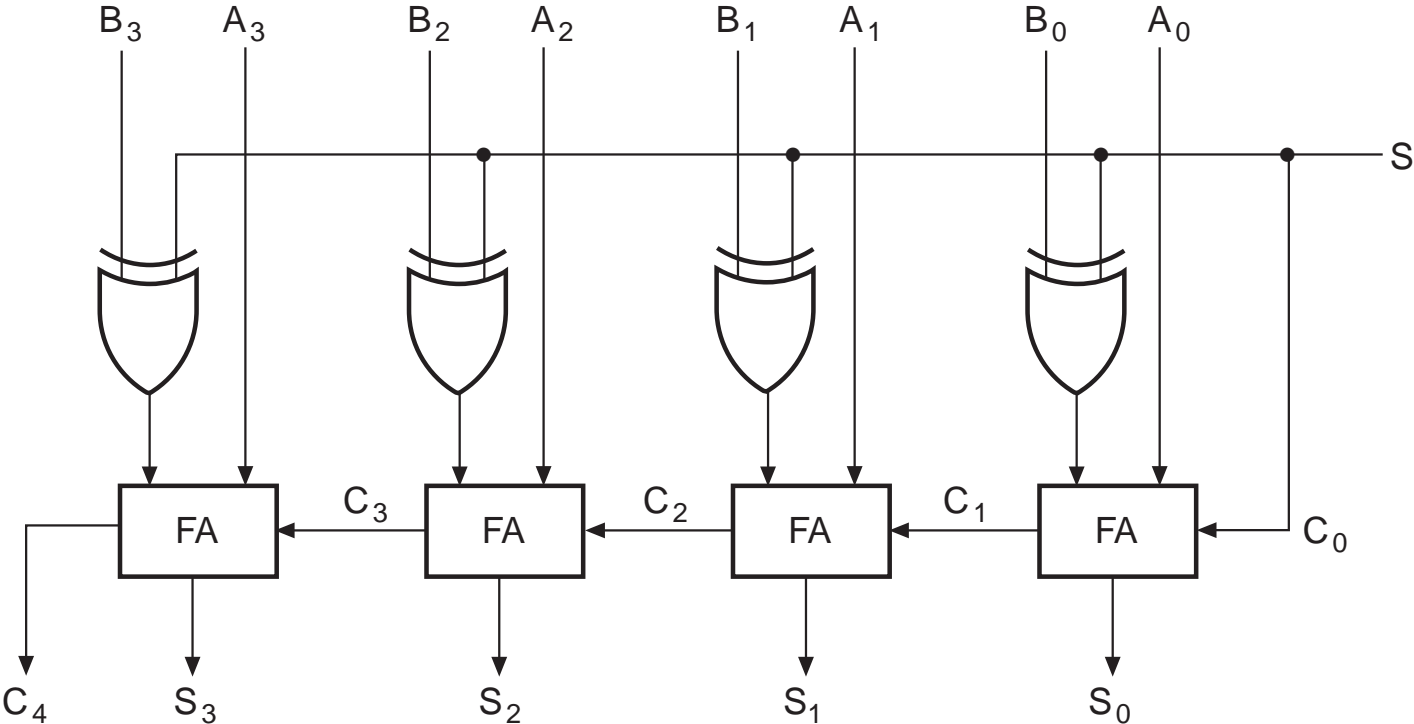


A 2-Bit by 2-Bit Binary Multiplier


		B ₁	B ₀
	A ₁	A ₀ B ₁	A ₀ B ₀
	A ₁ B ₁	A ₁ B ₀	
C ₃	C ₂	C ₁	C ₀

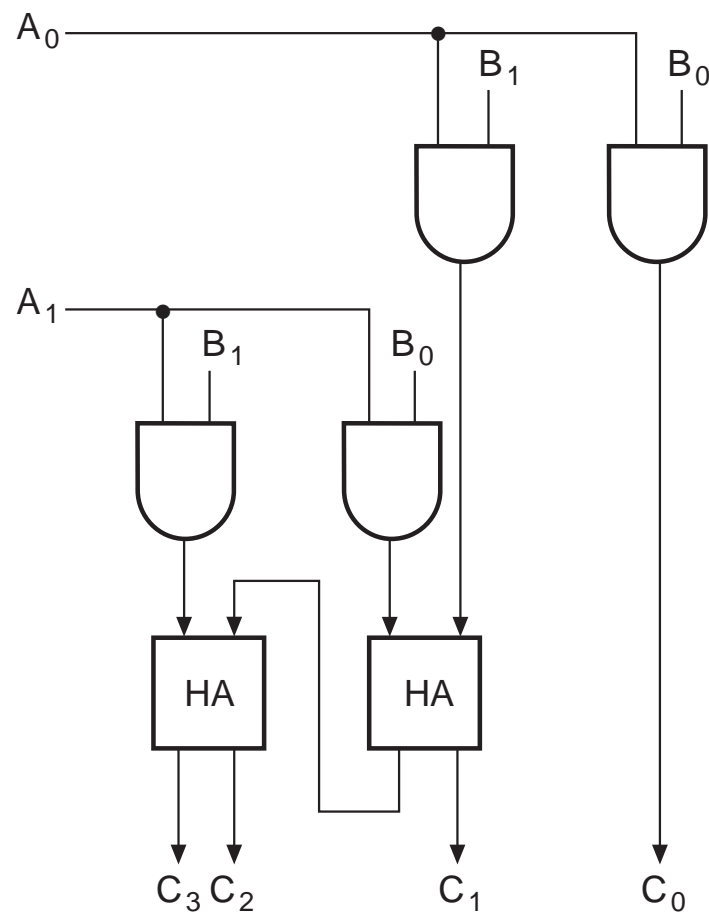



A 4-Bit by 3-Bit Binary Multiplier

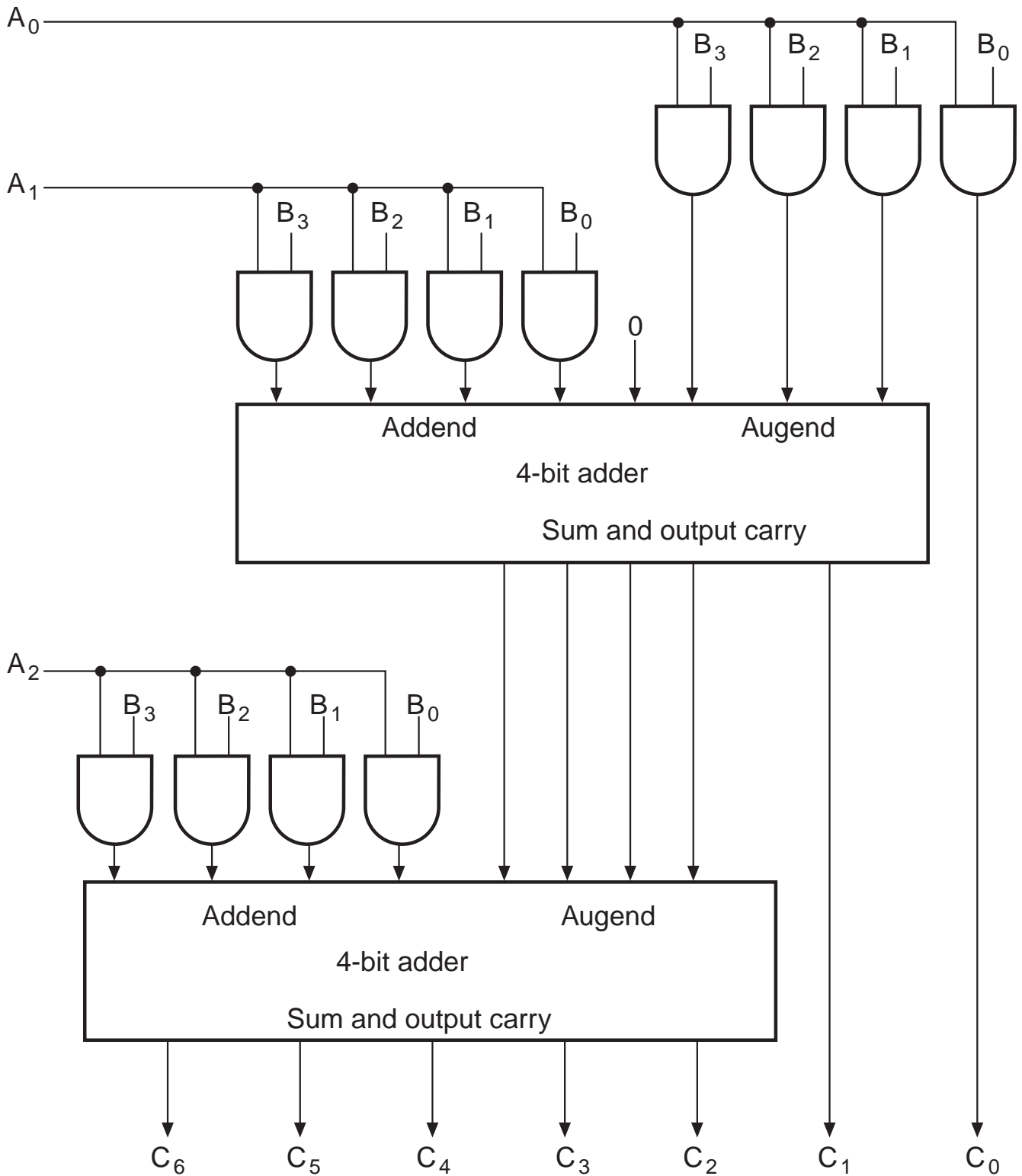


Block Diagram of BCD Adder

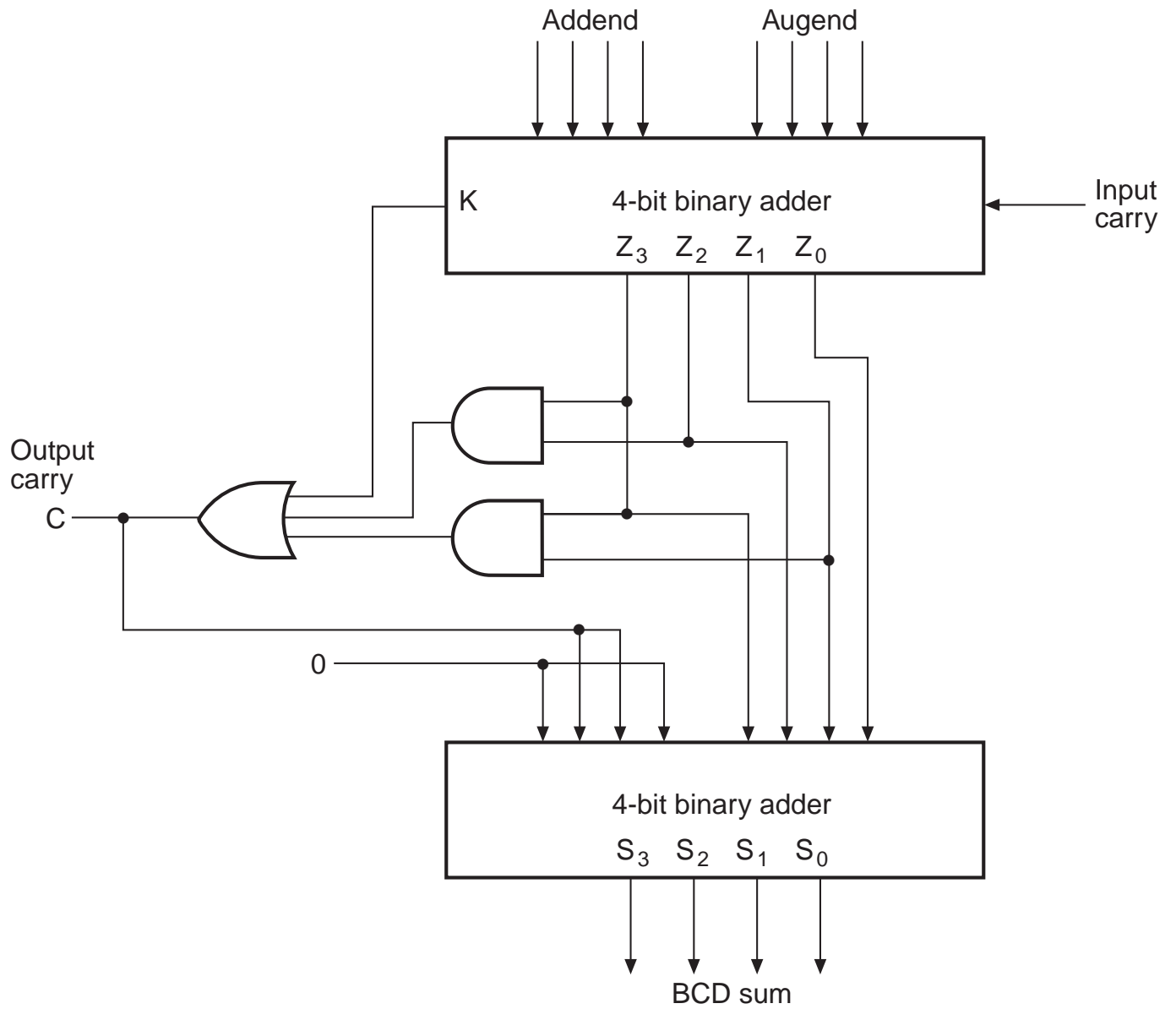

 

 

(a) 3-to-8 line

 


(b) 2-to-4 line


EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

(c) Truth table for decoder in (b) with EN and outputs negative logic

Example of a G-(AND) Dependency

 


(a) Block with G1 and G2

 


 (b) Equivalent interpretation

Standard Graphics Symbols for Multiplexers




(a) 8-to-1 line

 

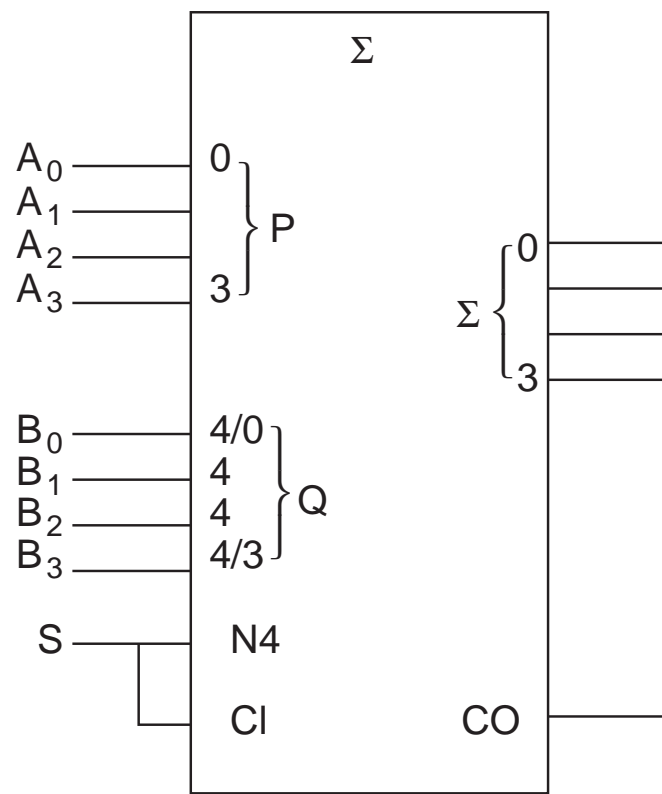
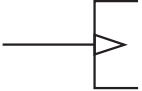
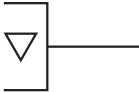
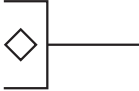
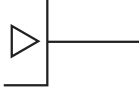


(b) Quadruple 2-to-1 line

Graphics Symbol for an Adder-Subtractor



Qualifying Symbols Associated with Inputs and Outputs

Symbol	Description
	Active-low input or output
	Logic negation input or output
	Enable input: enables all outputs when active
	Dynamic input
	Three-state output
	Open-circuit output
	Output with special amplification