
Timing pulse	Shift Register A				Shift Register B			
Initial value	1	0	1	1	0	0	1	0
After T_1	0	1	0	1	1	0	0	1
After T_2	0	0	1	0	1	1	0	0
After T_3	0	0	0	1	0	1	1	0
After T_4	0	0	0	0	1	0	1	1

Counting Sequence of Binary Counter

Upward Counting Sequence				Downward Counting Sequence			
Q ₃	Q ₂	Q ₁	Q ₀	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	1	1	1	1
0	0	0	1	1	1	1	0
0	0	1	0	1	1	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	0	1	1
0	1	0	1	1	0	1	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	0	0
1	0	0	0	0	1	1	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	0	1
1	0	1	1	0	1	0	0
1	1	0	0	0	0	1	1
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	1
1	1	1	1	0	0	0	0

State Table and Flip-Flop Inputs for Binary Counter





Present state				Next state				Flip-flop inputs							
Q_3	Q_2	Q_1	Q_0	Q_3	Q_2	Q_1	Q_0	J_{Q3}	K_{Q3}	J_{Q2}	K_{Q2}	J_{Q1}	K_{Q1}	J_{Q0}	K_{Q0}
0	0	0	0	0	0	0	1	0	×	0	×	0	×	1	×
0	0	0	1	0	0	1	0	0	×	0	×	1	×	×	1
0	0	1	0	0	0	1	1	0	×	0	×	×	0	1	×
0	0	1	1	0	1	0	0	0	×	1	×	×	1	×	1
0	1	0	0	0	1	0	1	0	×	×	0	0	×	1	×
0	1	0	1	0	1	1	0	0	×	×	0	1	×	×	1
0	1	1	0	0	1	1	1	0	×	×	0	×	0	1	×
0	1	1	1	1	0	0	0	1	×	×	1	×	1	×	1
1	0	0	0	1	0	0	1	×	0	0	×	0	×	1	×
1	0	0	1	1	0	1	0	×	0	0	×	1	×	×	1
1	0	1	0	1	0	1	1	×	0	0	×	×	0	1	×
1	0	1	1	1	1	0	0	×	0	1	×	×	1	×	1
1	1	0	0	1	1	0	1	×	0	×	0	0	×	1	×
1	1	0	1	1	1	1	0	×	0	×	0	1	×	×	1
1	1	1	0	1	1	1	1	×	0	×	0	×	0	1	×
1	1	1	1	0	0	0	0	×	1	×	1	×	1	×	1

State Table and Flip-Flop Inputs for BCD Counter


Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	Y	T_{Q8}	T_{Q4}	T_{Q2}	T_{Q1}
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

State Table and Flip-Flop Inputs for Binary Counter


Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	0	1	0	×	0	×	1	×
0	0	1	0	1	0	0	×	1	×	×	1
0	1	0	1	0	0	1	×	×	1	0	×
1	0	0	1	0	1	×	0	0	×	1	×
1	0	1	1	1	0	×	0	1	×	×	1
1	1	0	0	0	0	×	1	×	1	0	×

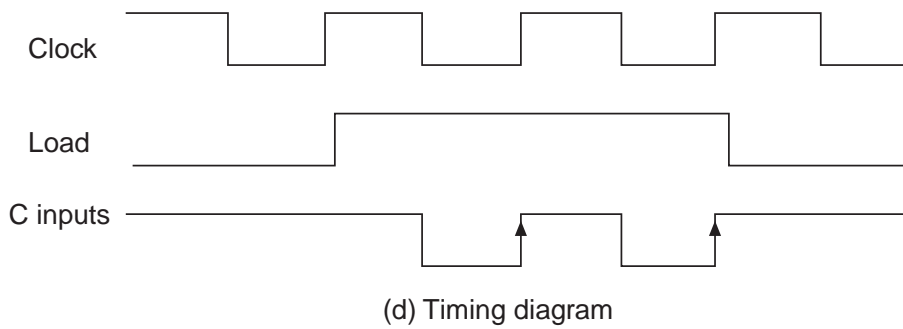  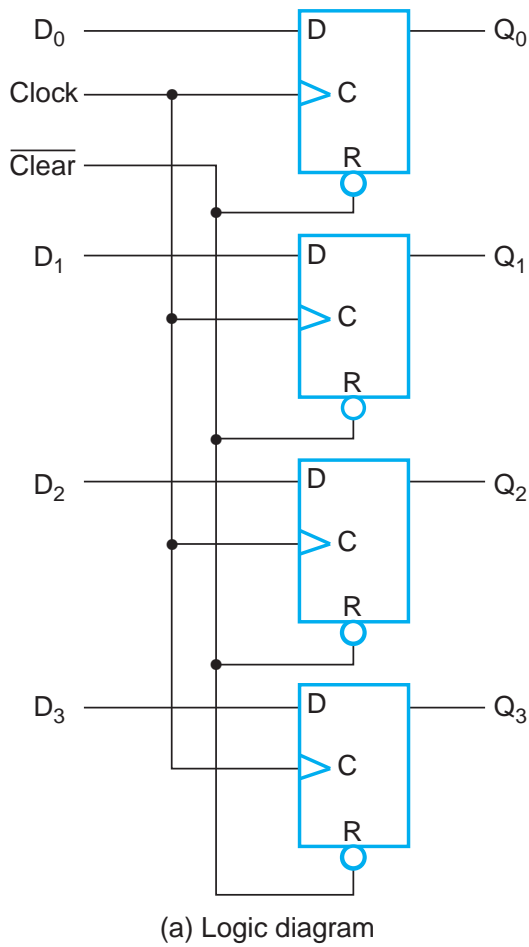


4-Bit Register with Parallel Load

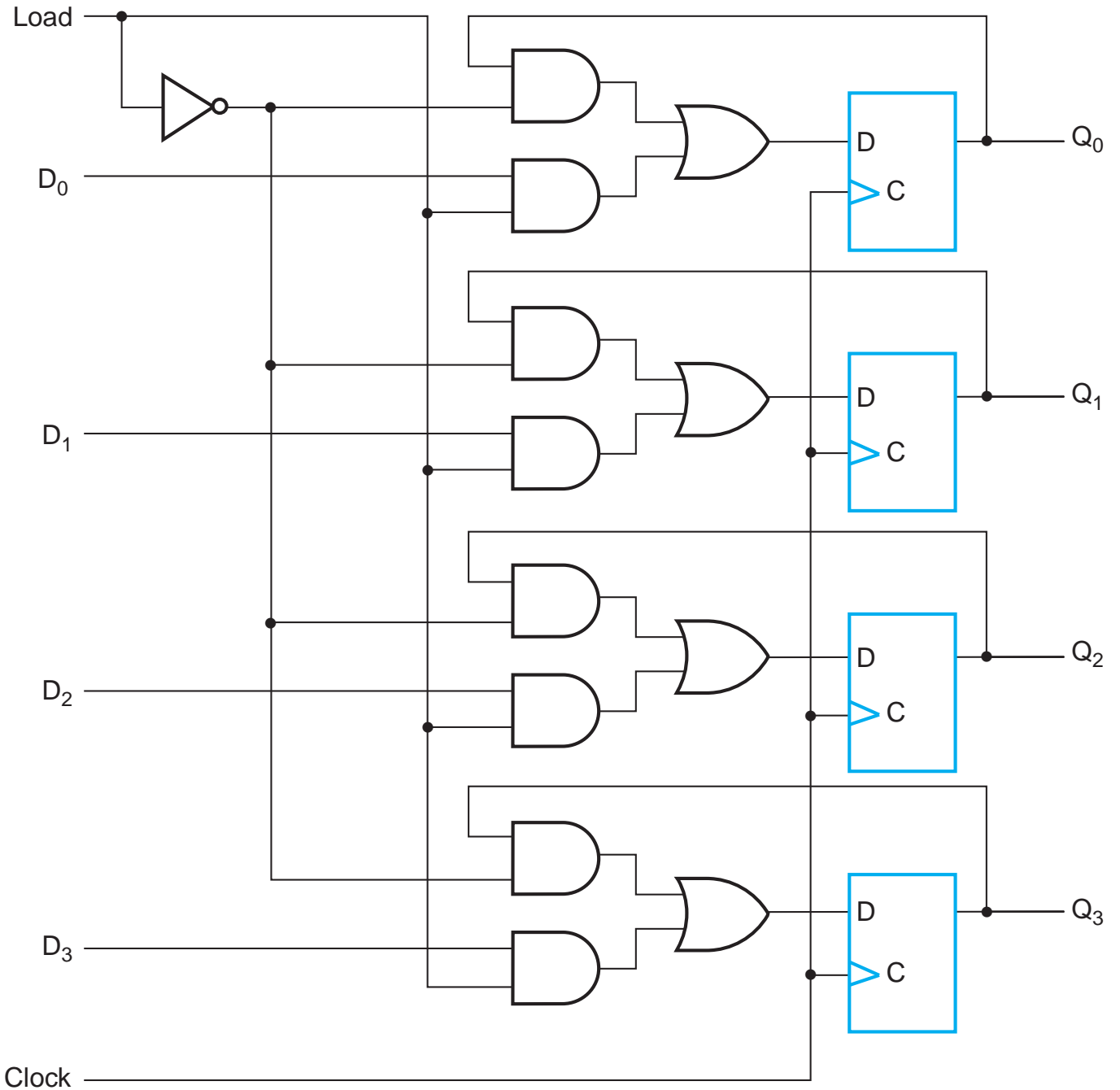

4-Bit Shift Register

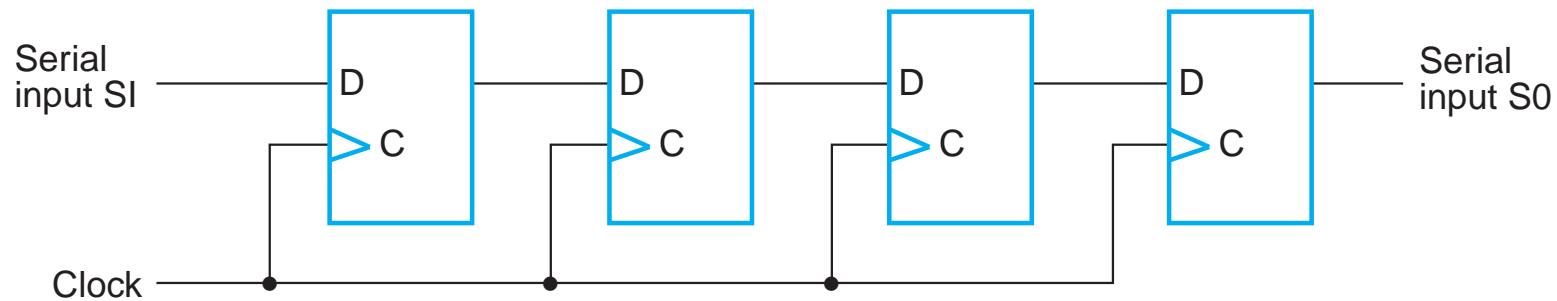


(a) Logic diagram

 


(b) Symbol

Serial Transfer

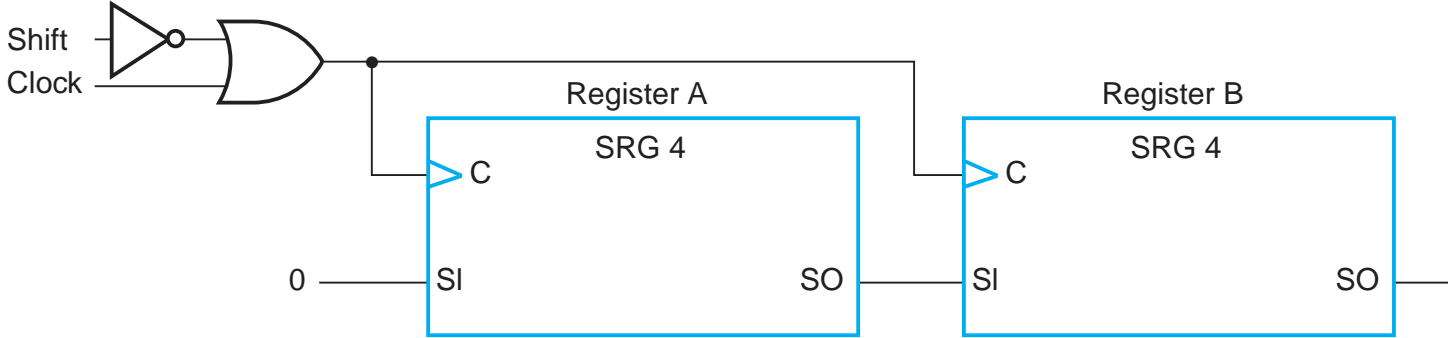


(a) Block diagram

 


(b) Timing diagram


Serial Addition

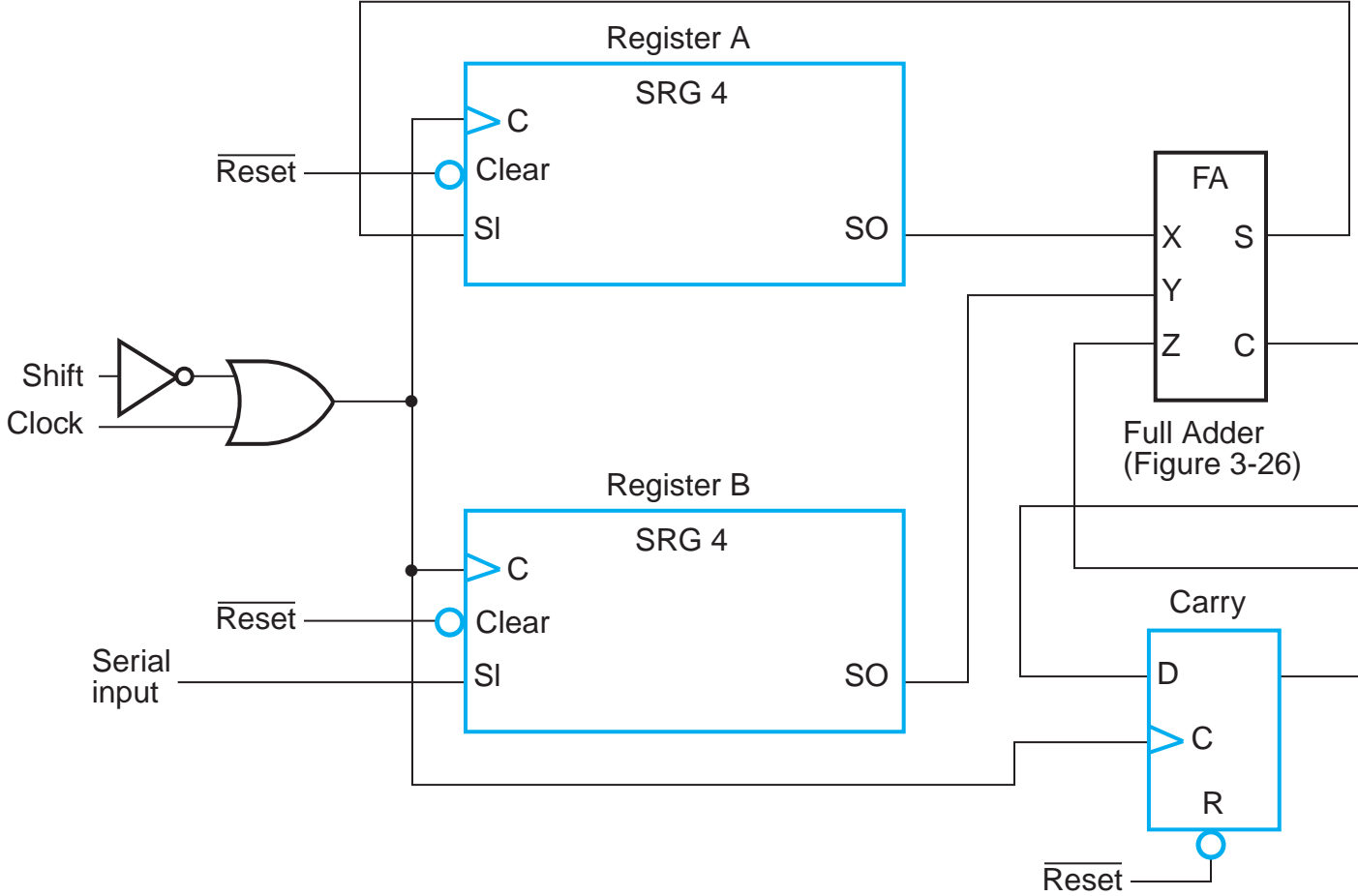


Shift Register with Parallel Load

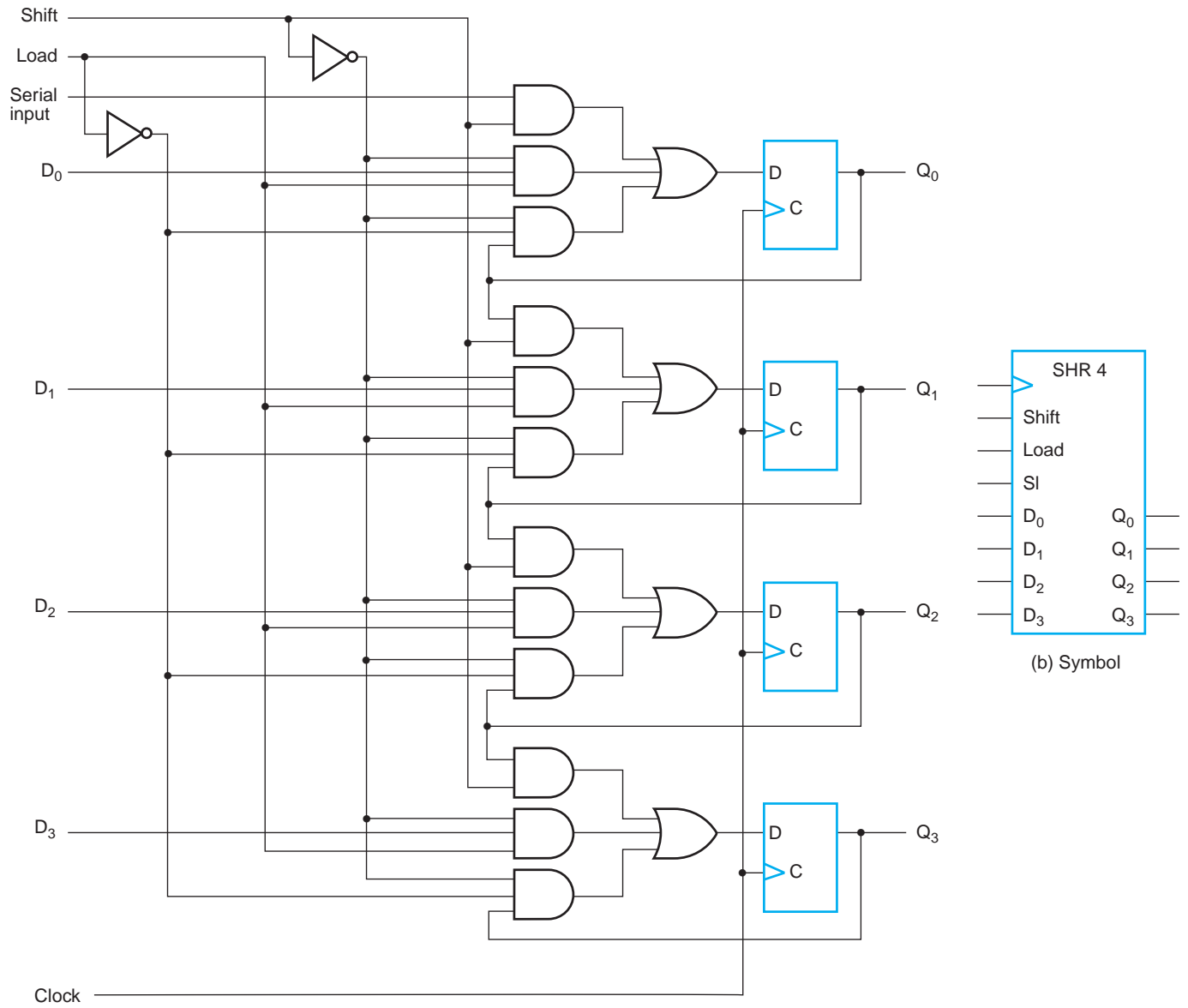

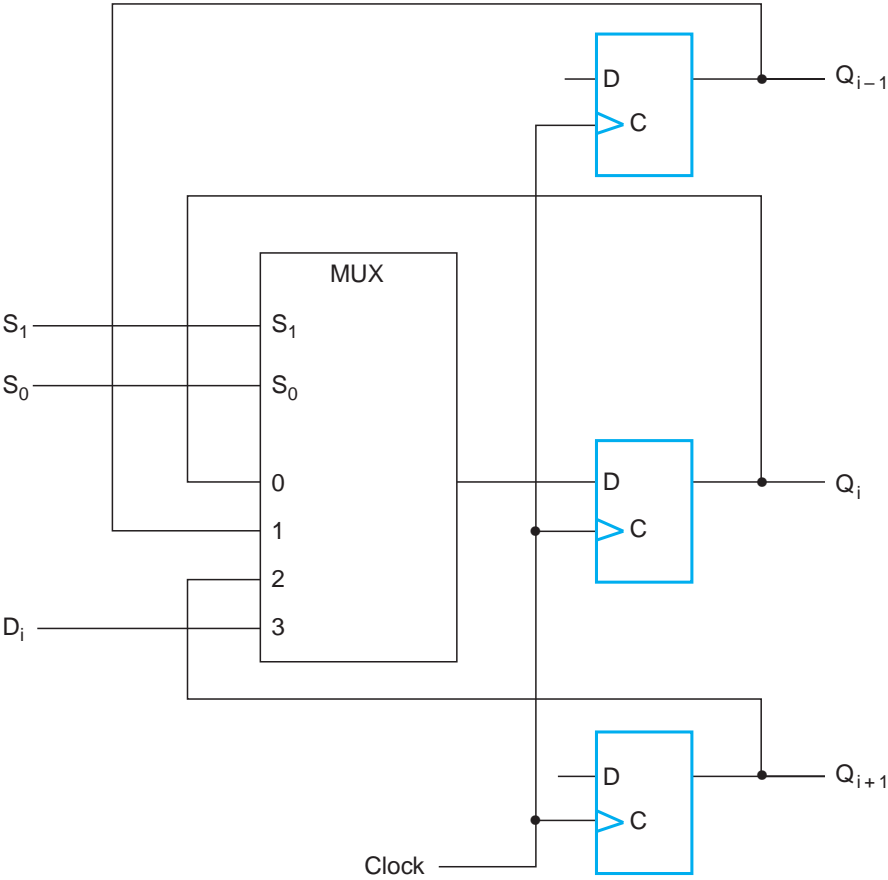Bidirectional Shift Register with Parallel Load




(a) Logic diagram of one typical stage

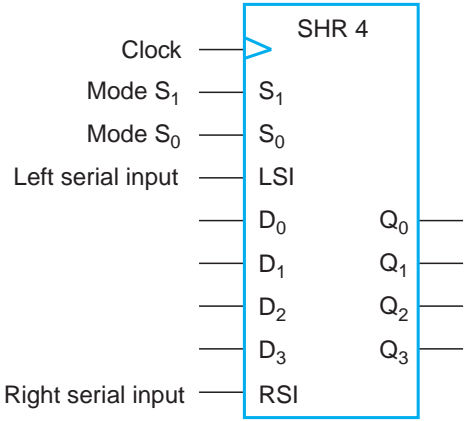


(b) Symbol


4-Bit Ripple Counter

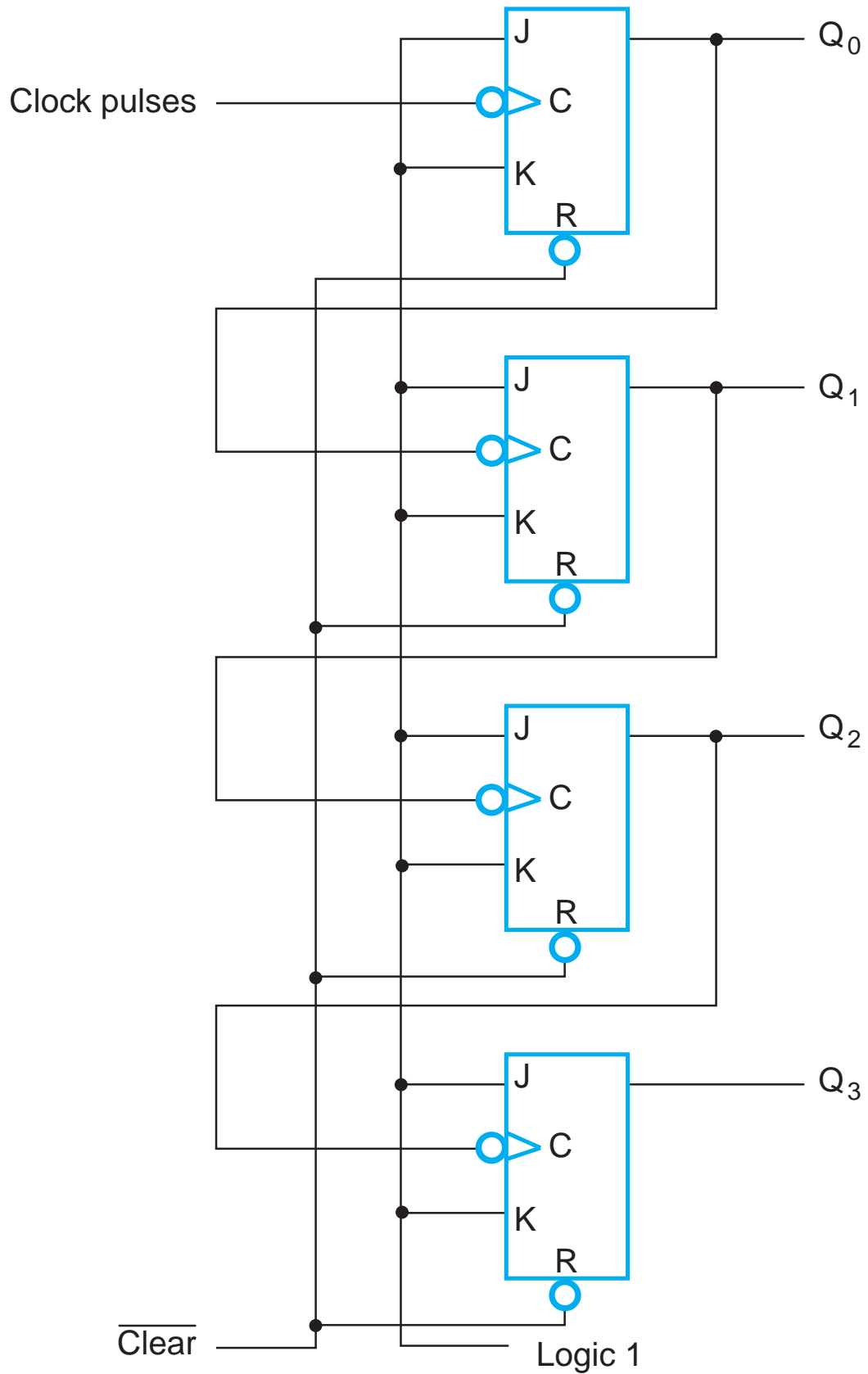

 
Maps for Input Equations of a Binary Counter




$J_{Q3} = Q_0 Q_1 Q_2$

 


$K_{Q3} = Q_0 Q_1 Q_2$

 


$J_{Q2} = Q_0 Q_1$

 

$K_{Q2} = Q_0 Q_1$

 


$J_{Q1} = Q_0$

 


$K_{Q1} = Q_0$

4-Bit Synchronous Binary Counter

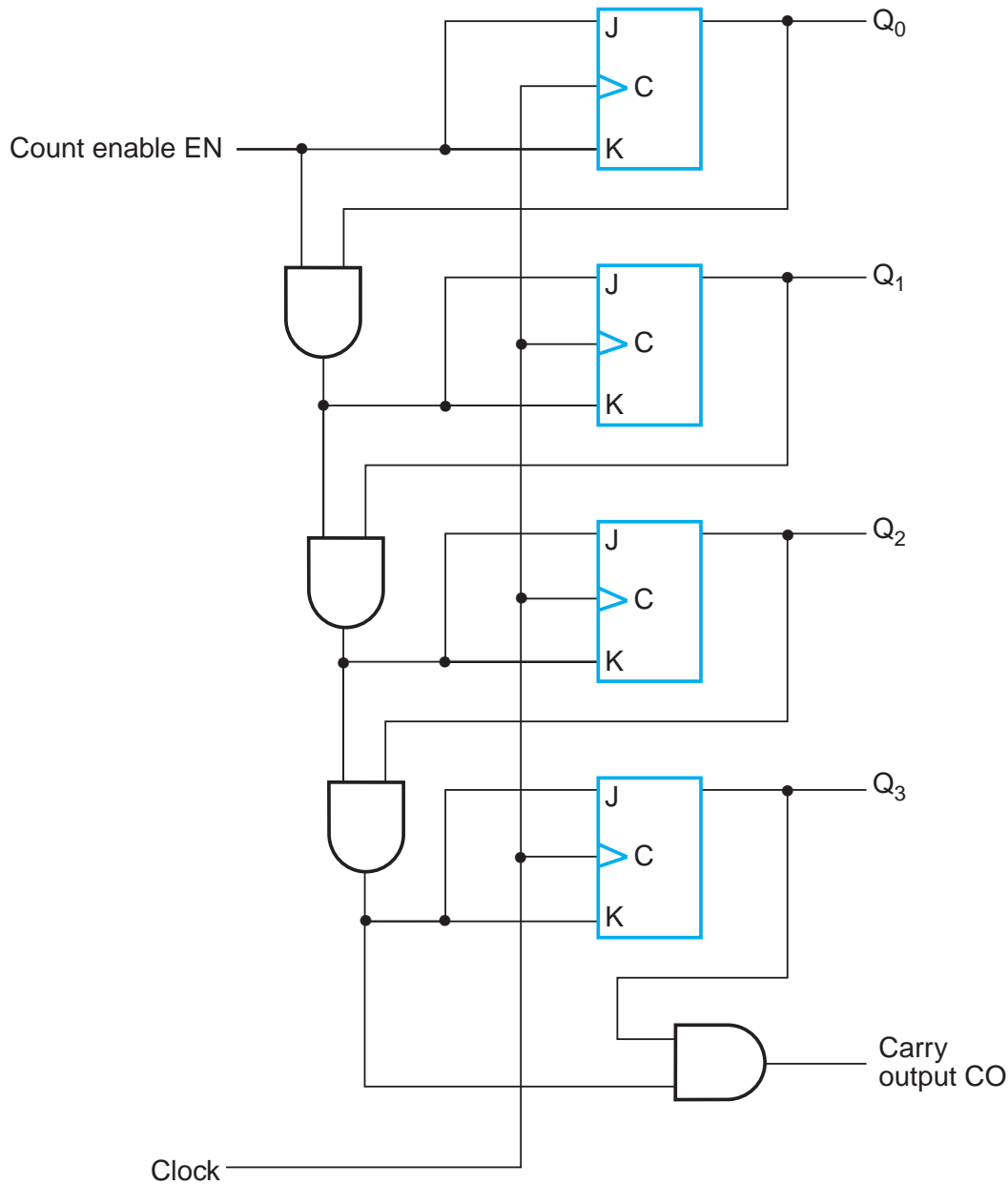


(a) Logic diagram

 

(b) Symbol


4-Bit Binary Counter with *D* Flip-Flops

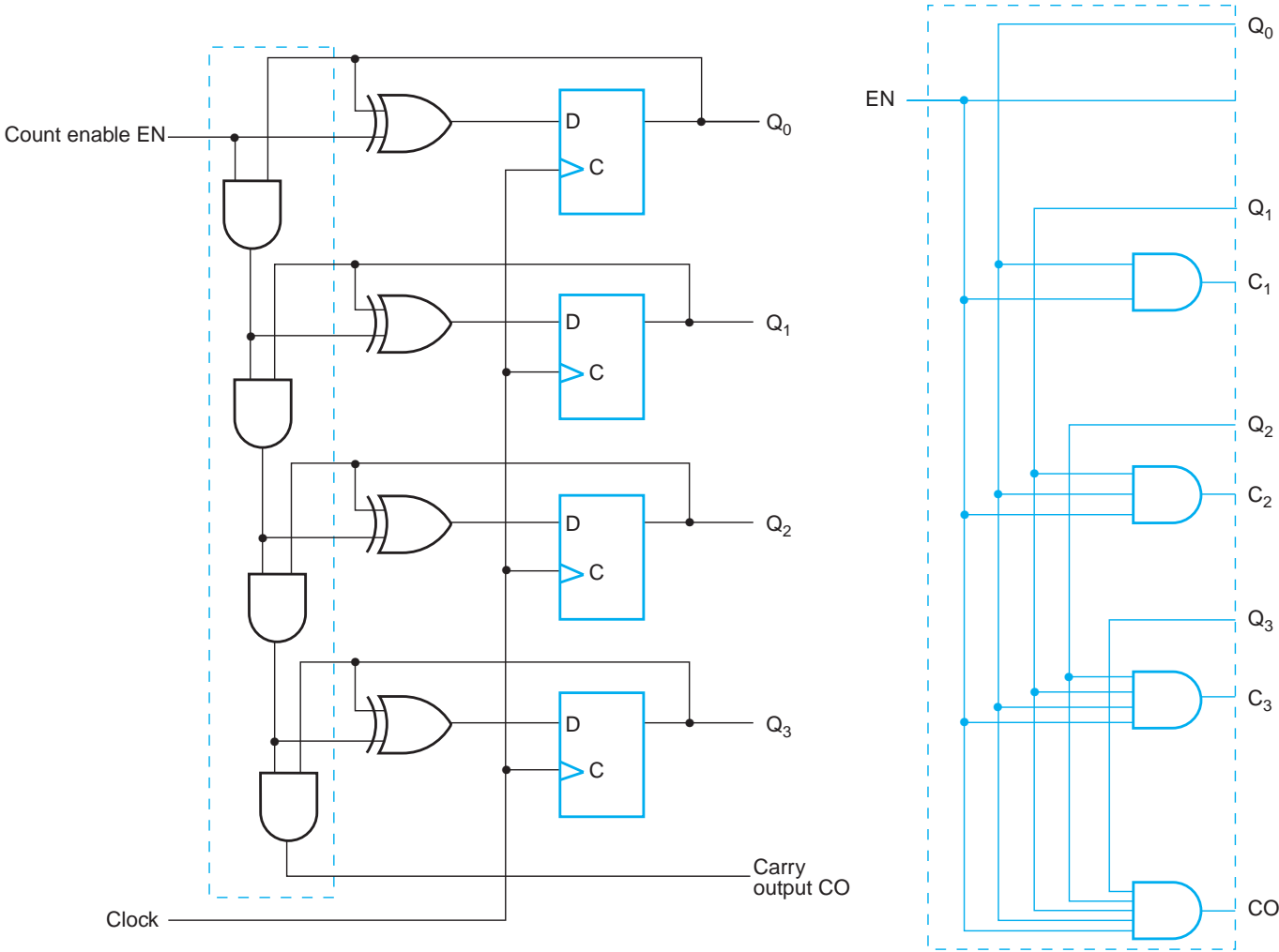


(a) Serial gating

(b) Parallel gating


4-Bit Binary Counter with Parallel Load

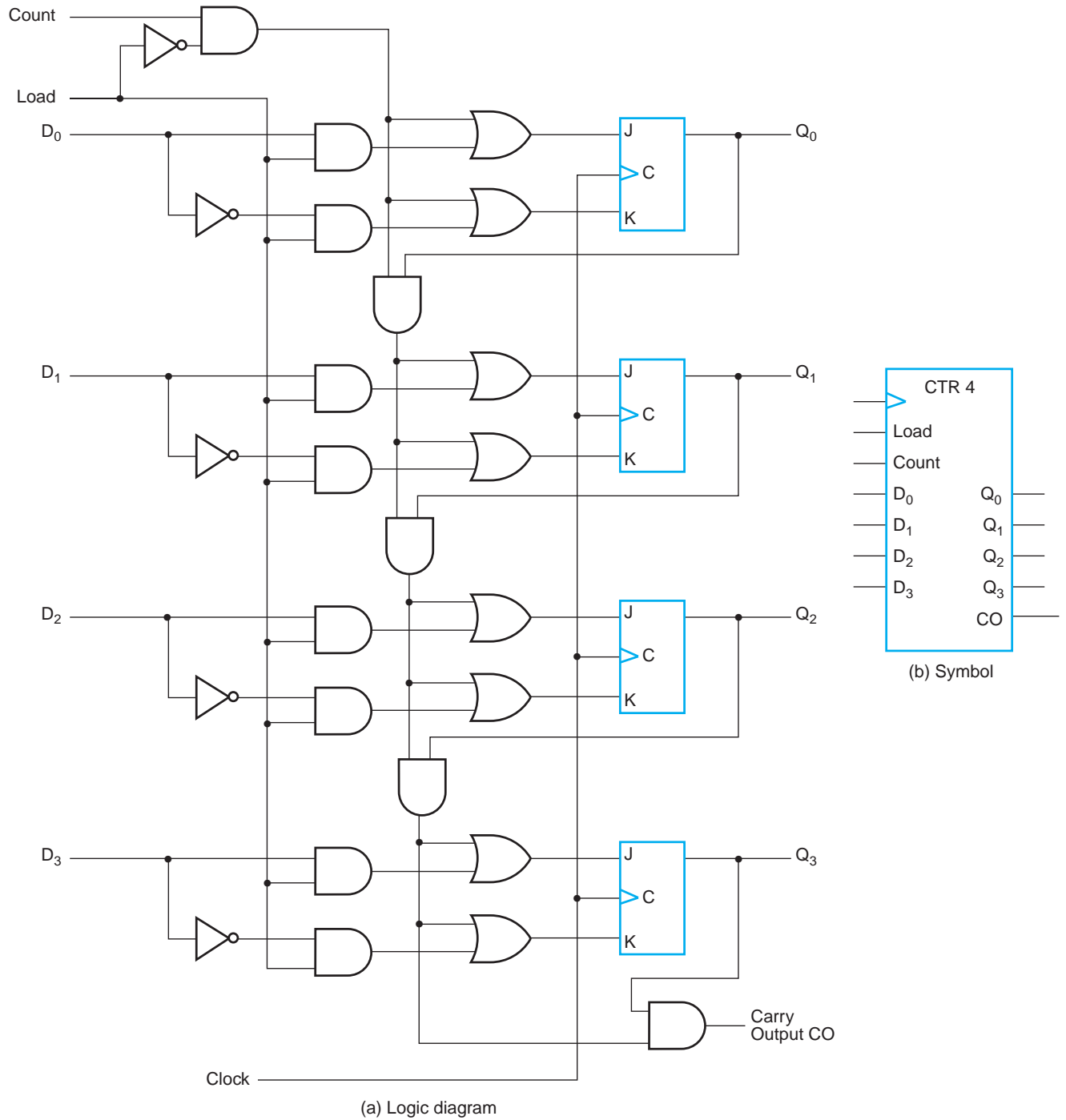


BCD Counter

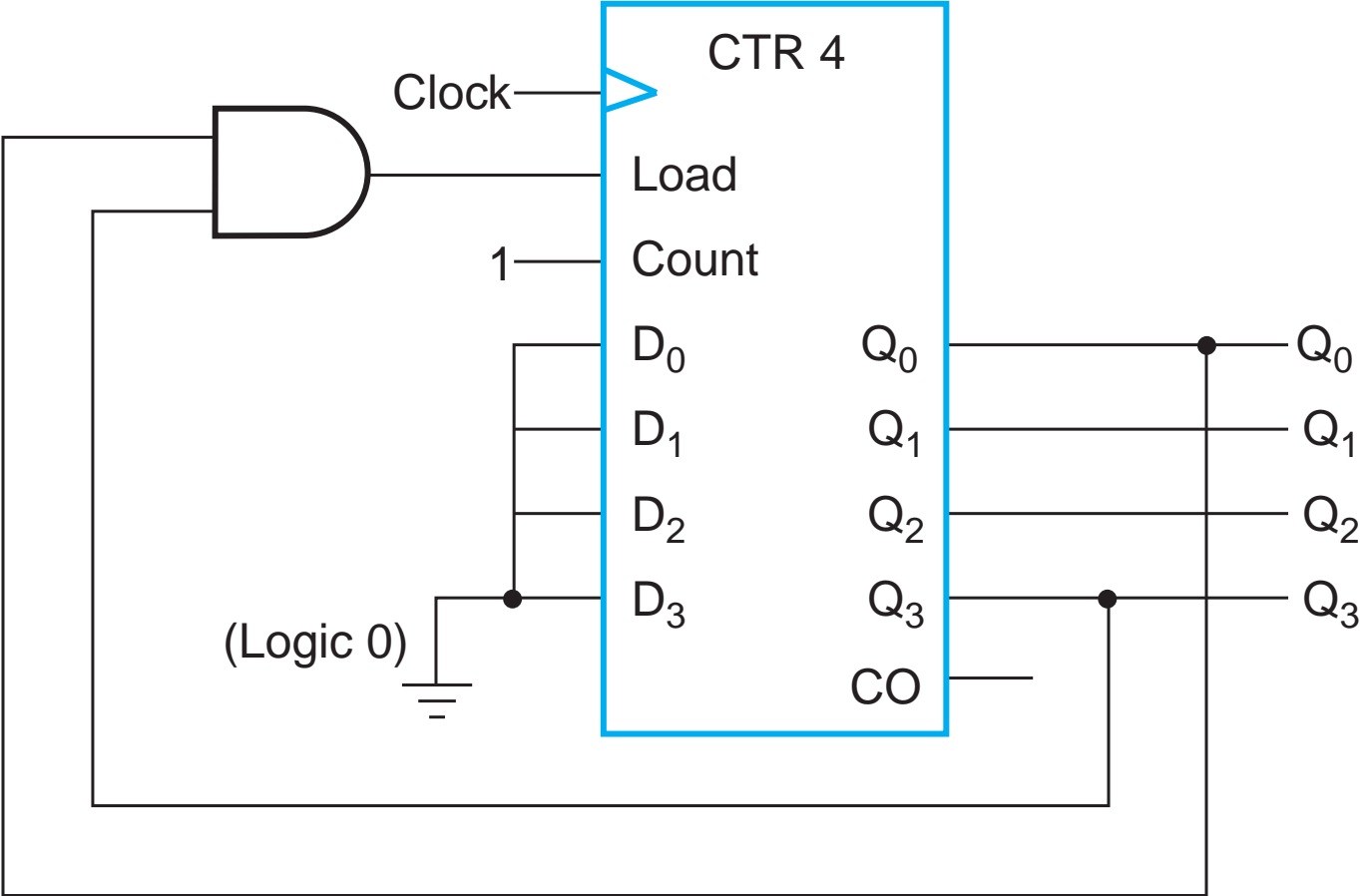

Counter with Arbitrary Count

 


(a) Logic diagram

 


(b) State diagram


Standard Graphics Symbols for Registers

 

(a) 4-bit register

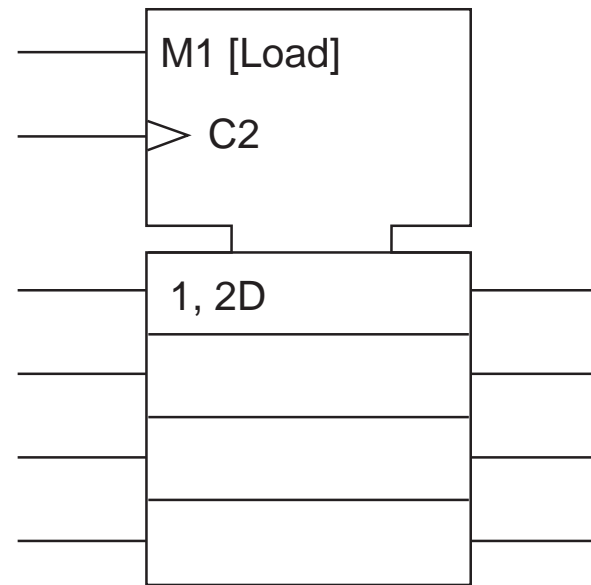

(b) 4-bit register with parallel load

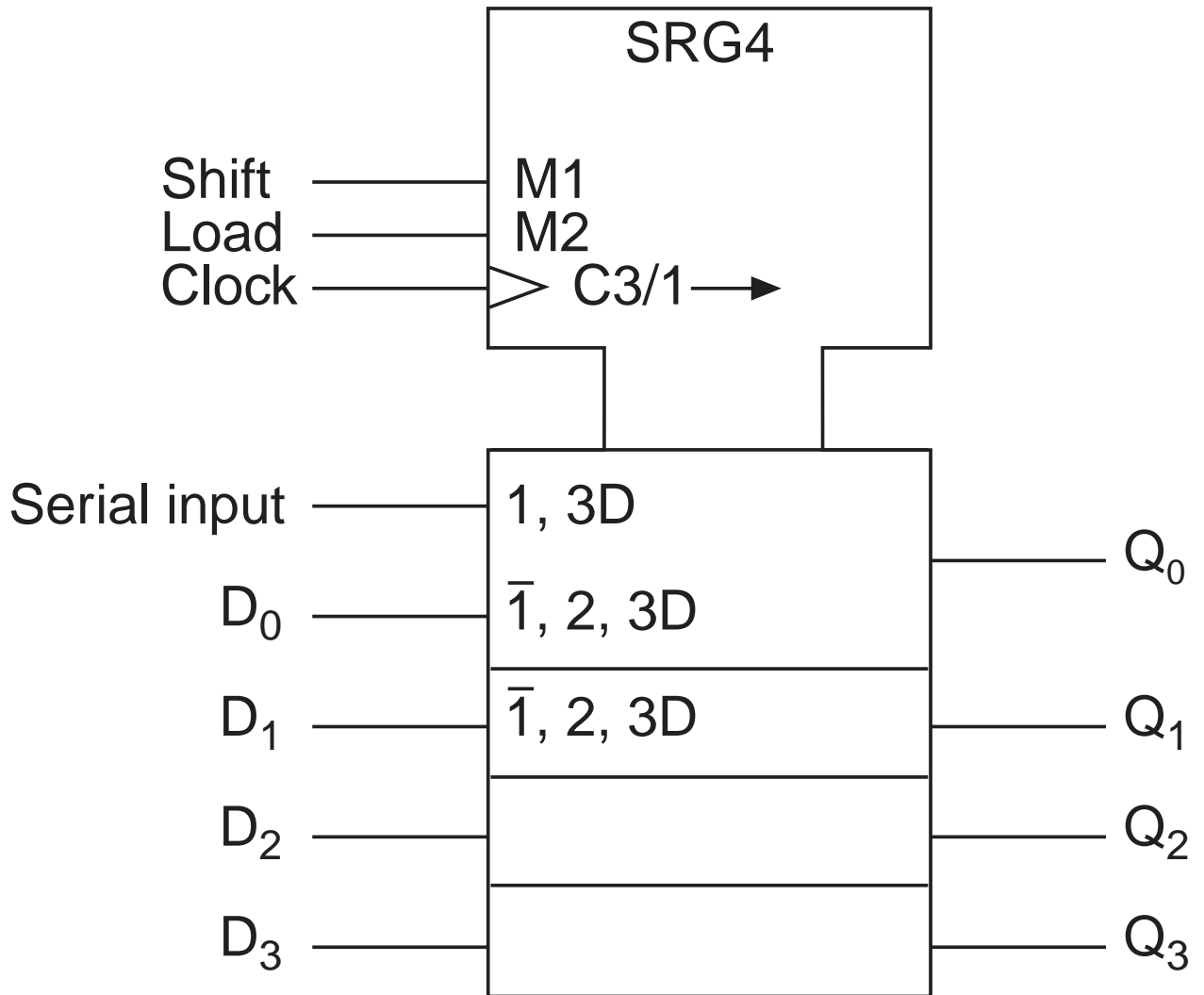

T-124 Graphic Symbol for a 4-Bit Binary Counter with Parallel Load

