

## Basic Symbols for Register Transfers

Symbol	Description	Examples
Letters (and numerals)	Denotes a register	$AR, R2, DR, IR$
Parentheses	Denotes a part of a register	$R2(1), R2(7:0), AR(L)$
Arrow	Denotes transfer of data	$R1 \leftarrow R2$
Comma	Separates simultaneous transfers	$R1 \leftarrow R2, R2 \leftarrow R1$
Square brackets	Specifies an address for memory	$DR \leftarrow M[AR]$

Symbolic designation	Description
$R0 \leftarrow R1 + R2$	Contents of $R1$ plus $R2$ transferred to $R0$
$R2 \leftarrow \overline{R2}$	Complement of the contents of $R2$ (1's complement)
$R2 \leftarrow \overline{R2} + 1$	2's complement of the contents of $R2$
$R0 \leftarrow R1 + \overline{R2} + 1$	$R1$ plus 2's complement of $R2$ transferred to $R0$ (subtraction)
$R1 \leftarrow R1 + 1$	Increment the contents of $R1$ (count up)
$R1 \leftarrow R1 - 1$	Decrement the contents of $R1$ (count down)

---

Symbolic designation	Description
$R0 \leftarrow \overline{R1}$	Logical bitwise NOT (1's complement)
$R0 \leftarrow R1 \wedge R2$	Logical bitwise AND (clears bits)
$R0 \leftarrow R1 \vee R2$	Logical bitwise OR (sets bits)
$R0 \leftarrow R1 \oplus R2$	Logical bitwise XOR (complements bits)

---

## Function Table for Arithmetic Circuit

Select		Input	$G = A + Y + C_{in}$	
$S_1$	$S_0$	$Y$	$C_{in} = 0$	$C_{in} = 1$
0	0	all 0's	$G = A$ (transfer)	$G = A + 1$ (increment)
0	1	$B$	$G = A + B$ (add)	$G = A + B + 1$
1	0	$\overline{B}$	$G = A + \overline{B}$	$G = A + \overline{B} + 1$ (subtract)
1	1	all 1's	$G = A - 1$ (decrement)	$G = A$ (transfer)

## Function Table for ALU

Operation Select				Operation	Function
$S_2$	$S_1$	$S_0$	$C_{in}$		
0	0	0	0	$G = A$	Transfer $A$
0	0	0	1	$G = A + 1$	Increment $A$
0	0	1	0	$G = A + B$	Addition
0	0	1	1	$G = A + B + 1$	Add with carry input of 1
0	1	0	0	$G = A + \overline{B}$	$A$ plus 1's complement of $B$
0	1	0	1	$G = A + \overline{B} + 1$	Subtraction
0	1	1	0	$G = A - 1$	Decrement $A$
0	1	1	1	$G = A$	Transfer $A$
1	0	0	X	$G = A \wedge B$	AND
1	0	1	X	$G = A \vee B$	OR
1	1	0	X	$G = A \oplus B$	XOR
1	1	1	X	$G = \overline{A}$	NOT (1's complement)

## Function Table for 4-Bit Barrel Shifter

Select		Output				Operation
$S_1$	$S_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$	
0	0	$D_3$	$D_2$	$D_1$	$D_0$	No rotation
0	1	$D_2$	$D_1$	$D_0$	$D_3$	Rotate one position
1	0	$D_1$	$D_0$	$D_3$	$D_2$	Rotate two positions
1	1	$D_0$	$D_3$	$D_2$	$D_1$	Rotate three positions

## G Select, H Select, and MF Select Codes Defined in Terms of FS Codes

FS	MF Select	G Select	H Select	Microoperation
00000	0	0000	0	$F = A$
00001	0	0001	1	$F = A + 1$
00010	0	0010	0	$F = A + B$
00011	0	0011	1	$F = A + B + 1$
00100	0	0100	0	$F = A + \bar{B}$
00101	0	0101	1	$F = A + \bar{B} + 1$
00110	0	0110	0	$F = A - 1$
00111	0	0111	1	$F = A$
01000	0	1000	0	$F = A \wedge B$
01010	0	1010	0	$F = A \vee B$
01100	0	1100	0	$F = A \oplus B$
01110	0	1110	0	$F = \bar{A}$
10000	1	0000	0	$F = sr A$
10001	1	0001	1	$F = sl A$

## Encoding of Control Word for the Datapath

DA, AA, BA		MB		FS		MD		RW	
Function	Code	Function	Code	Function	Code	Function	Code	Function	Code
<i>R0</i>	000	Register	0	$F = A$	00000	Function	0	No write	0
<i>R1</i>	001	Constant	1	$F = A + 1$	00001	Data In	1	Write	1
<i>R2</i>	010			$F = A + B$	00010				
<i>R3</i>	011			$F = A + B + 1$	00011				
<i>R4</i>	100			$F = A + \bar{B}$	00100				
<i>R5</i>	101			$F = A + \bar{B} + 1$	00101				
<i>R6</i>	110			$F = A - 1$	00110				
<i>R7</i>	111			$F = A$	00111				
				$F = A \wedge B$	01000				
				$F = A \vee B$	01010				
				$F = A \oplus B$	01100				
				$F = \bar{A}$	01110				
				$F = sr A$	10000				
				$F = sl A$	10001				




Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 + \overline{R3} + 1$	$R1$	$R2$	$R3$	Register	$F = A + \overline{B} + 1$	Function	Write
$R4 \leftarrow sl R6$	$R4$	$R6$	—	Register	$F = sl A$	Function	Write
$R7 \leftarrow R7 + 1$	$R7$	$R7$	—	Register	$F = A + 1$	Function	Write
$R1 \leftarrow R0 + 2$	$R1$	—	—	Constant	$F = A + B$	Function	Write
Data out $\leftarrow R3$	—	—	$R3$	Register	—	—	No Write
$R4 \leftarrow$ Data in	$R4$	—	—	—	—	Data in	Write
$R5 \leftarrow 0$	$R5$	$R0$	$R0$	Register	$F = A \oplus B$	Function	Write

T-167                      Examples of Microoperations from Table 7-11, Using Binary Control Words

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	001	010	011	0	00101	0	1
$R4 \leftarrow s1 R6$	100	110	000	0	10001	0	1
$R7 \leftarrow R7 + 1$	111	111	000	0	00001	0	1
$R1 \leftarrow R0 + 2$	001	000	000	1	00010	0	1
Data out $\leftarrow R3$	000	000	011	0	00000	0	0
$R4 \leftarrow$ Data in	100	000	000	0	00000	1	1
$R5 \leftarrow 0$	101	000	000	0	01100	0	1

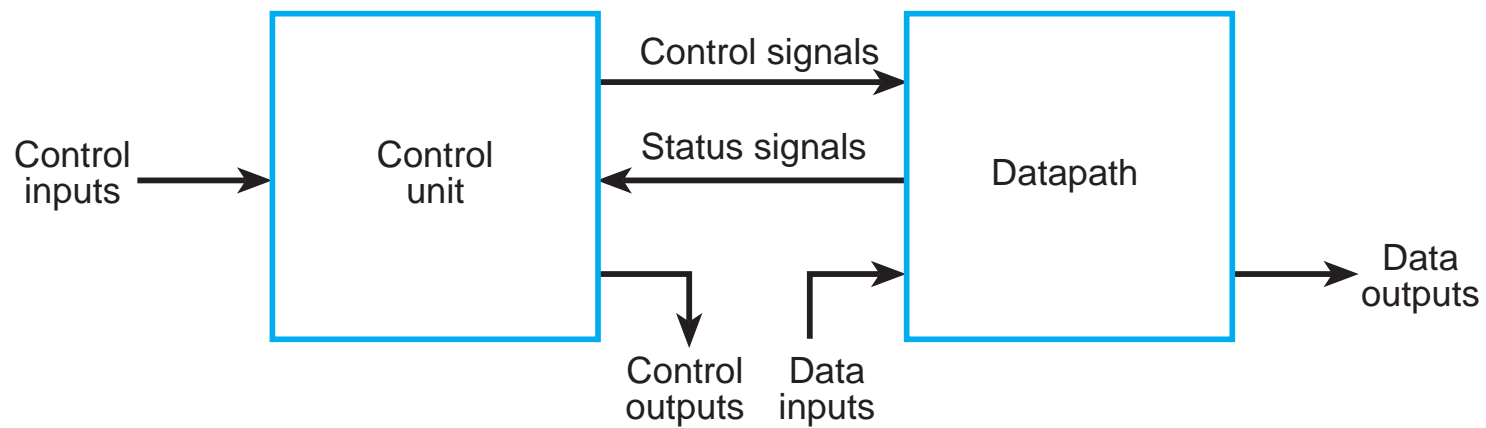
## Interaction between Datapath and Control Unit



## Block Diagrams of Registers




(a) Register R

 

(b) Individual bits of 8-bit register





(c) Numbering of 16-bit register

 


(d) Two-part 16-bit register

T-170

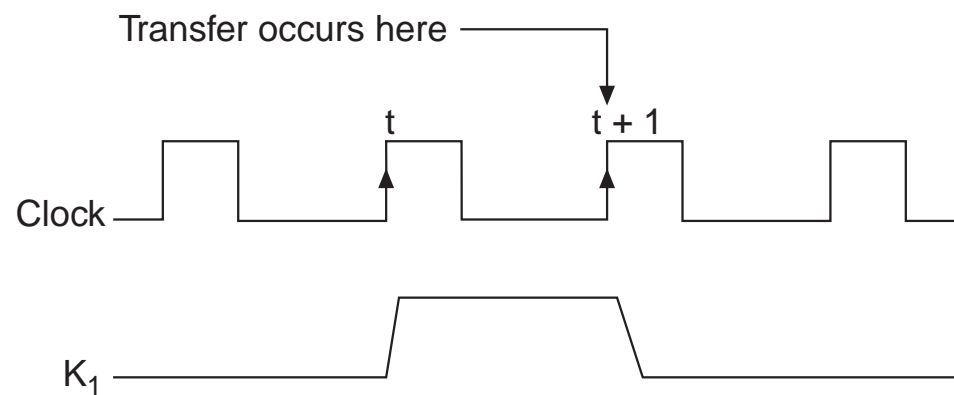 
### Transfer from R1 to R2 when $K_1 = 1$



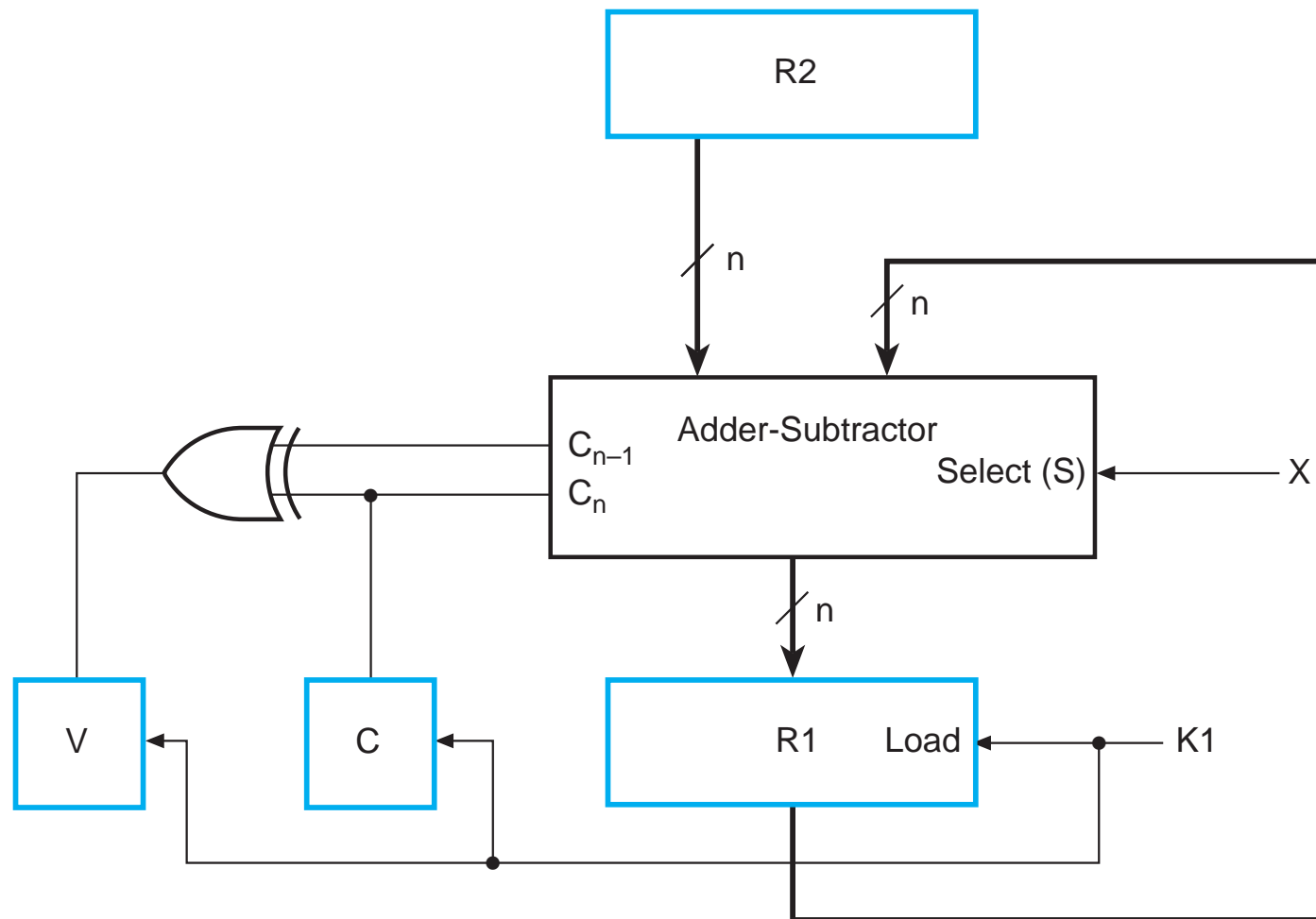
### Implementation of Add and Subtract Microoperations



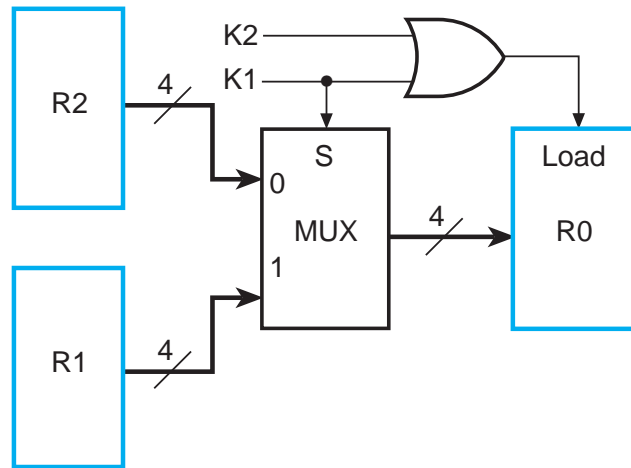
# Use of Multiplexers to Select between Two Registers




(a) Block diagram

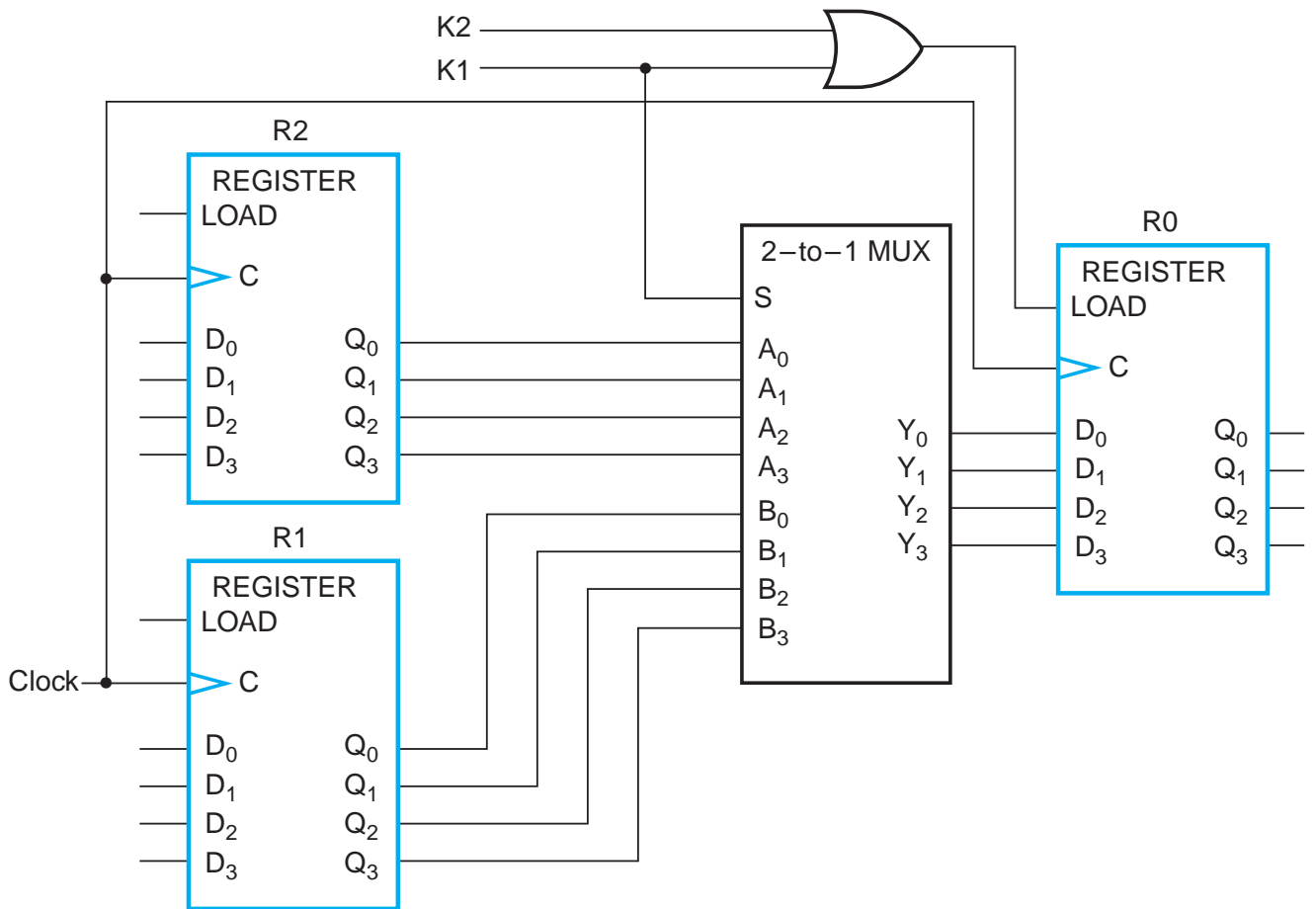

(b) Detailed logic

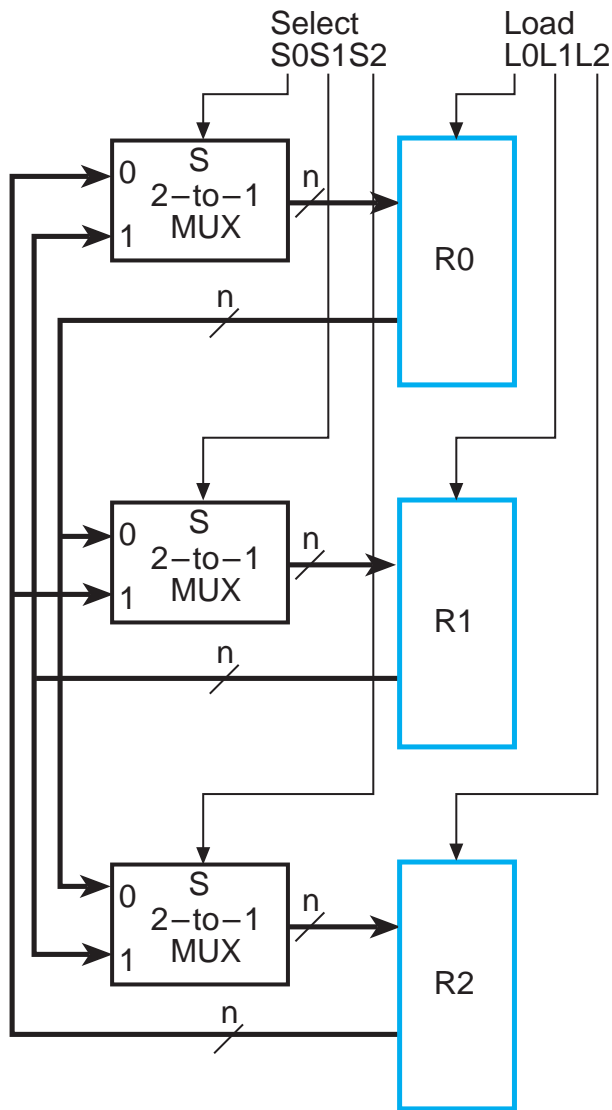


(a) Dedicated multiplexers

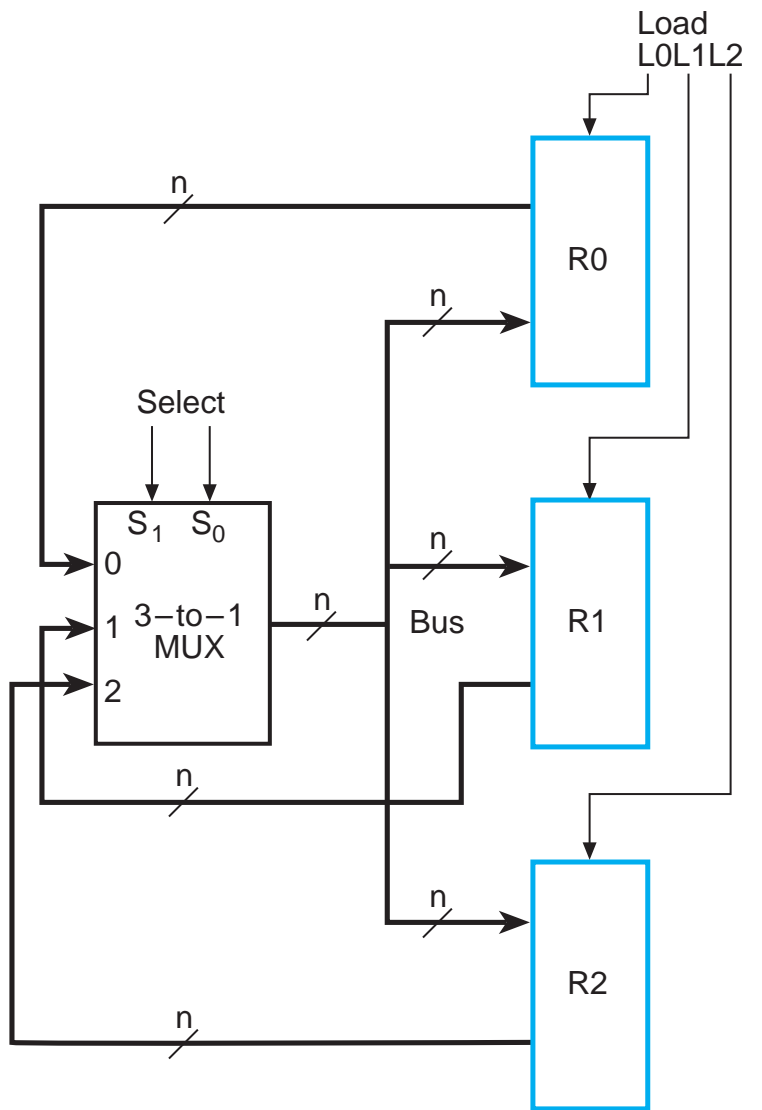


(b) Single Bus




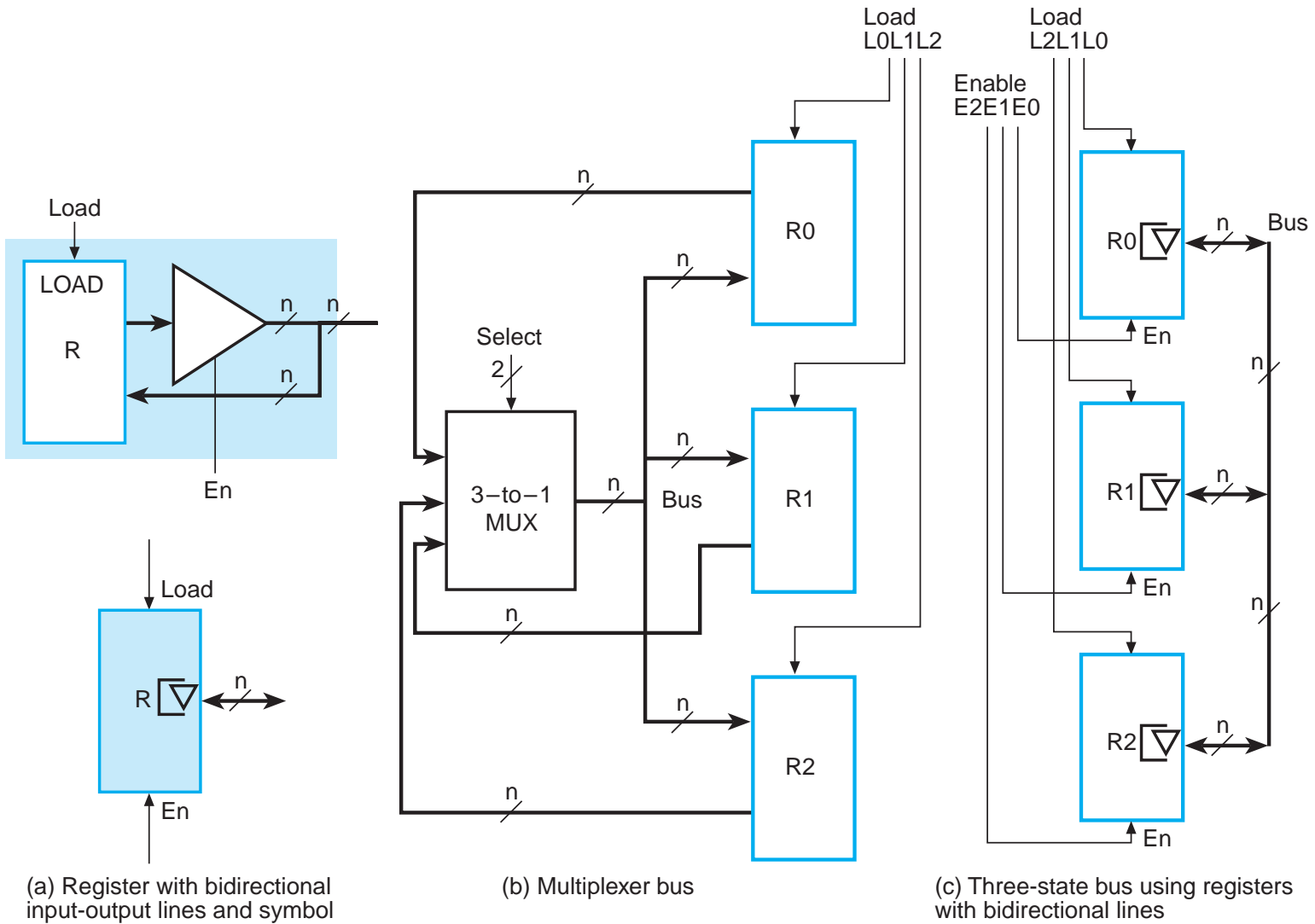
### Three-State Bus versus Multiplexer Bus



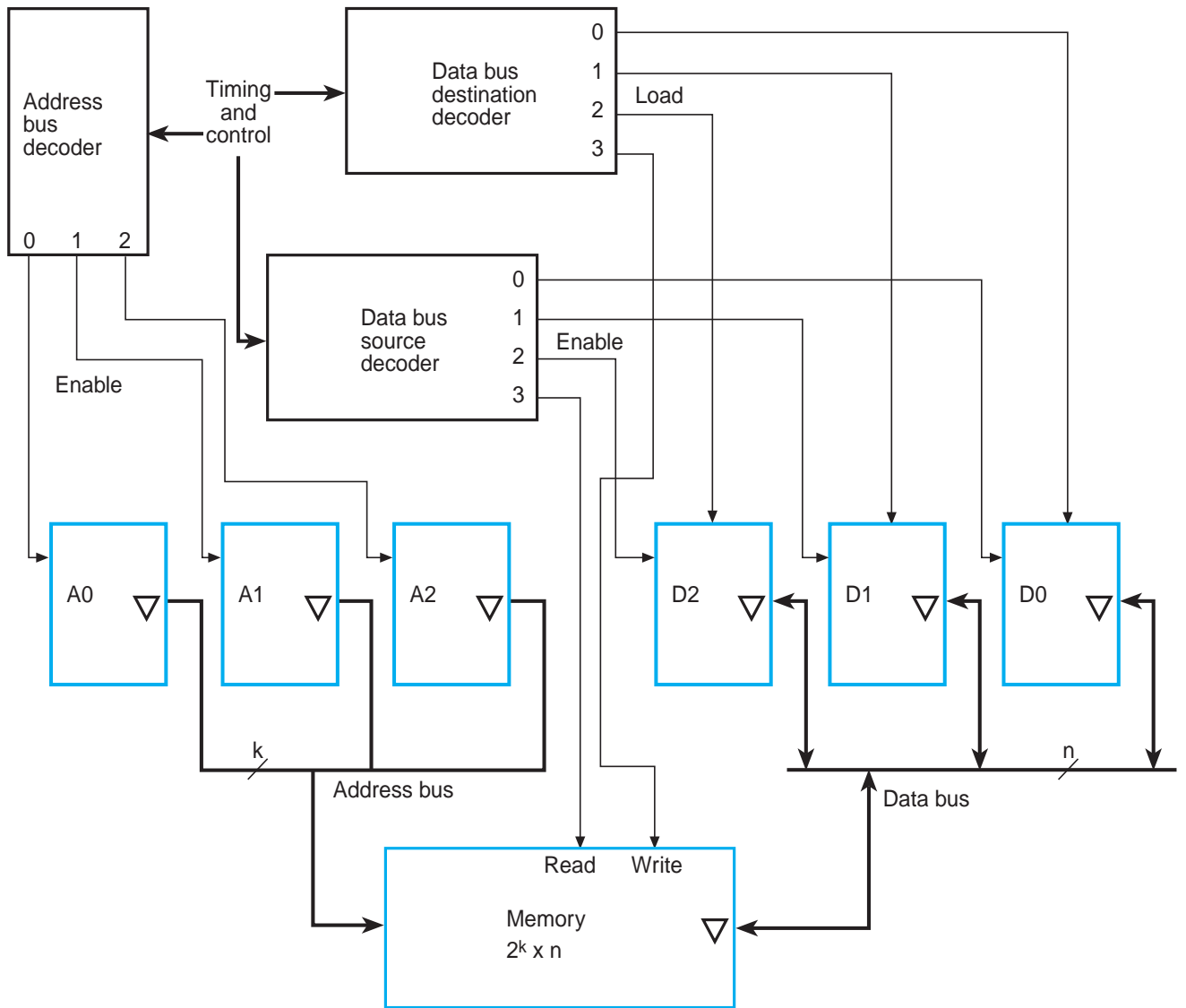


# Block Diagram of a Datapath

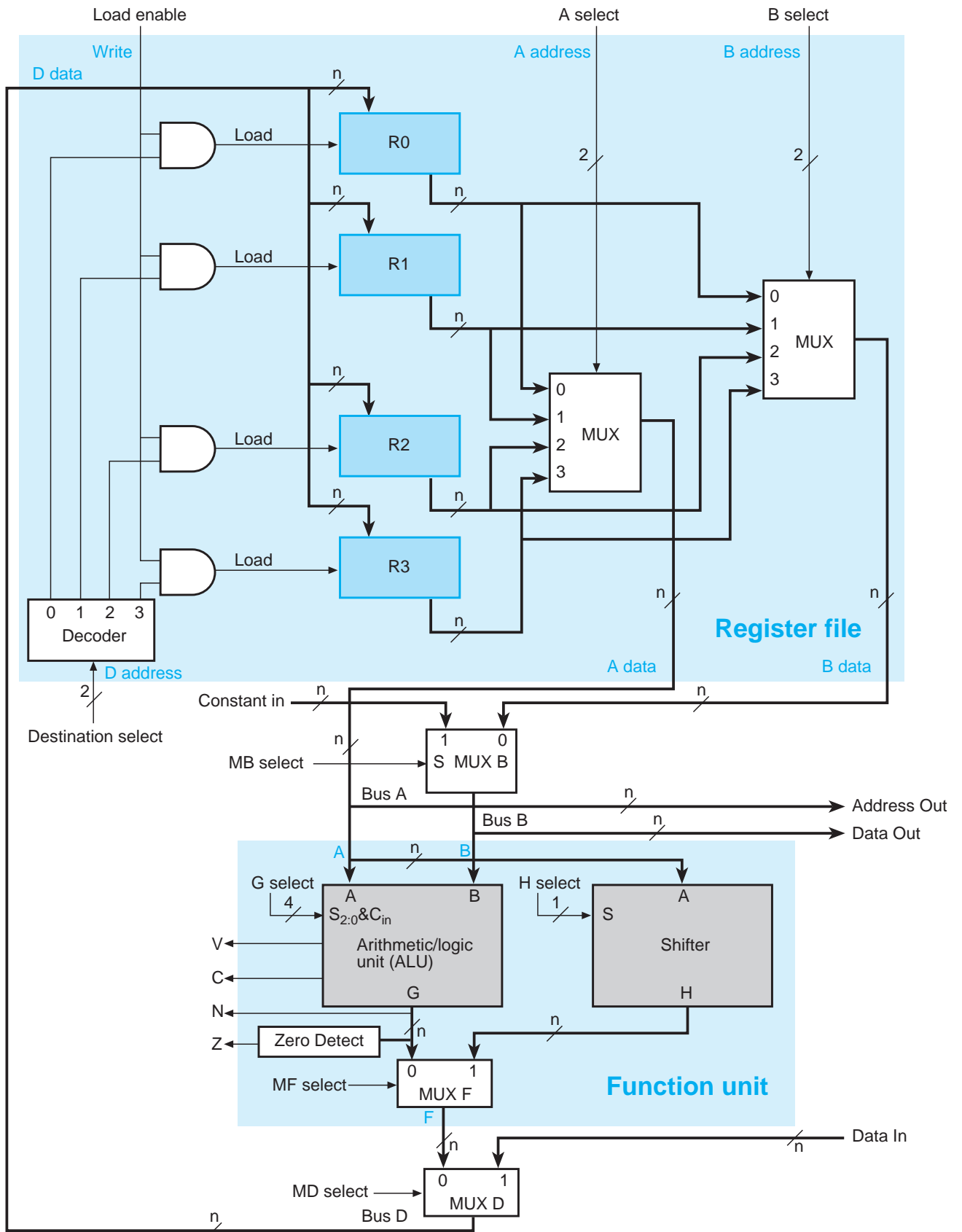

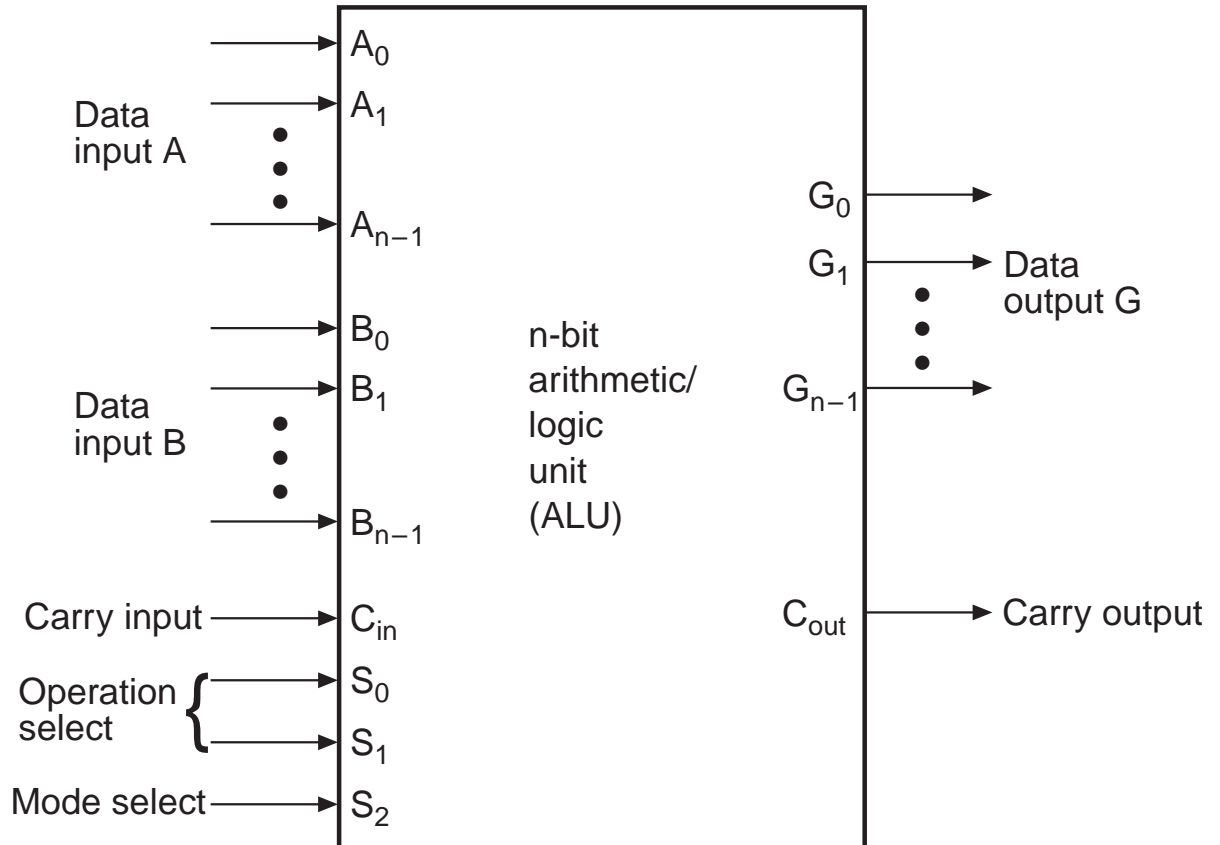Block Diagram of  $n$ -Bit ALU

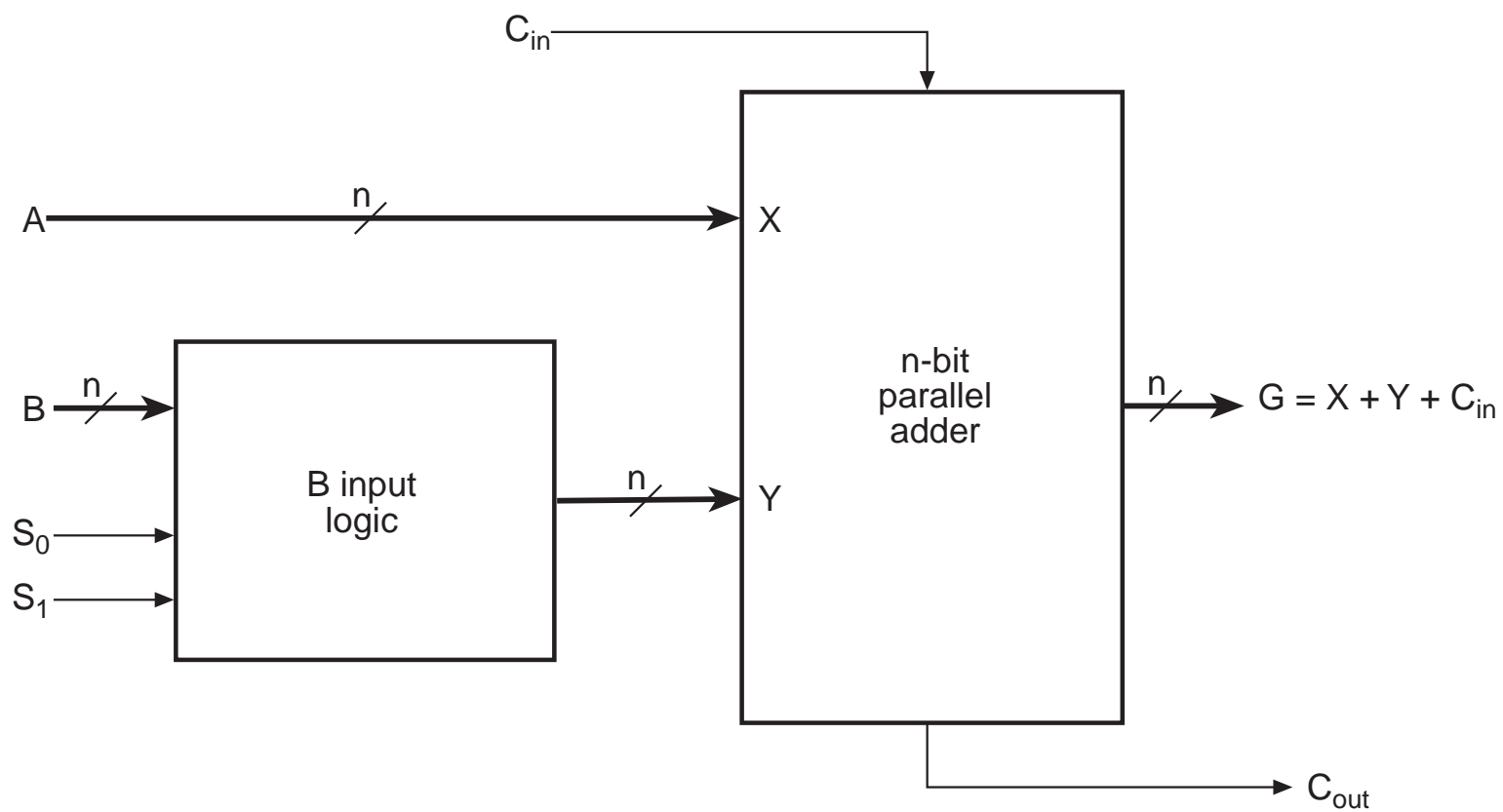
## Block Diagram of an Arithmetic Circuit



## B Input Logic for One Stage of Arithmetic Circuit

Inputs			Output	
$S_1$	$S_0$	$B_i$	$Y_i$	
0	0	0	0	$Y_i = 0$
0	0	1	0	
0	1	0	0	$Y_i = B_i$
0	1	1	1	
1	0	0	1	$Y_i = \bar{B}_i$
1	0	1	0	
1	1	0	1	$Y_i = 1$
1	1	1	1	


(a) Truth table

 

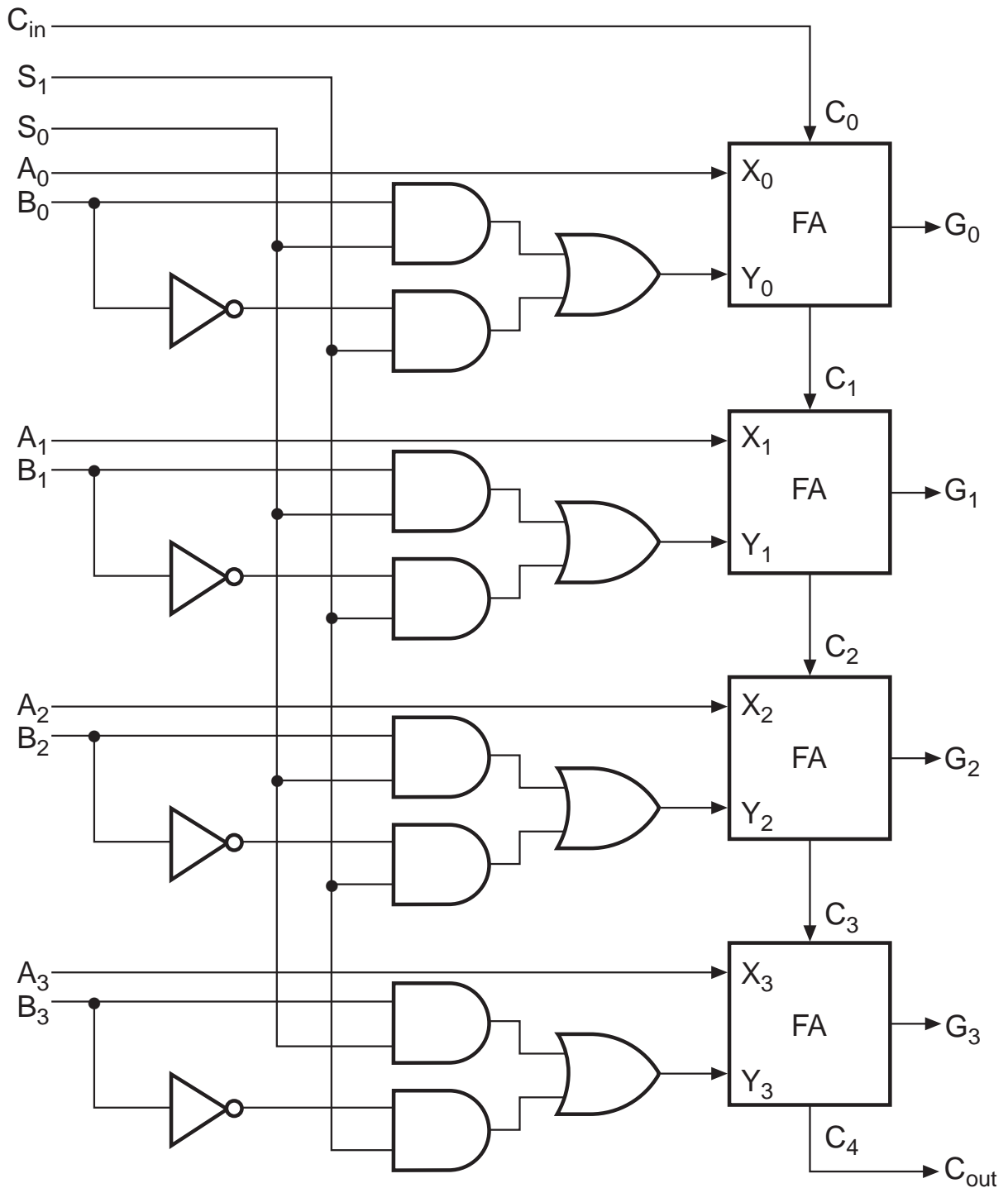
(b) Map Simplification:

$$Y_i = B_i S_0 + \bar{B}_i S_1$$

Logic Diagram of a 4-bit Arithmetic Circuit



## One Stage of Logic Circuit

 


(a) Logic Diagram

$S_1$	$S_0$	Output	Operation
0	0	$G = A \wedge B$	AND
0	1	$G = A \vee B$	OR
1	0	$G = A \oplus B$	XOR
1	1	$G = \bar{A}$	NOT


(b) Function Table




## One Stage of ALU

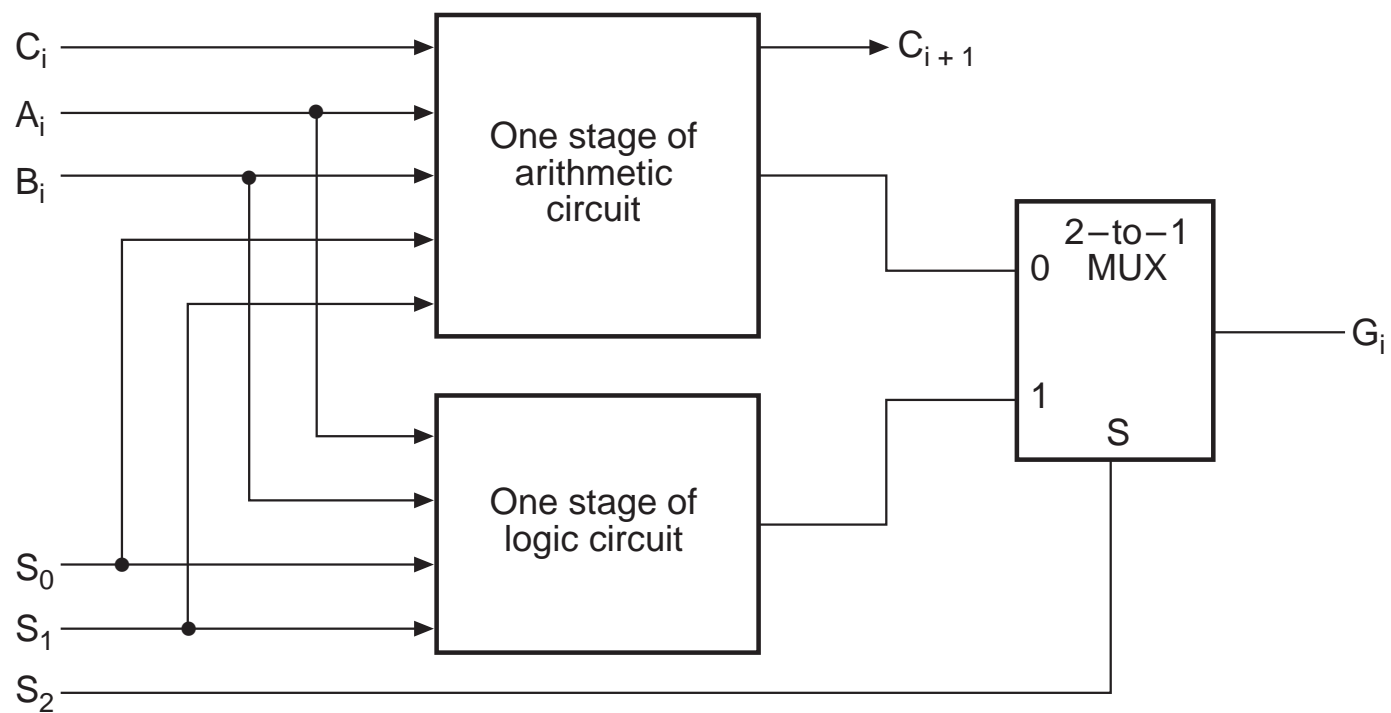


### 4-Bit Basic Shifter

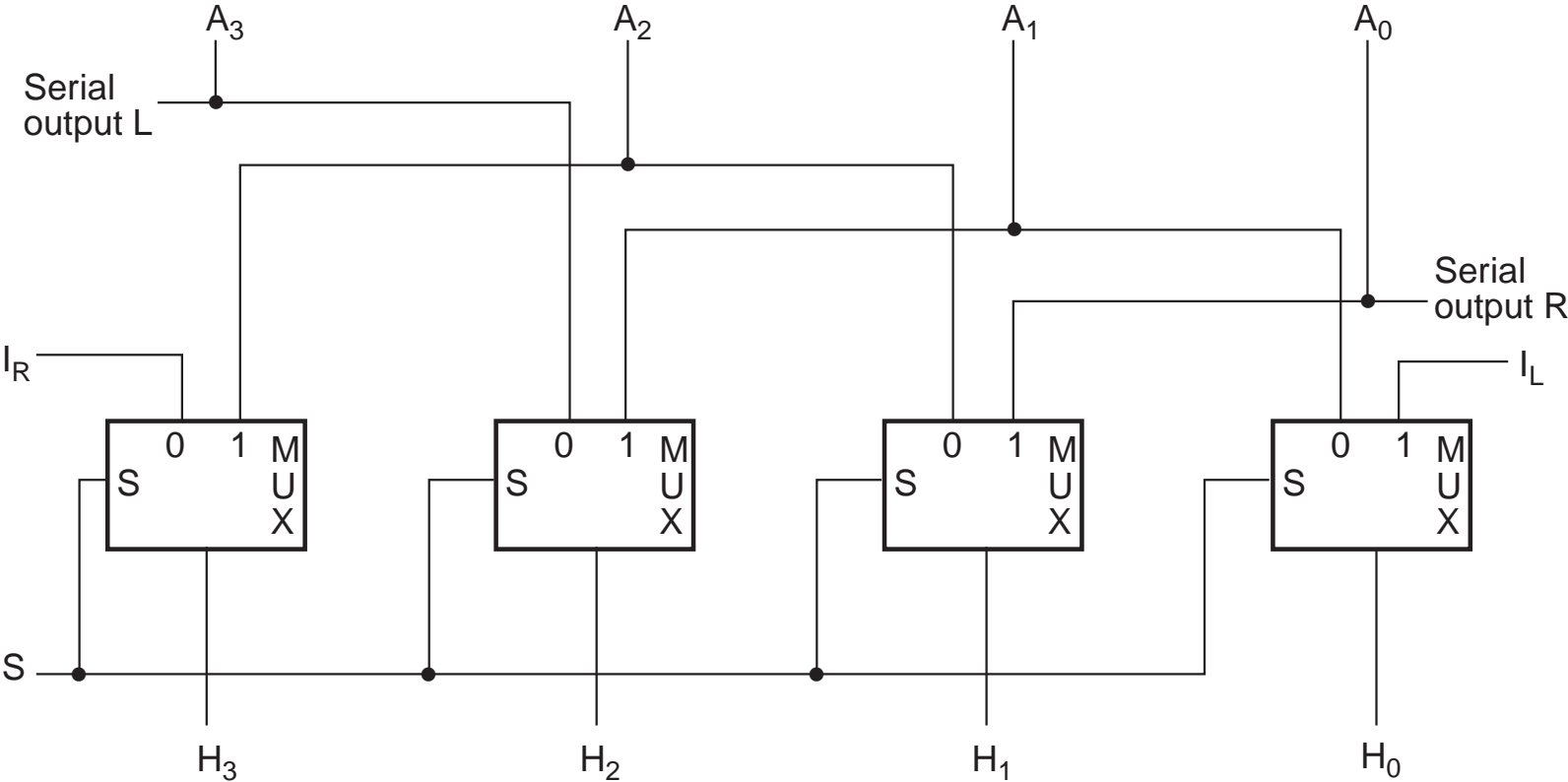


### 4-Bit Barrel Shifter

 

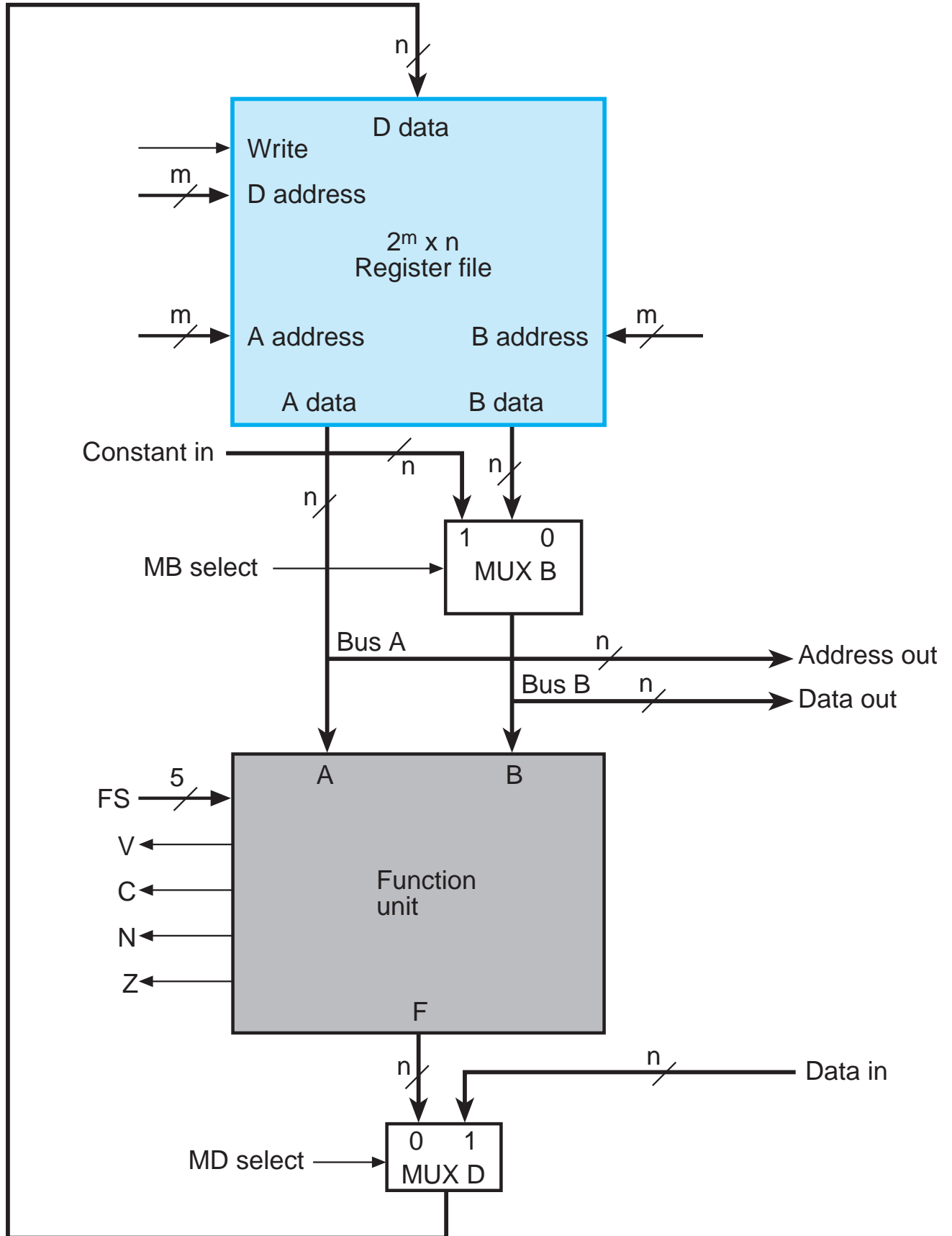
### Block Diagram of Datapath Using the Register File and Function Unit



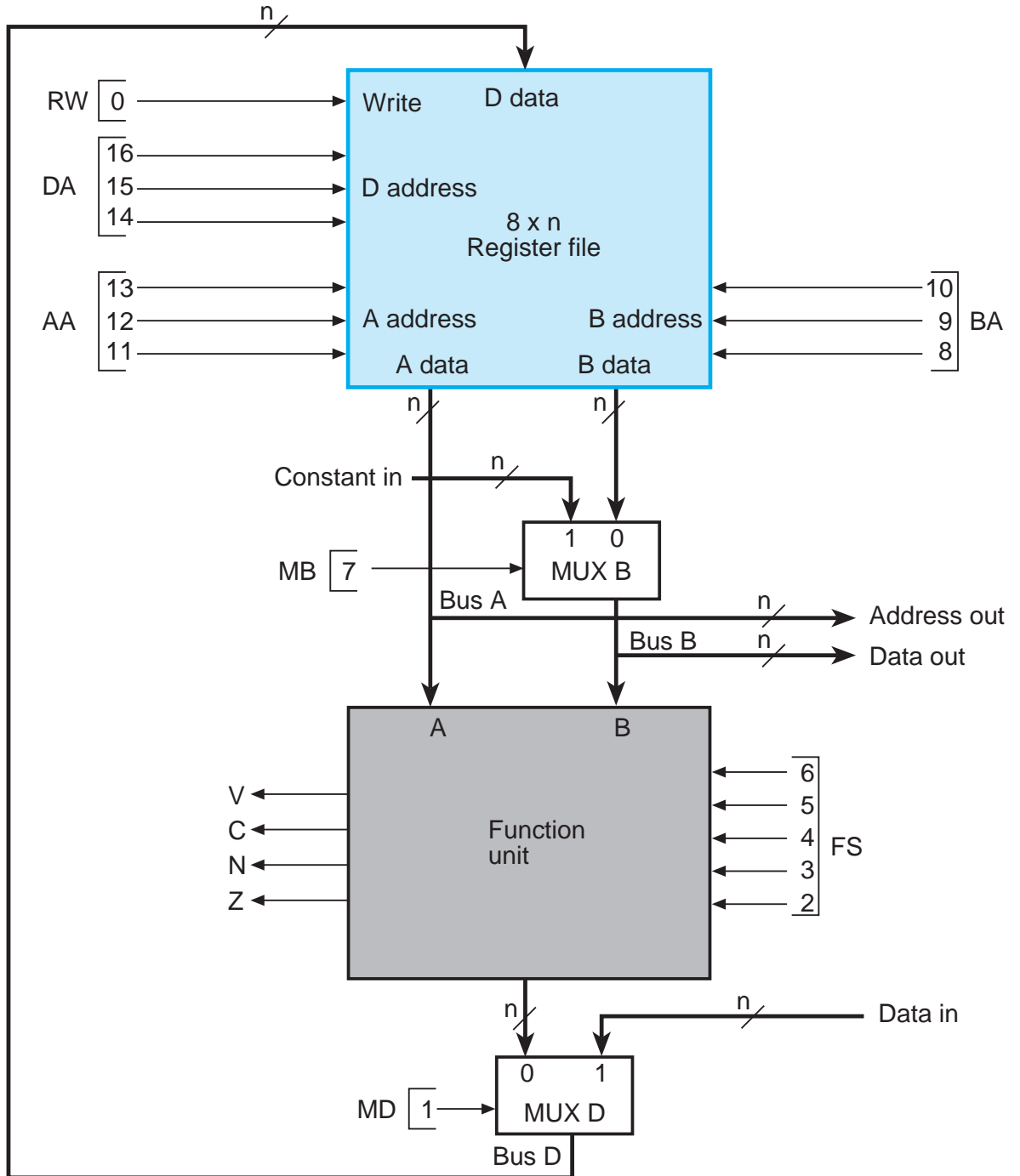



(a) Block Diagram

 


(b) Control word
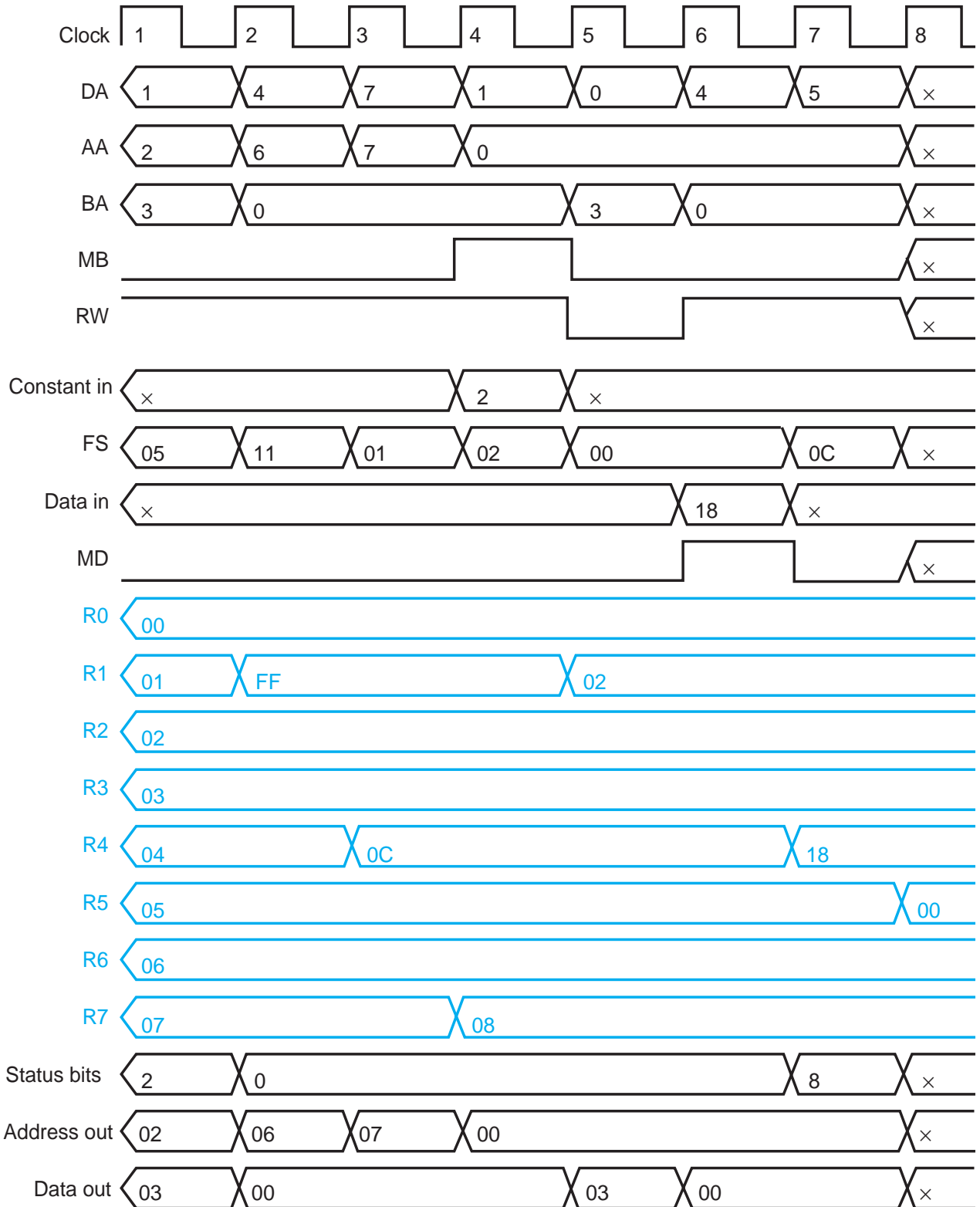
# T-187 Simulation of the Microoperation Sequence in Table 7-12



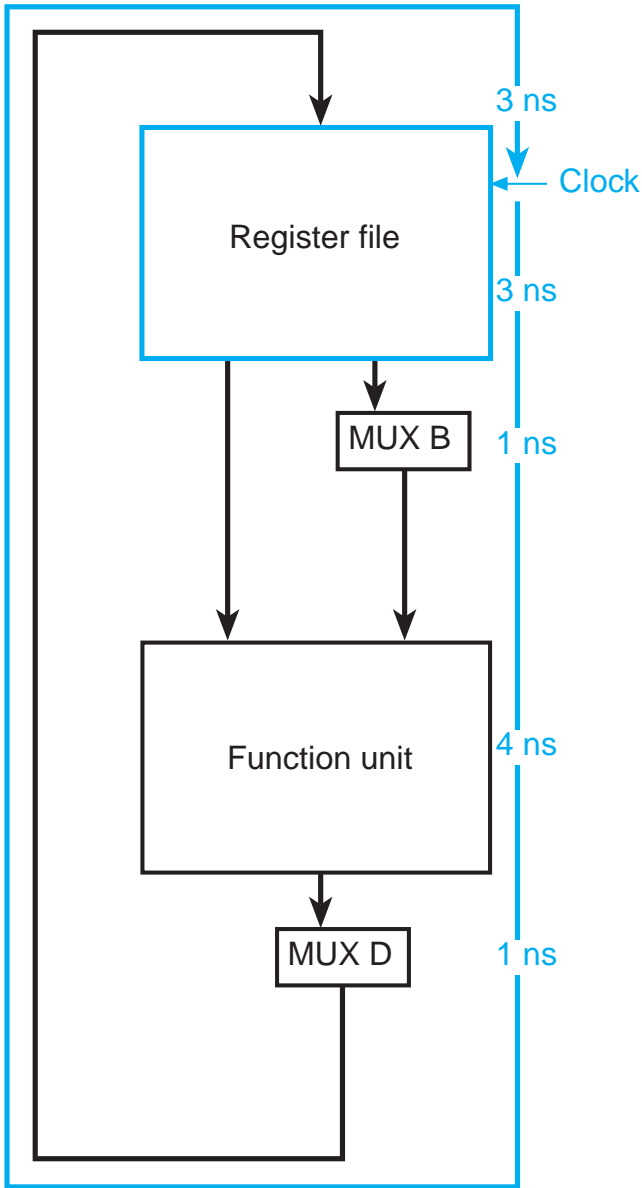


(a) Conventional

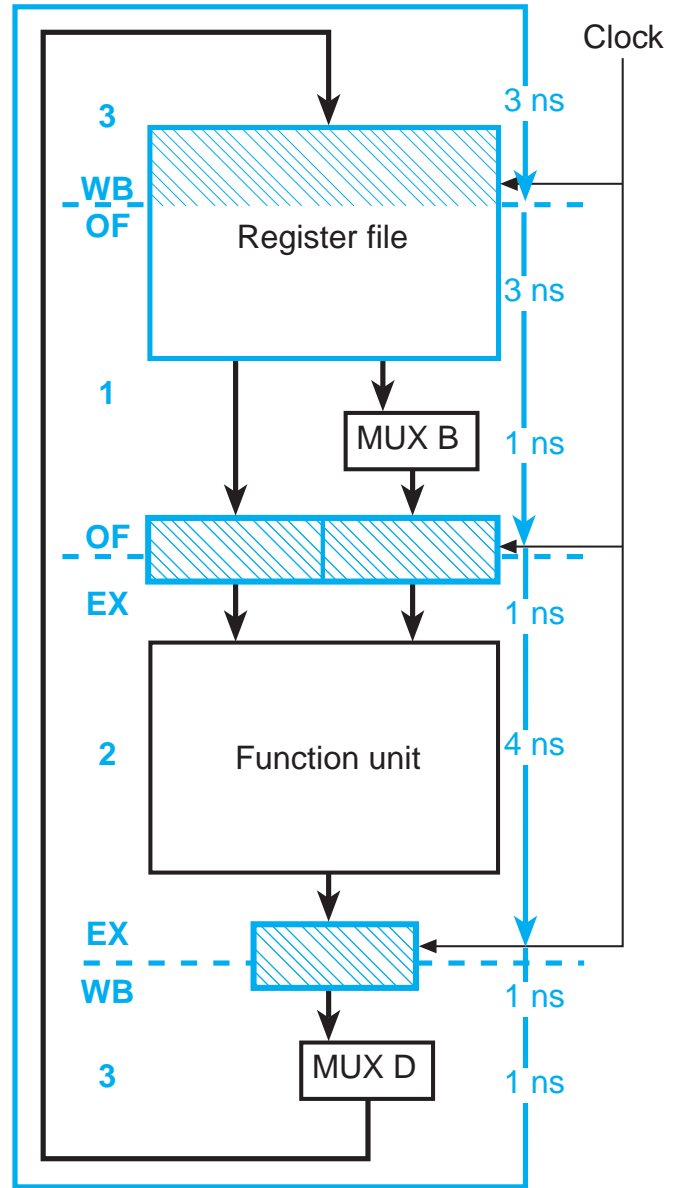


(b) Pipelined
 
# Assembly Line Analogy to Datapath Pipeline





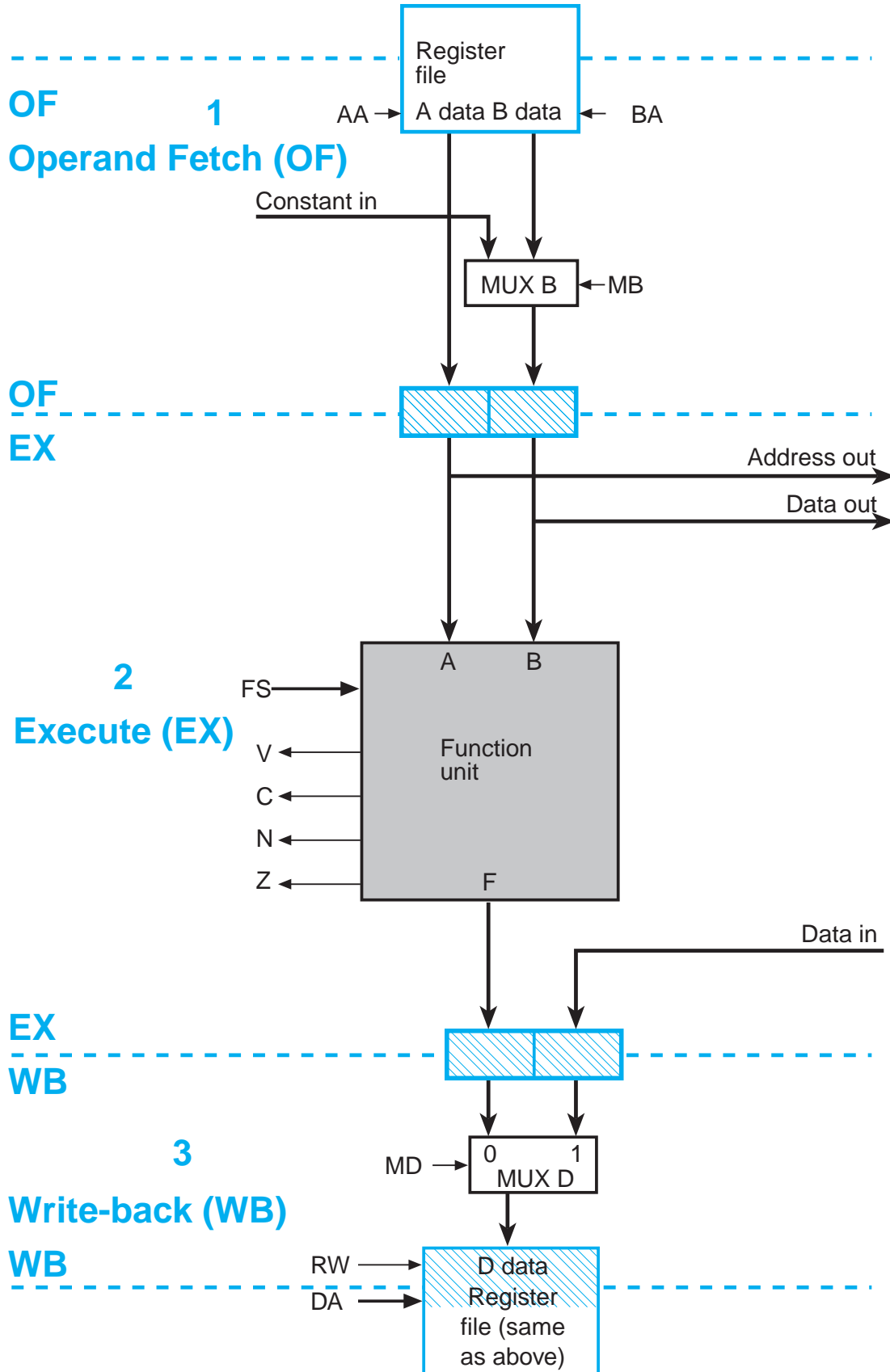

Pipeline Execution Pattern for Microoperation Sequence in Table 7-12

