

---

# High-speed ADC techniques - overview and scaling issues -

Vladimir Stojanovic

---

# Outline

---

- High-Speed ADC applications
- Basic ADC performance metrics
- Architectures – overview
- ADCs in 90s
- Limiting factors
- Conclusion

# High-speed ADC applications

---

- Wireless LAN Data Channel (1-50MS/s, 6-10b)
- Magnetic Storage Read Channel (200-1000MS/s, 6-8b)
- ADSL data channel (3-10MS/s, 12-16b)
- Digital Multi-Standard TV Baseband ADC  
(20MS/s, 8-10b)
- CATV Decoder Modem ADC (10-20MS/s, 8-10b)
- HDTV – various apps (50-75MS/s, 10b)
- Digital-IF for Multi-standard Broadcast TV rcvr  
(100-200Mb/s, 8-12b)
- Serial high-speed links with MPAM modulation  
(5-10Gs/s, 4-6b)

# Basic ADC performance metrics

- **Aperture time uncertainty**

- **Peak SNR**

$$\text{SNR}_p = 6.02N + 1.76 \text{ [dB]}$$

- **Effective # of bits**

$$\text{SNDR} = 6.02\text{ENOB} + 1.76 \text{ [dB]}$$

- **Dynamic range**

$$\text{DR} = P_{\text{full scale sin}} / P_{\text{sin@0dB SNR}}$$

- **Spurious Free Dynamic Range**


- **Static errors:**

**DNL** - differential non-linearity

**INL** - integral non-linearity

Offset

**Gain error**

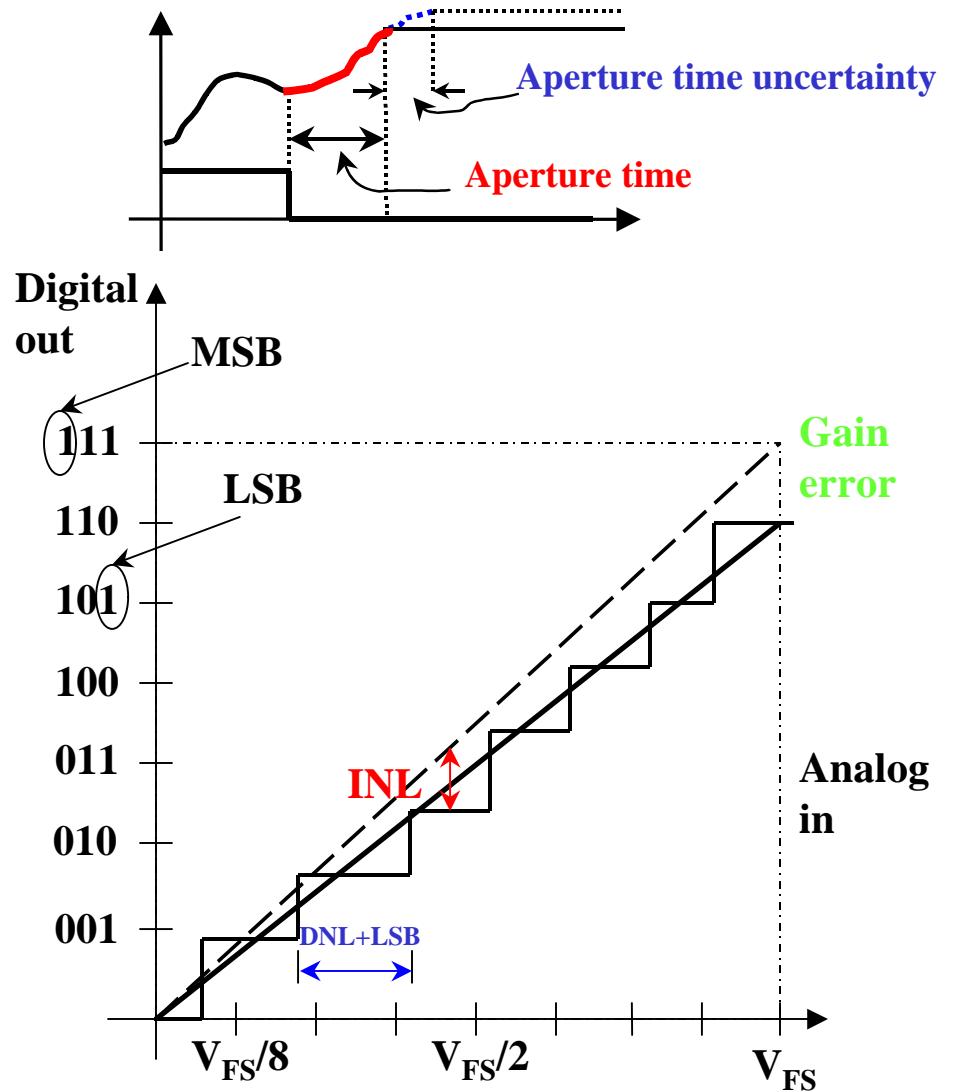

# Architectures

---


- Flash
  - Interpolation
  - Averaging
- Folding
  - Folding and Interpolation
- Two-step
  - Subranging
  - Flash
- Pipeline
  - Per-stage calibration

# Flash ADC

---


Best up to 8 bits:

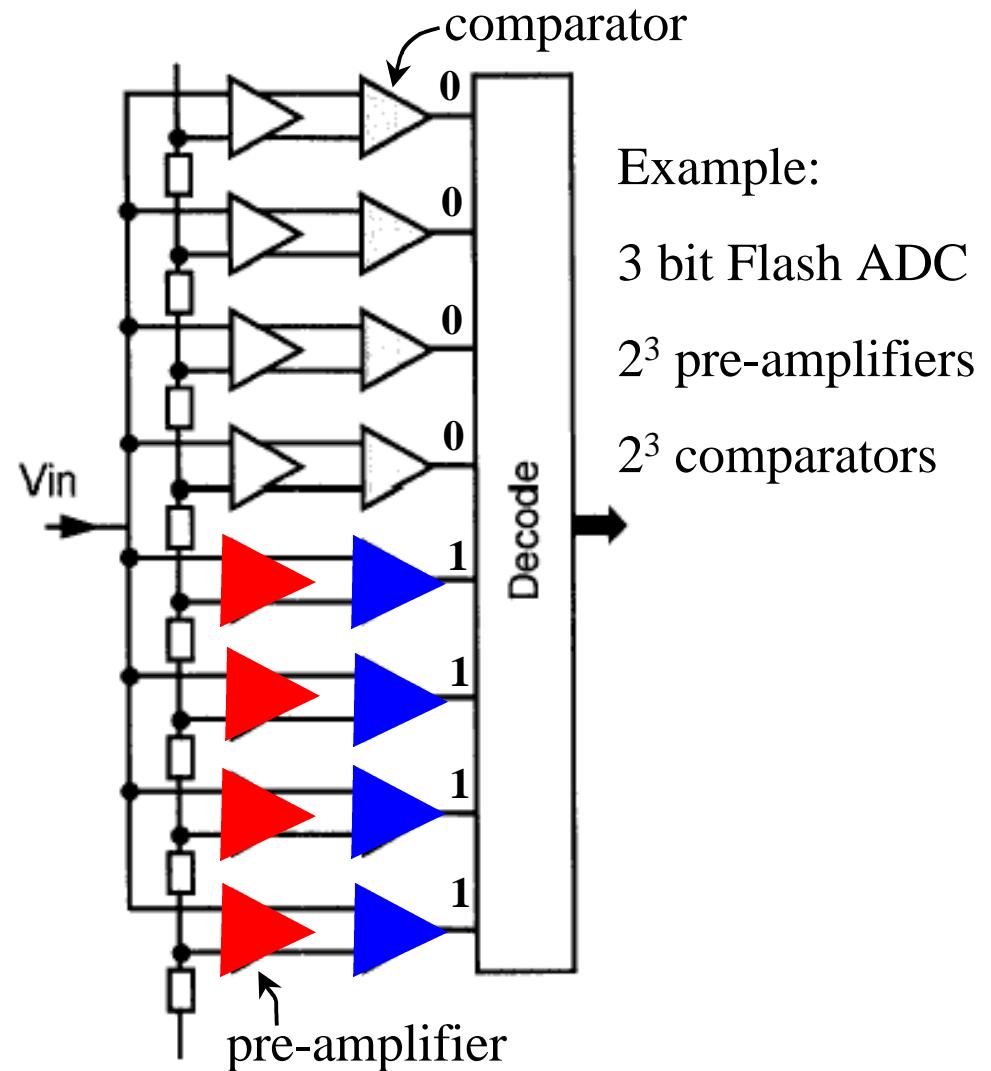- + Speed
- + Simplicity
- Exponential complexity
- Big input capacitance
- Bubbles in thermo code
- Power
- Difference in signal delay to each comparator




# Interpolation in Flash ADC

---

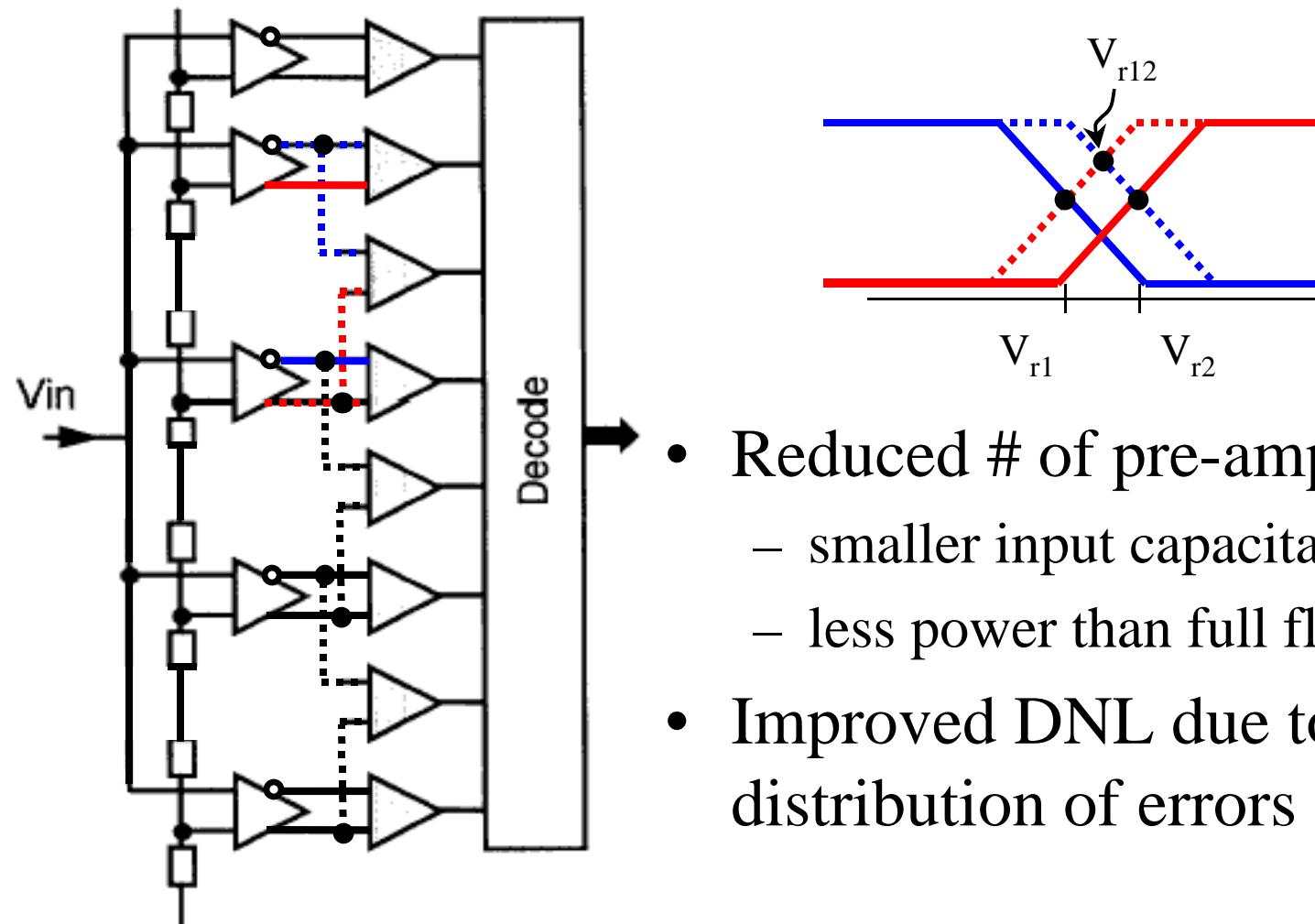

# Averaging in Flash ADC

---

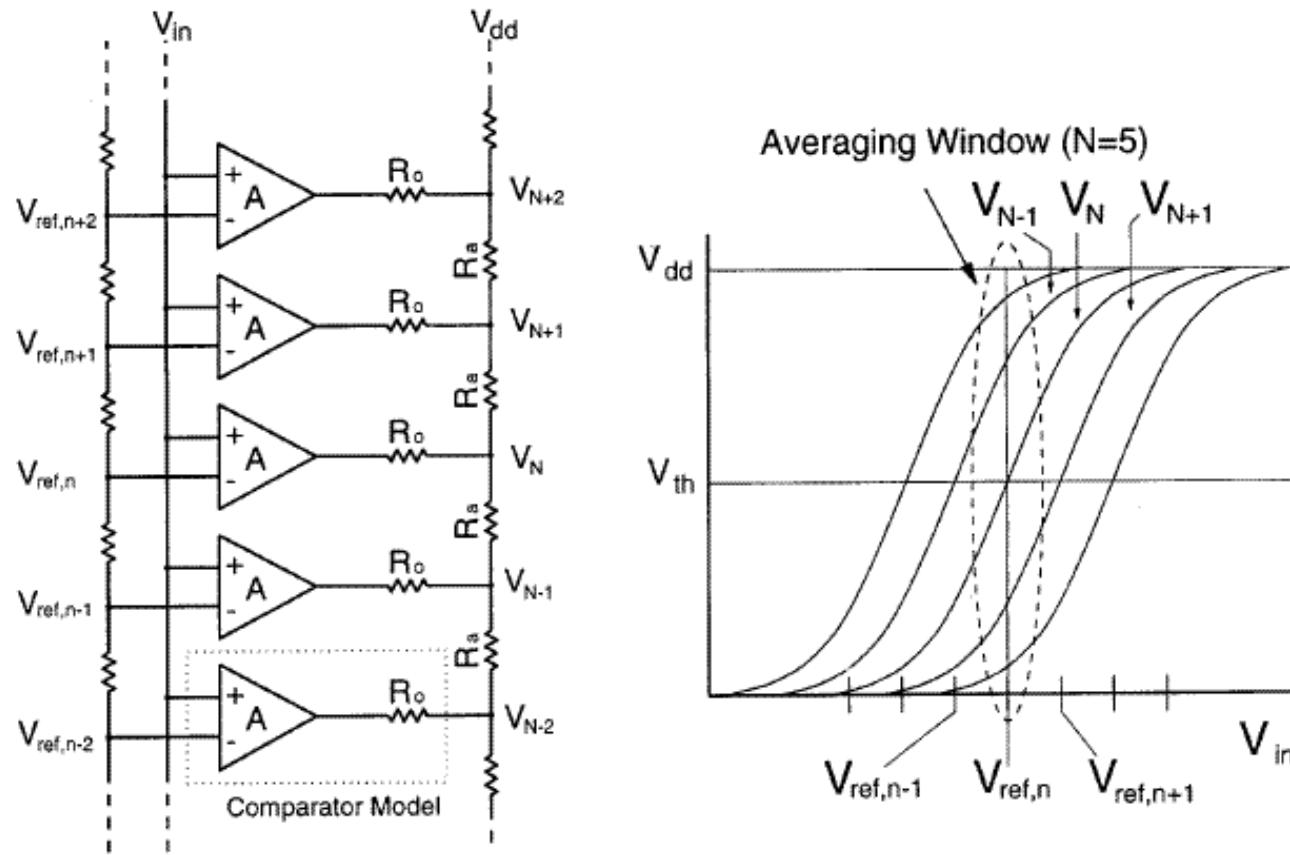


Pre-amps reduce effect of comparator offset ( $\sim 15\text{-}50\text{mV}$ )  
But introduce offsets ( $\sim 3\text{mV}\text{-}10\text{mV}$ )  
Solution – Average out the pre-amplifier offsets with resistor network

---


# Effect of Averaging

---

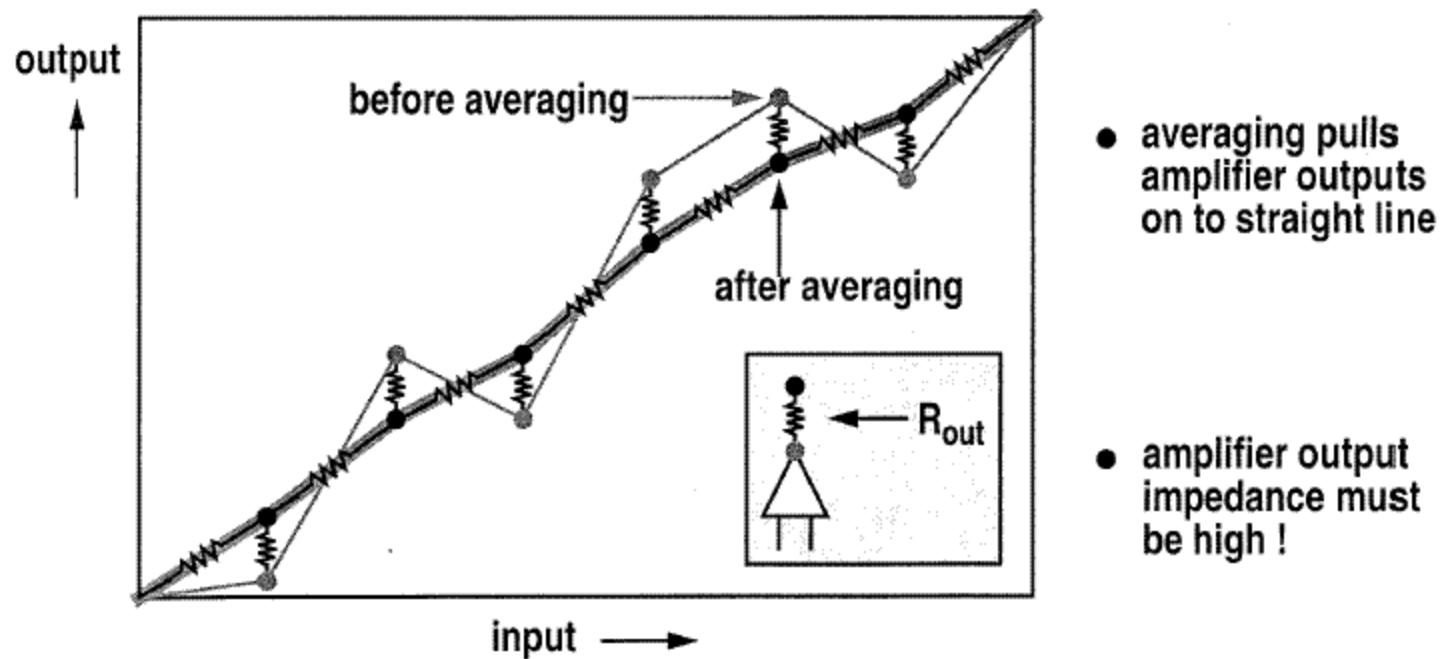

# Averaging effect on offset, INL, DNL

---


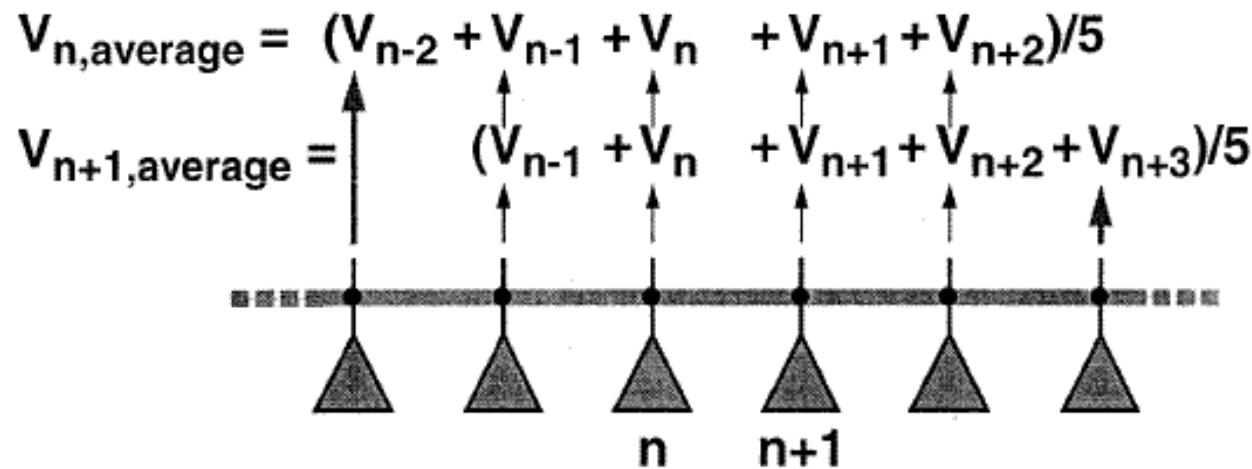


- neighboring signals highly correlated after averaging
- $\Delta = (V_{n-2} - V_{n+3})/5$  and  $s_{\text{average}} = \frac{s_{\text{individual}}}{\sqrt{5}}$
- 
- DNL improves with # of averaging stages
- INL, offset improve with square-root of averaging stages

# Folding and Two-step ADCs

---

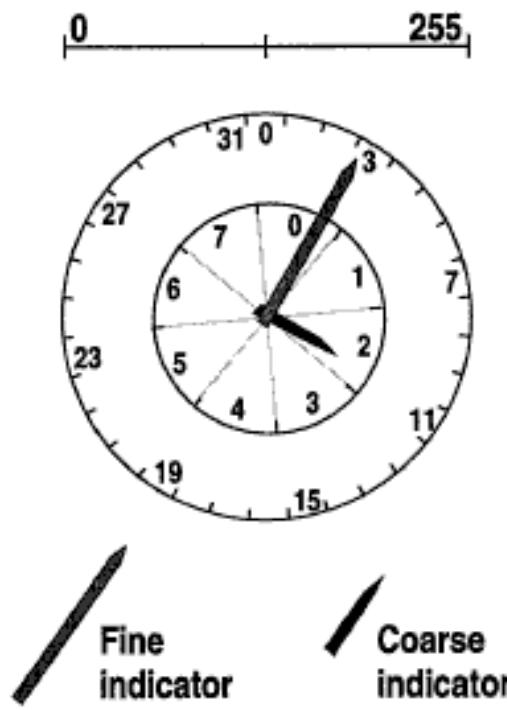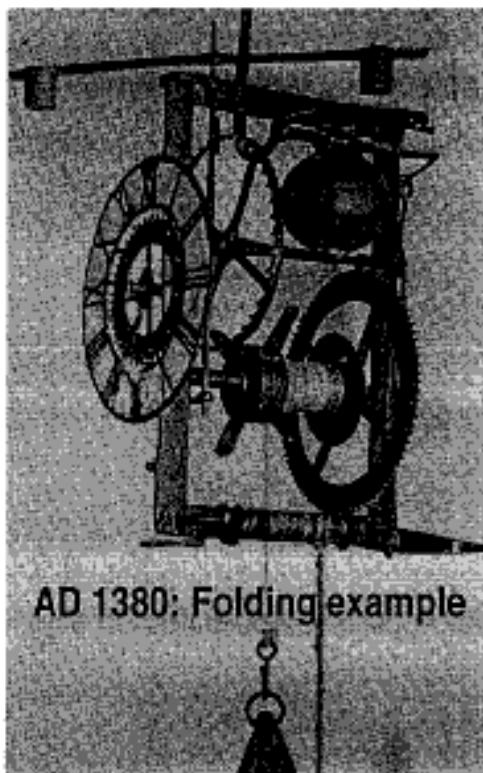**Folding: Continuous Two Step A/D Converter**




Two architectures, same idea:

- Folding
- Two-step

- Coarse ADC gets MSBs and residue

- Fine ADCs get LSBs from residue


# Folding ADC

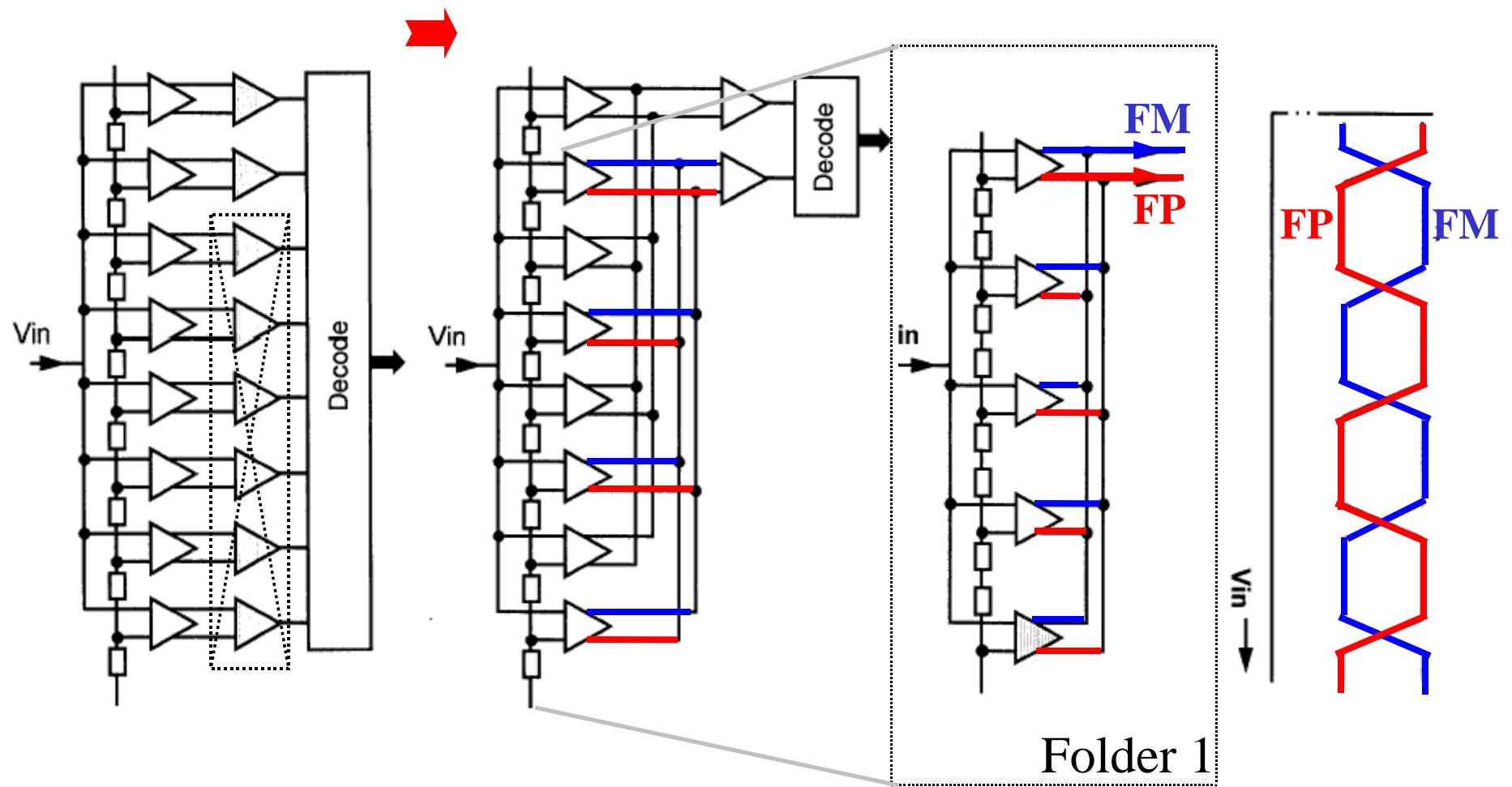

Example: 3bit, 4x Folding ADC

# Folding ADC: Block Diagram



---

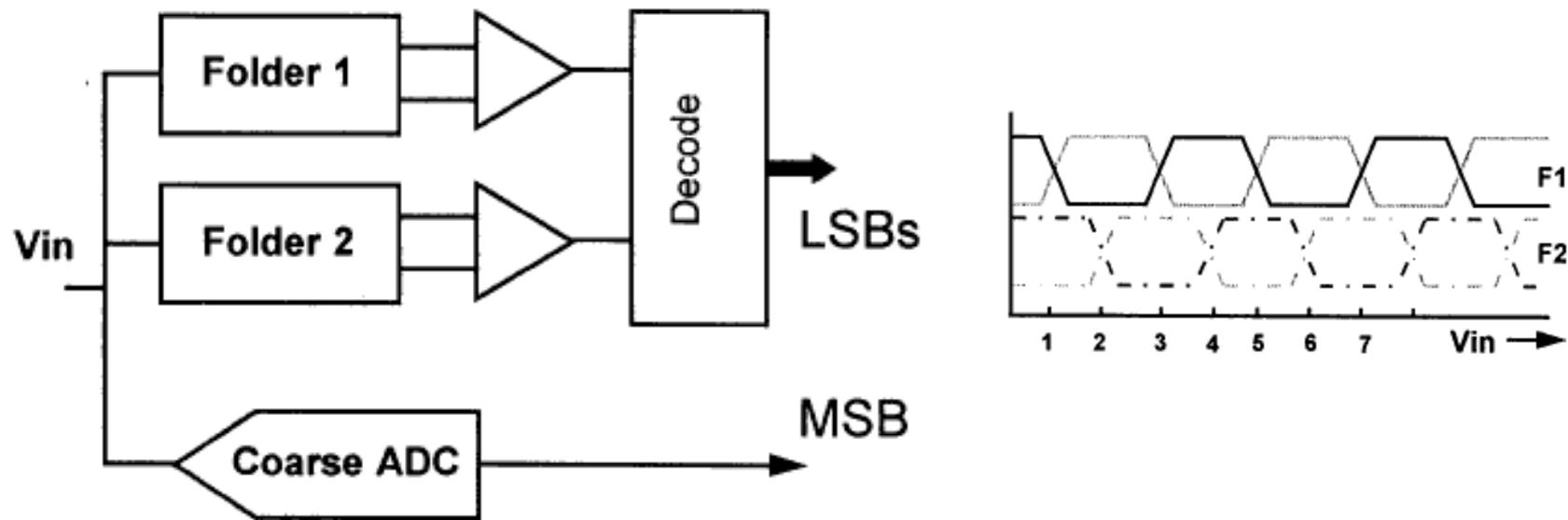

- Folding tradeoff
    - + Fewer comparators
    - Faster signals
  - Fold x 4
    - + From 8 to 2 comparators
    - max.  $F_{out} > 4 F_{in}$
  - Critical issue is to match timing of coarse ADC and fine (folded) ADCs
  - Non-linearity around the folding point significantly reduces performance if amplitude is quantized
-

# Folding & Interpolating ADC

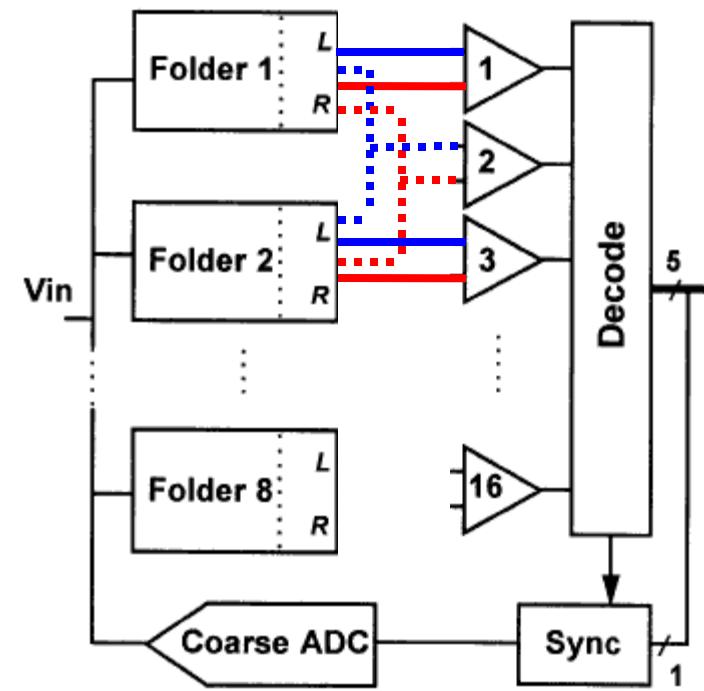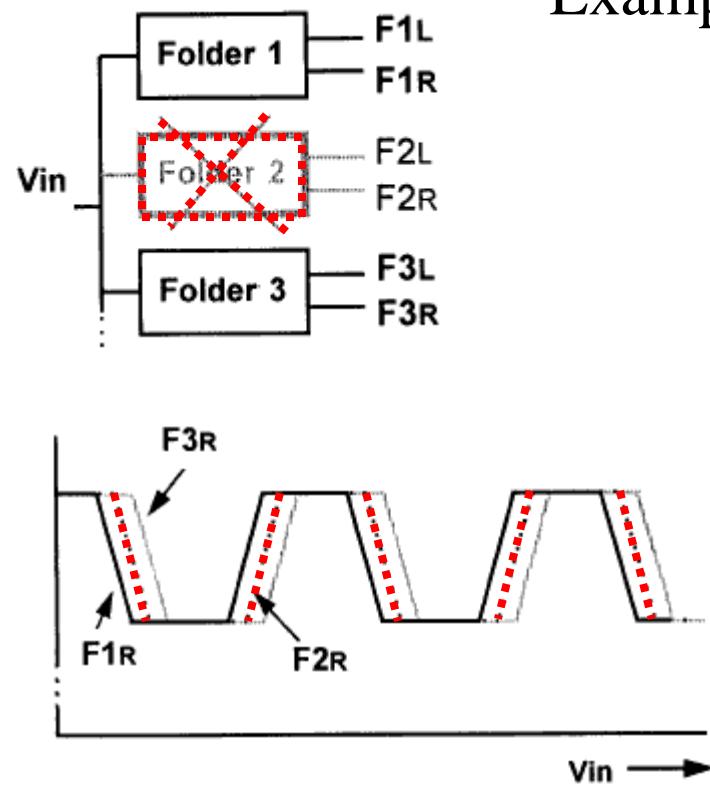Example: 6bit, 4x fold, 2x interpolate ADC



With interpolation – only detect zero crossing points

# Two-step: subranging ADC


---

- +  $2(2^{N/2}-1)$  comparators

Coarse bank selects which part  
of reference ladder to connect to  
fine bank


- Speed limited by settling  
of fine references

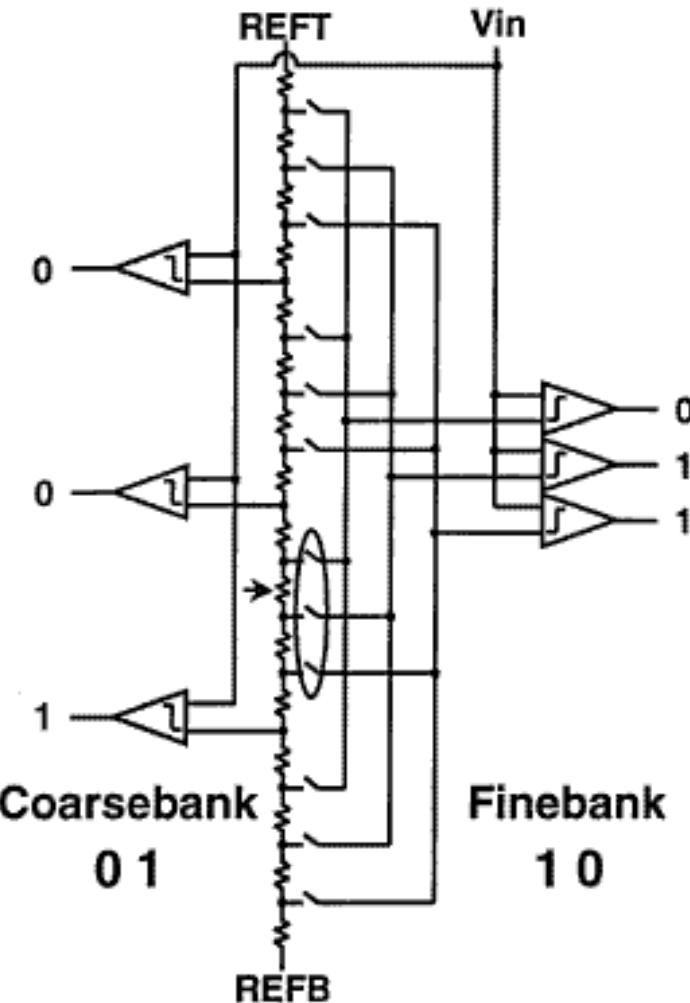parasitic capacitance from  $> 2^N$   
switches + large kickback



# Two-step: Flash ADC


---

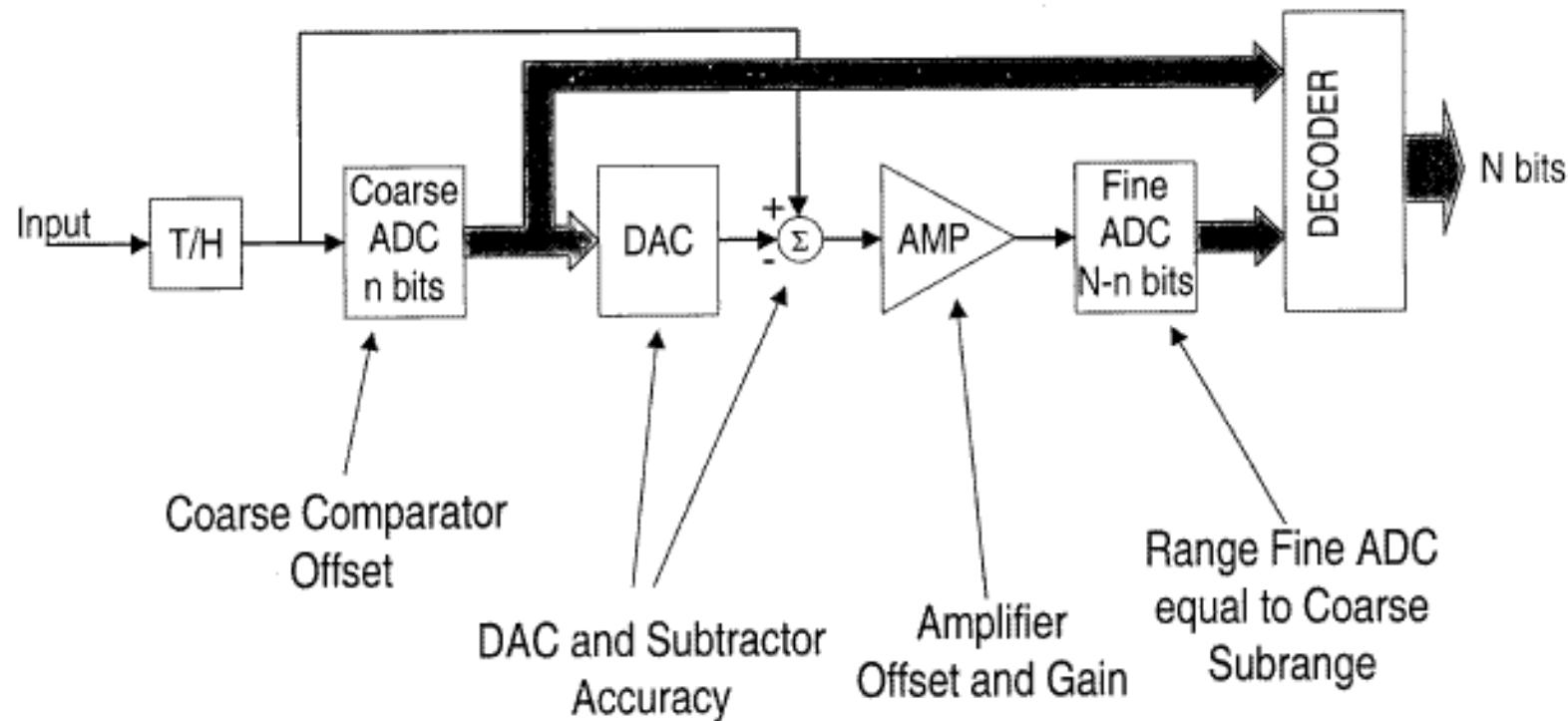

- Two-step ADC accuracy challenges

# Pipelined ADC


---

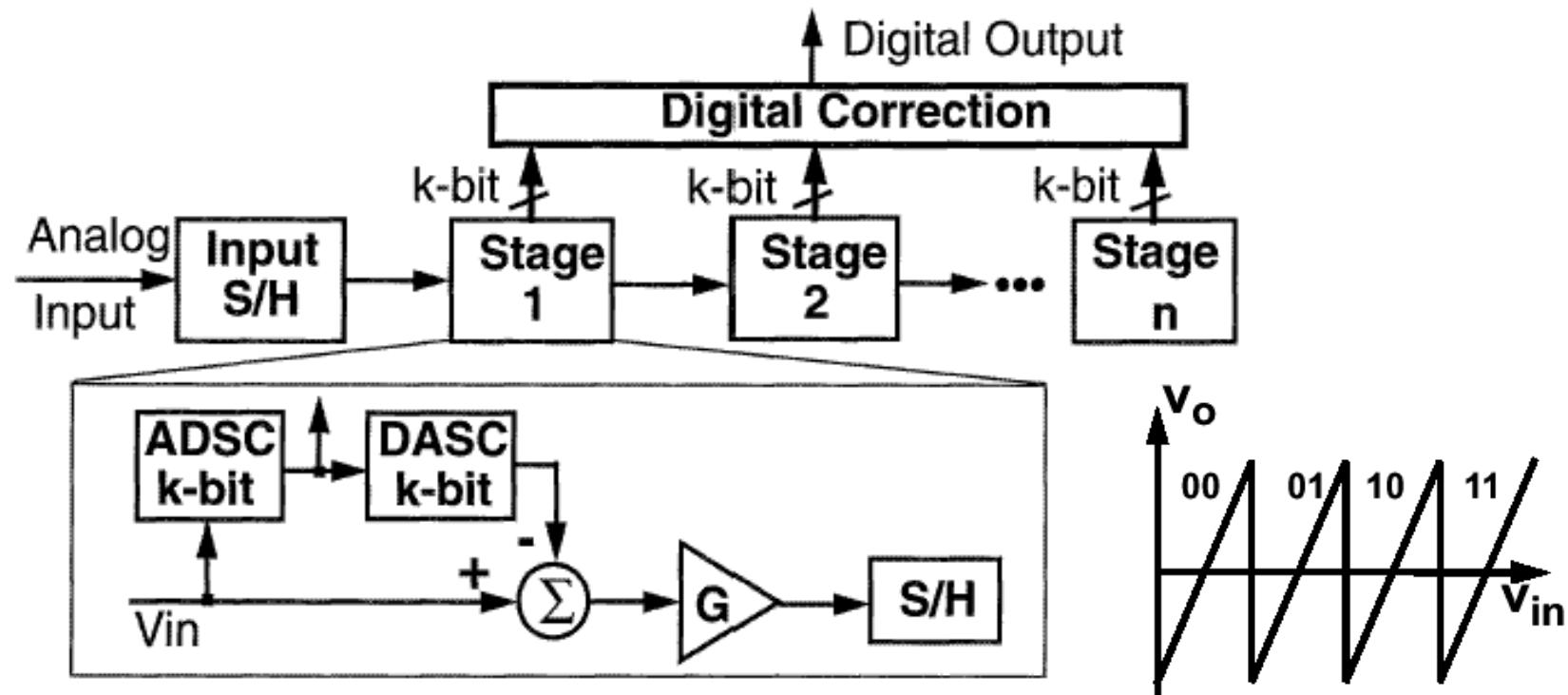

- All stages process different data simultaneously
  - throughput only depends on speed of each stage
  - complexity traded for latency

# Effect of stage ADC non-linearity errors

2-bit example:

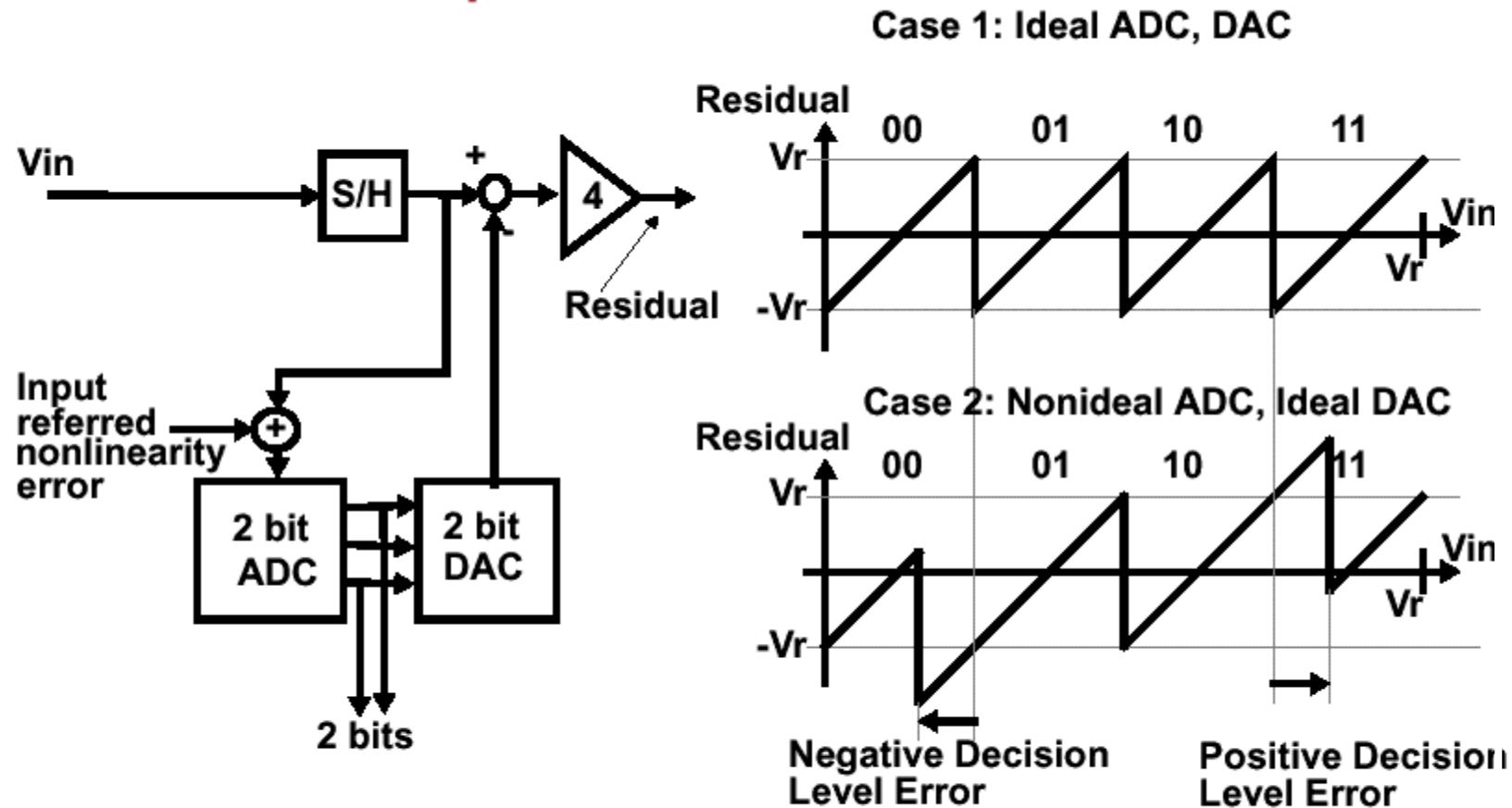


**Key Point: Can remove ADC Errors by Increasing ADC range in next stg**

# Removing stage ADC non-linearity errors

---

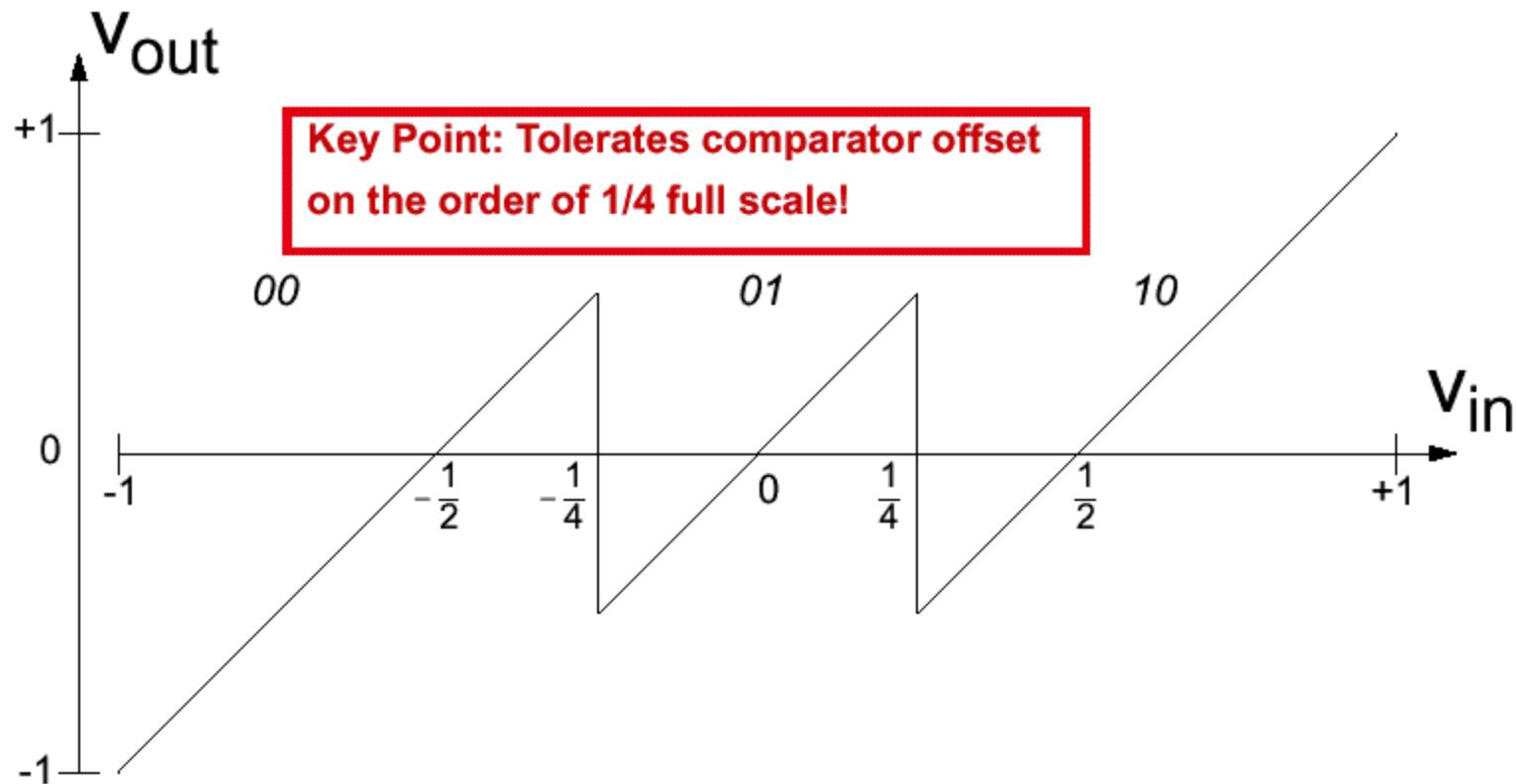
**Important Case: 1.5 bit/Stage with Digital Correction**



**Final Result: DAC Linearity and amplifier gain errors ultimately limit linearity**

# Interstage gain error propagation


---

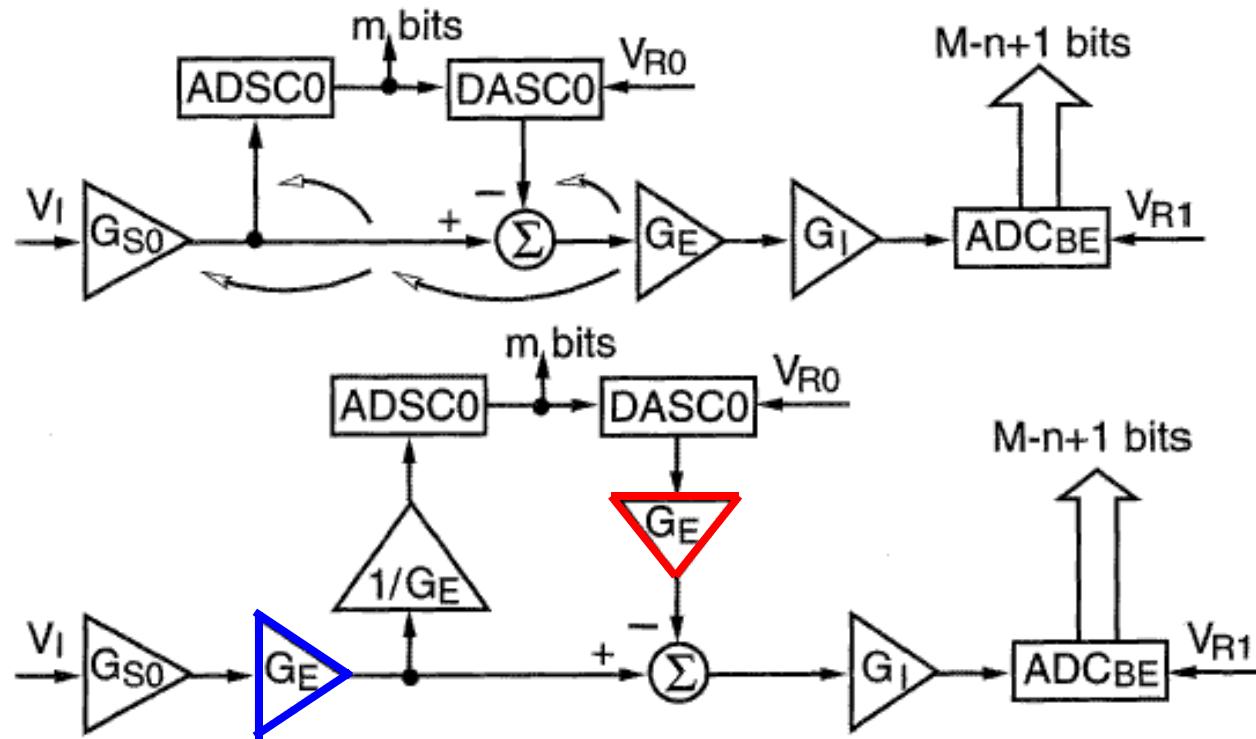

$G_E$  models interstage gain error  
Only need to correct for the red block in each stage !


---

# Interstage gain error calibration

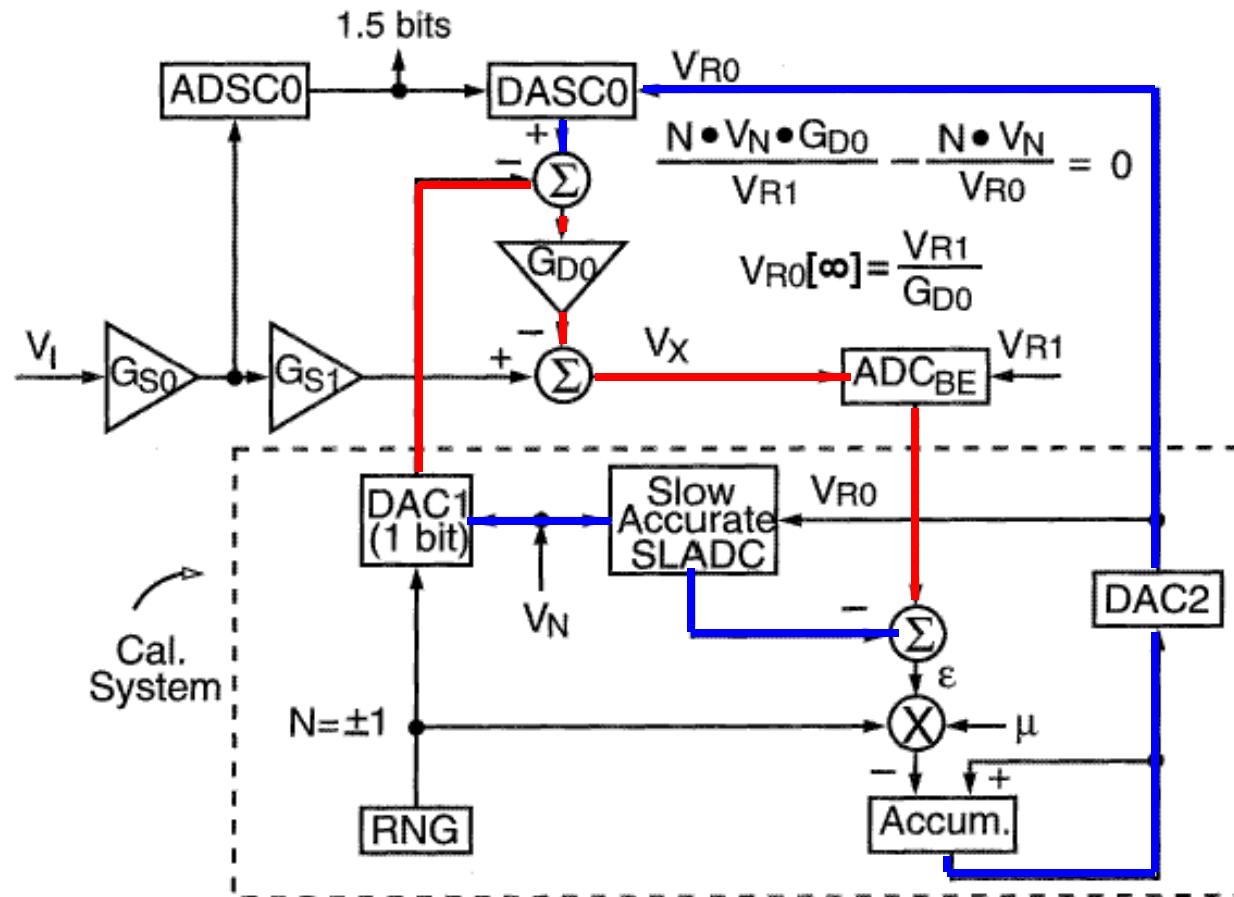

# Time-Interleaved, pipelined ADCs

---

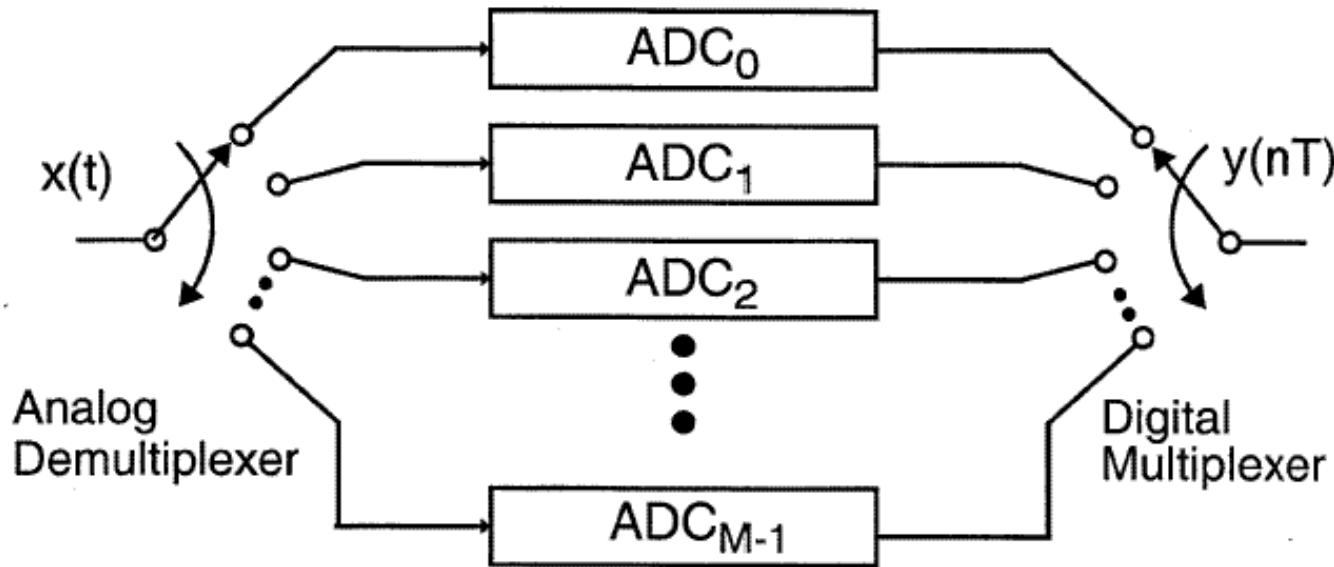

- Clock each ADC at  $F_s/M$
- Increase throughput and area  $M$  times


Gain mismatch  $\Rightarrow$  Amplitude Modulation

Offset mismatch  $\Rightarrow$  Additive Tones

Timing mismatch  $\Rightarrow$  Phase modulation

# Gain and offset calibration


---

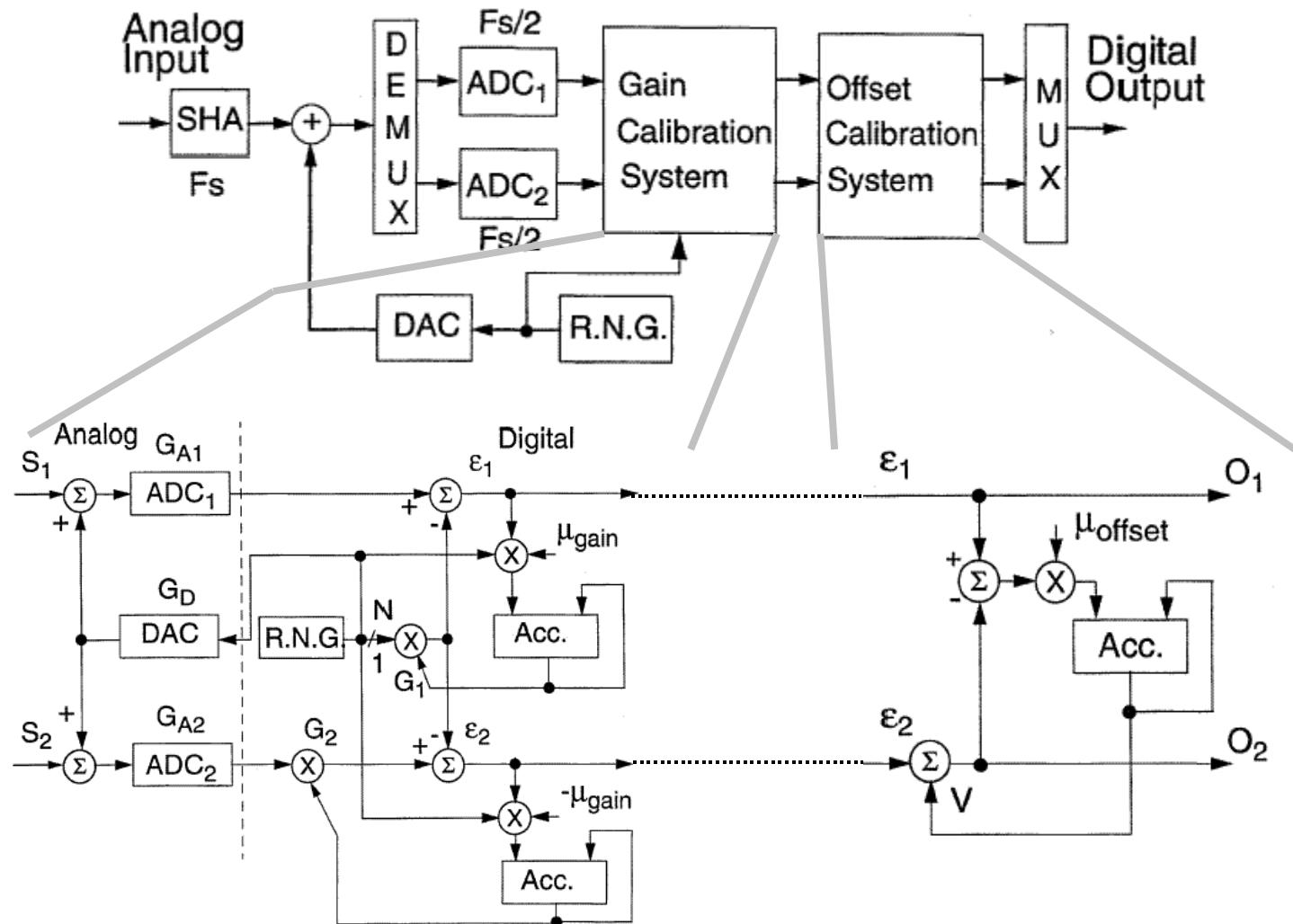

# Calibration results


---

Measured Results - Before Calibration

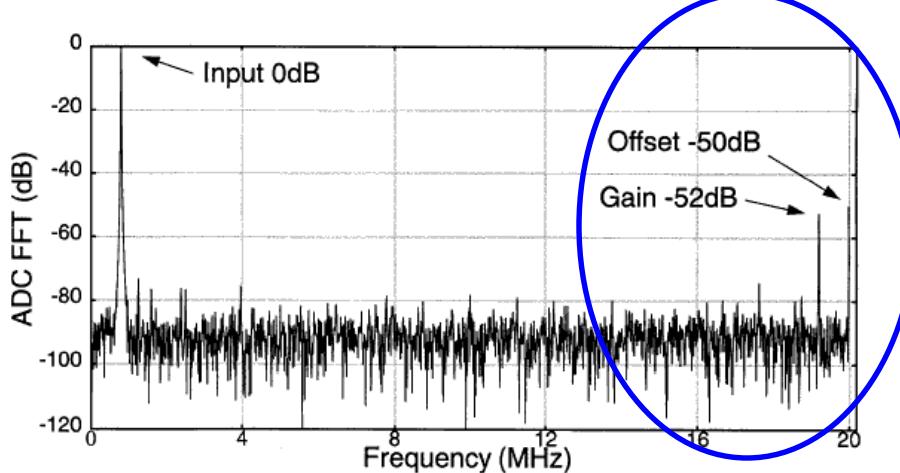

SNDR limited by  
mismatches

Measured Results - Calibration Activated

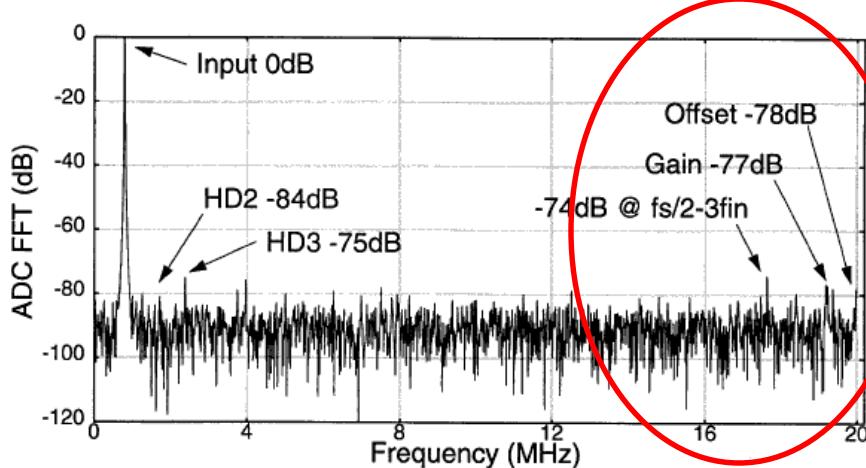

SNDR limited by  
non-linear  
mismatches

# ADCs in '90s

---

- Analyzed a bunch of ADCs
  - different technologies
  - different specs
- Use metrics from digital domain to see how ADCs scale with mainstream digital CMOS
- Two main metrics:
  - Delay of fan-out of 4 inverter (FO4)
  - Energy dissipated driving the gate of minimum size inverter (MSI)

# Metrics ...

---

- Unit Delay

$$FO4 = \frac{500\text{ps}}{\text{mm}} L_{ch}[\text{mm}]$$

- Unit Energy

$$Cg_{MSI} = (4+8)I \frac{2fF}{\text{mm}} = \frac{12fF}{\text{mm}} L_{ch}[\text{mm}]$$

$$MSI = \frac{6fF}{\text{mm}} L_{ch}[\text{mm}] \times Vdd^2$$

- Approach:

- Normalize sampling period to FO4
- Energy/sample=Power/Rate
- Normalize Energy/sample by MSI
- ED=normalized Energy \* normalized Sampling period
- Figure of merit FM~ Resolution\*ln2 – ln(ED)

# ADCs in '90s: Raw data

---

Author	Conf/Jour.	Resolution	Speed [MS]	Tech. [um]	P [mW]	Vdd [V]	A [mm <sup>2</sup> ]	INL [LSB]	DNL [LSB]	ENOB	SNDR	SFDR	Cin [fF]	Style
M. Choi	ISSCC 01	6	1300	0.35	250	3.3	0.8	0.35	0.2	5	32	44	1	Full-Flash with preamp & two stage averaging
G. Geelen	ISSCC 01	6	1100	0.35	300	3.3	0.35	0.6	0.7	4.5	29	40		Flash, 3 avg, 2 interpolate, distrib T/H
K. Nagaraj	JSSC 00	6	700	0.25	190	3.3	0.45	0.4	0.4	4.7	30	40		Flash, interleaved S/H, interpolation
Y. Tamba	ISSCC 99	6	500	0.4	400	3.3	2.4	0.55	0.65	5.4	34	45		Flash, offset comp. per comp, distrib T/H
K. Yoon	ISSCC 99	6	500	0.6	330	3.3	4	0.5	0.4	3.6	23	34		Flash, interpol., auto-zero (bg), intern T/H
B. Song	VLSI 99	6	50	0.35	20	1	4.8	0.7	0.6	4.2	27			Flash, Current Interpolation, low-supply
K. Nagaraj	JSSC 99	6	75	0.5	110	3.3	1	1	1	5.2	33			Flash with 1-bit folding
M. Flynn	ISSCC 98	6	400	0.5	200	3.2	0.6	0.5	0.5	4	26		1.2	Flash, Folding, interpolating current mode
I. Tsukamoto	ISSCC 98	6	400	0.35	190	3	1.2	0.25	0.2					Full-Flash with interleav. auto-zero error cor
J. Spalding	ISSCC 96	6	200	0.6	400	5	2.7	0.5	0.5	5	32	35		Full-Flash, auto-zero comparators
R. Roovers	JSSC 96	6	175	0.7	160	3.3	12	1	0.8	4	26		4	Current Interpolation
I. Tsukamoto	JSSC 96	6	200	0.5	110	3	1.6	0.5	0.3	4	26	32		Full-Flash, interl auto-zero, chopper comp
J. Ming	ISSCC 00	8	80	0.5	250	3	10.3	0.5	0.3	7.3	46	59		pipelined, inter-stage bg calibration
K. Yoon	VLSI 00	8	125	0.35	110	3.3	0.8	1.5	0.7	6.4	40			Flash, fold. & interpol, w. equalizing preamp
Y-T. Wang	JSSC 00	8	150	0.6	400	3.3	1.8	1.24	0.6	6.4	40		1.5	Sliding window pipe. interpolation, dual ch.
M-J. Choe	VLSI 00	8	100	0.5	165	5	1.7	1.3	0.4	6.1	38			pipelined folding
W. Bright	ISSCC 98	8	75	0.5	70	3.3	5.5	0.5	0.5	6.85	43			parallel, pipelined, dual sampling, 1.5b/stage
K. Nagaraj	JSSC 97	8	52	0.9	250	5	15	1	0.2	7.2	45	55		parallel, pipelined, dual sampling, 1.5b/stage
A. Venes	ISSCC 96	8	80	0.5	80	3.3	0.3	0.8	0.45	6.6	42		2	folding&interp, distrib T/H
M. Flynn	ISSCC 95	8	100	1	250	3.3	4			7.2	45		5	folding&interp, current mode interpolation
B. Nauta	ISSCC 95	8	70	0.8	110	5	0.8	0.5	0.2				4.8	folding&interpolating
M. Pelgrom	JSSC 94	8	25	1	250	5	2.8	0.5	0.5	6.4	40			Full-Flash optimized for random offset
C. Conroy	JSSC 93	8	85	1	1100	5	25	1	0.8	6.5	41	46	2	4-way interleaved, pipelined 1.5b/stage
Y. Park	ISSCC 01	10	100	0.18	80	1.8	2.5	0.76	0.66	9	56	64		pipelined, 1.5b/stage, no calibration
B. Brandt	ISSCC 99	10	20	0.5	75	3.3	1.6	0.5	0.4	9.5	59			Two-step, subranging, interpolated comps
I. v.d.Ploeg	ISSCC 99	10	25	0.35	195	3.3	0.66	0.9	0.7	8.2	54	60		Two-step, offs comp res. amp, ladder sharing
K. Dyer	ISSCC 98	10	40	1	650	5	47	0.48	0.3	9	56	74		3-way interl, pipelined, mix signal bg calib
D. Fu	ISSCC 98	10	40	1	565	5	42	0.3	0.14	7.7	48	72		2-way interl, pipelined, digital bg calib LMS
A. Abo	VLSI 98	10	14	0.6	36	1.5	5.8	0.7	0.5	8.2	54			pipelined, 1.5b/stage, no calib, low power
K. Bult	ISSCC 97	10	50	0.5	240	5	2	1.1	0.6	8	50	52		Flash, improved averaging, folding


# ADCs in '90s: Scaled data

---

Labels	Author	Resolution	Ts [FO4]	Tech. [um]	Vdd [V]	A [M ]	ED/s	E/s[k MSI]	Emsi [fJ]	E/s [fJ]	FM	Style
[6_1]	M. Choi	6	4	0.35	3.3	26	37	8	23	192308	15	Full-Flash with preamp & two stage averaging
[6_2]	G. Geelen	6	5	0.35	3.3	11	62	12	23	272727	14	Flash, 3 avg, 2 interpolate, distrib T/H
[6_3]	K. Nagaraj	6	11	0.25	3.3	29	190	17	16	271429	12	Flash, interleaved S/H, interpolation
[6_4]	Y. Tamba	6	10	0.4	3.3	60	306	31	26	800000	11	Flash, offset comp. per comp, distrib T/H
[6_5]	K. Yoon	6	7	0.6	3.3	44	112	17	39	660000	13	Flash, interpol., auto-zero (bg), intern T/H
[6_6]	B. Song	6	114	0.35	1	157	21769	190	2	400000	2	Flash, Current Interpolation, low-supply
[6_7]	K. Nagaraj	6	53	0.5	3.3	16	2394	45	33	1466667	7	Flash with 1-bit folding
[6_8]	M. Flynn	6	10	0.5	3.2	10	163	16	31	500000	12	Flash, Folding, interpolating current mode
[6_9]	.Tsukamoto	6	14	0.35	3	39	359	25	19	475000	10	Full-Flash with interleav. auto-zero error cor
[6_10]	J. Spalding	6	17	0.6	5	30	370	22	90	2000000	10	Full-Flash, auto-zero comparators
[6_11]	R. Roovers	6	16	0.7	3.3	98	326	20	46	914286	11	Current Interpolation
[6_12]	.Tsukamoto	6	20	0.5	3	26	407	20	27	550000	10	Full-Flash, interl auto-zero, chopper comp
						x100						
[8_1]	J. Ming	8	50	0.5	3	165	58	116	27	3125000	8	pipelined, inter-stage bg calibration
[8_2]	K. Yoon	8	46	0.35	3.3	26	18	38	23	880000	10	Flash, fold. & interpol, w. equalizing preamp
[8_3]	Y-T. Wang	8	22	0.6	3.3	20	15	68	39	2666667	10	Sliding window pipe. interpolation, dual ch.
[8_4]	M-J. Choe	8	40	0.5	5	27	9	22	75	1650000	11	pipelined folding
[8_5]	W. Bright	8	53	0.5	3.3	88	15	29	33	933333	10	parallel, pipelined, dual sampling, 1.5b/stage
[8_6]	K. Nagaraj	8	43	0.9	5	74	15	36	135	4807692	10	parallel, pipelined, dual sampling, 1.5b/stage
[8_7]	A. Venes	8	50	0.501	3.3	5	15	31	33	1000000	10	folding&interp, distrib T/H
[8_8]	M.Flynn	8	20	1	3.3	16	8	38	65	2500000	12	folding&interp, current mode interpolation
[8_9]	B. Nauta	8	36	0.8	5	5	5	13	120	1571429	13	folding&interpolating
[8_10]	M.Pelgrom	8	80	1	5	11	53	67	150	10000000	8	Full-Flash optimized for random offset
[8_11]	C. Conroy	8	24	1	5	100	20	86	150	12941176	10	4-way interleaved, pipelined 1.5b/stage
						x1000						
[10_1]	Y. Park	10	111	0.18	1.8	309	25	229	3	800000	7	pipelined, 1.5b/stage, no calibration
[10_2]	B. Brandt	10	200	0.5	3.3	26	23	115	33	3750000	8	Two-step, subranging, interpolated comps
[10_3]	H. v.d.Ploeg	10	229	0.35	3.3	22	78	341	23	7800000	5	Two-step, offs comp res. amp, ladder sharing
[10_4]	K. Dyer	10	50	1	5	188	5	108	150	16250000	11	3-way interl, pipelined, mix signal bg calib
[10_5]	D. Fu	10	50	1	5	168	5	94	150	14125000	11	2-way interl, pipelined, digital bg calib LMS
[10_6]	A. Abo	10	238	0.6	1.5	64	76	317	8	2571429	5	pipelined, 1.5b/stage, no calib, low supply
[10_7]	K. Bult	10	80	0.5	5	32	5	64	75	4800000	11	Flash, improved averaging, folding


# Sampling period vs. technology - 6bit

---

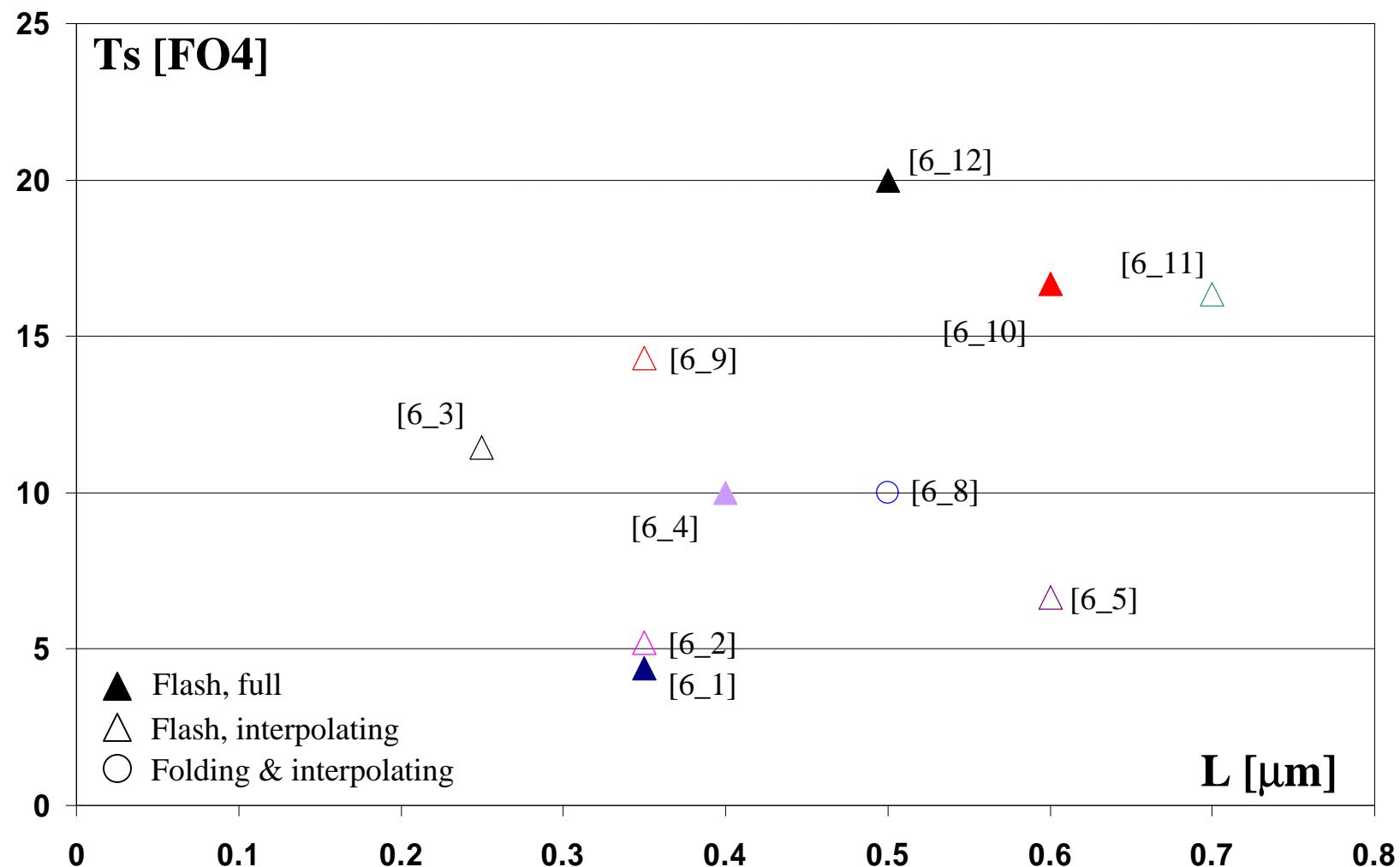


# Sampling period vs. technology - 8bit

---

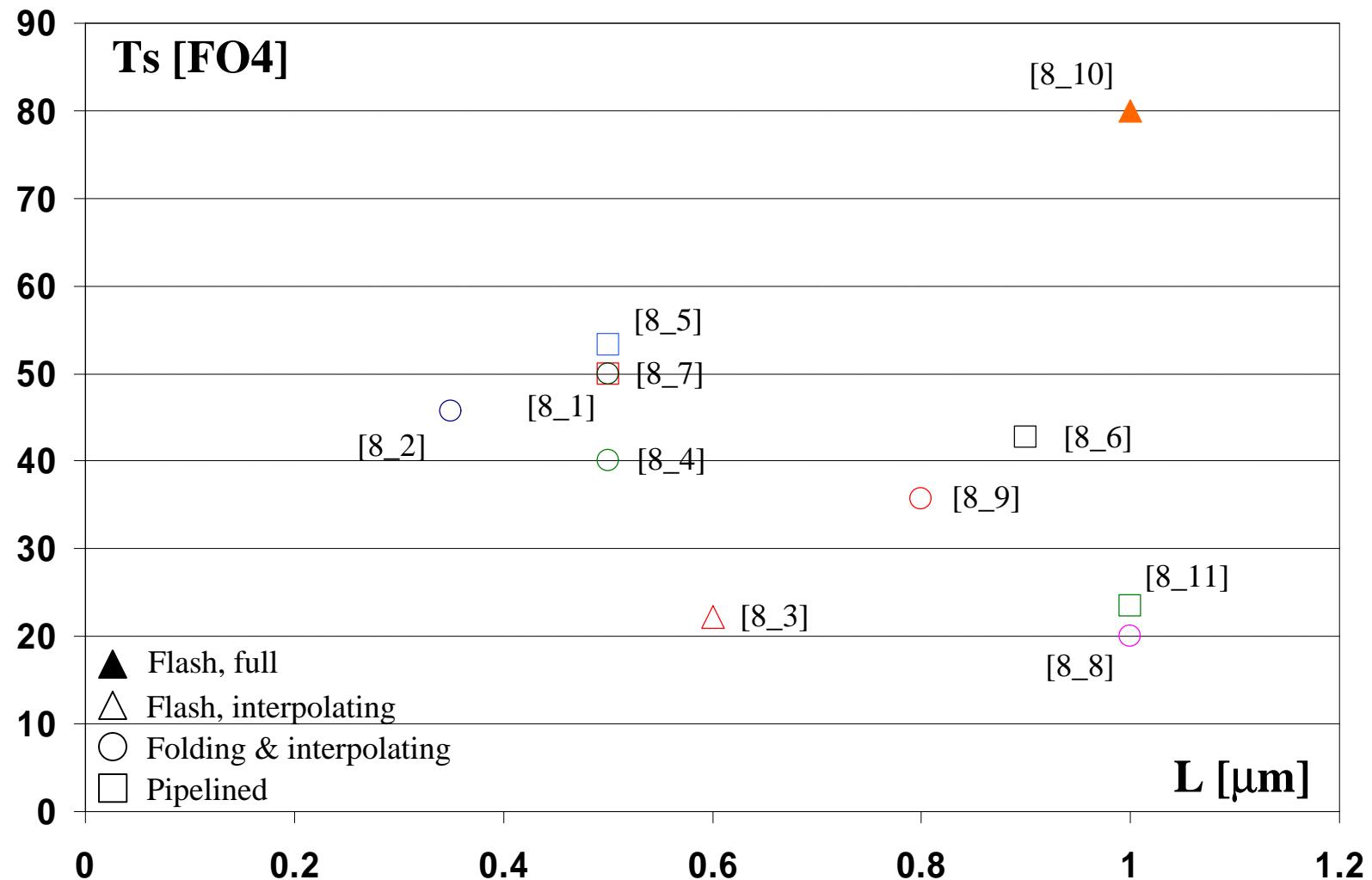


# Sampling period vs. technology - 10bit

---

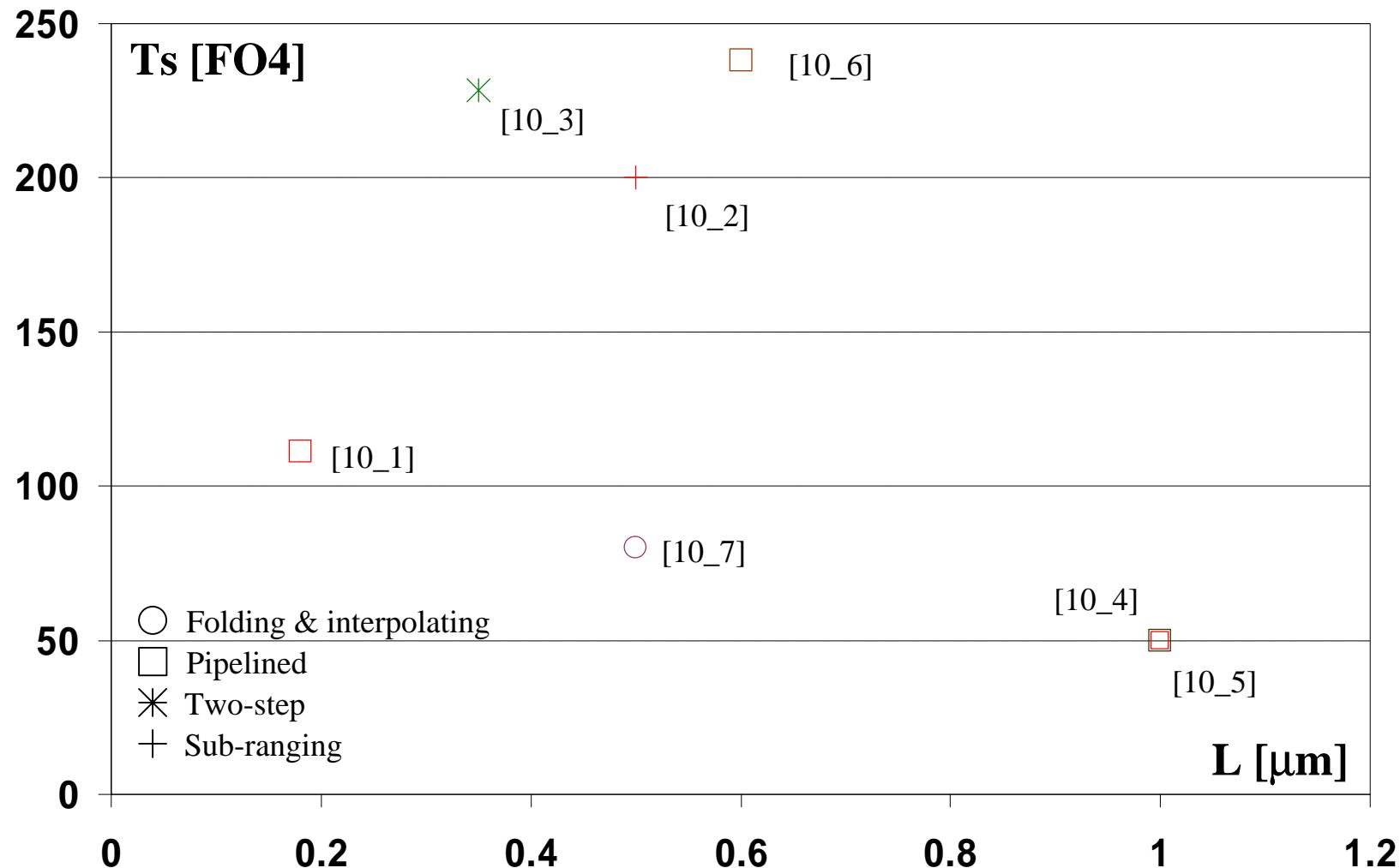


# Energy\*''Delay'' vs. technology - 6bit

---

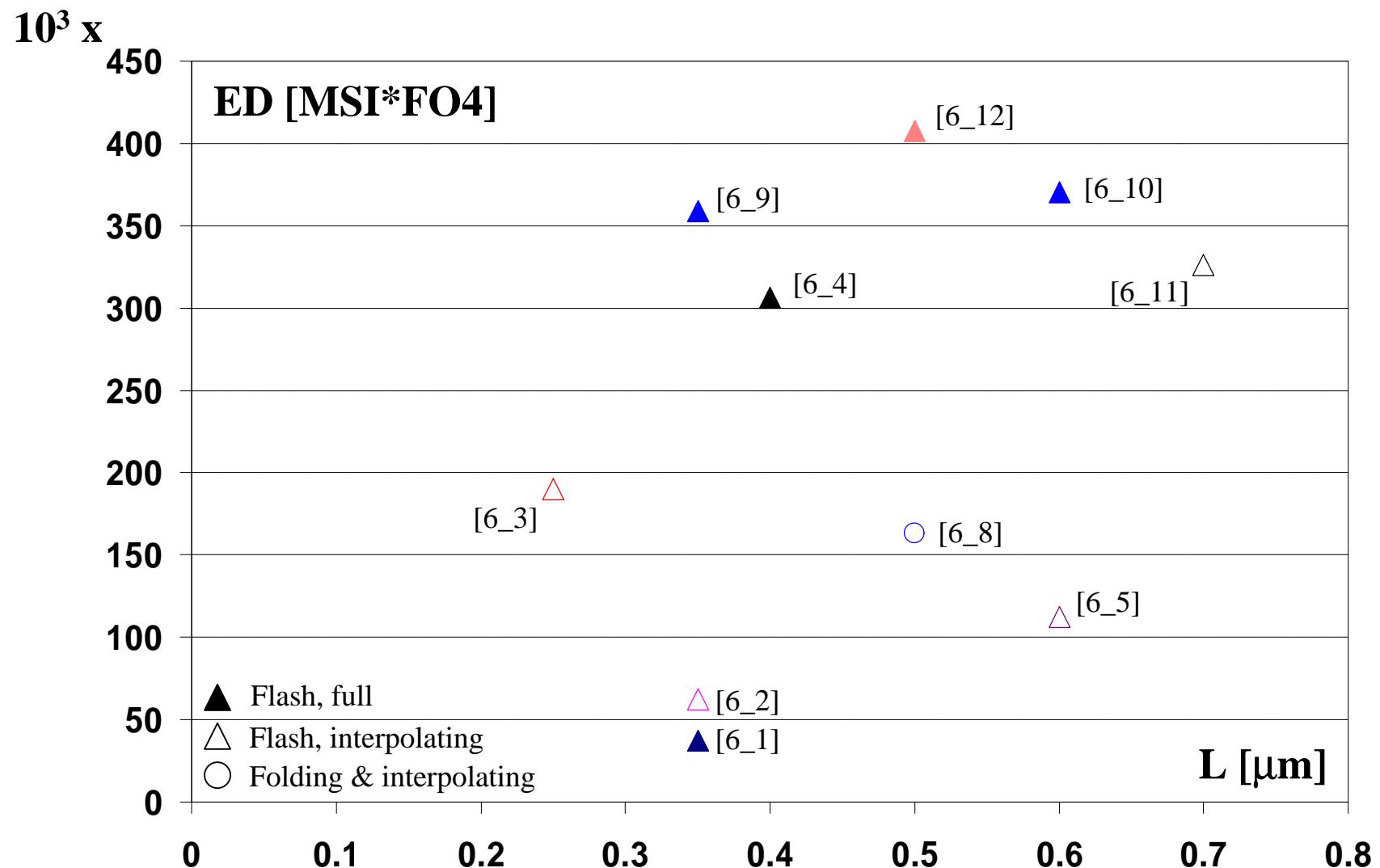


# Energy\*''Delay'' vs. technology - 8bit

---

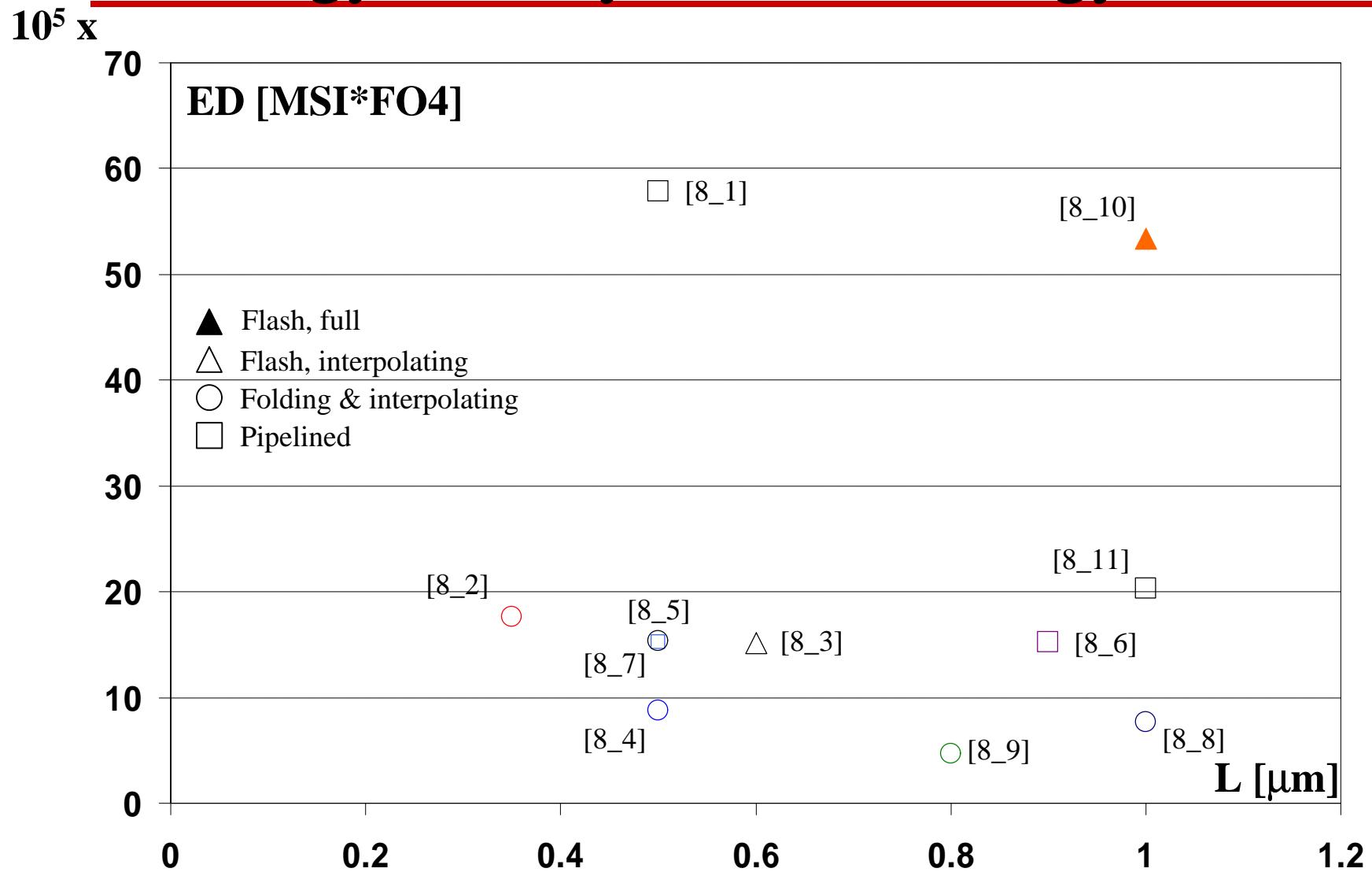


# Energy\*”Delay” vs. technology - 10bit

---

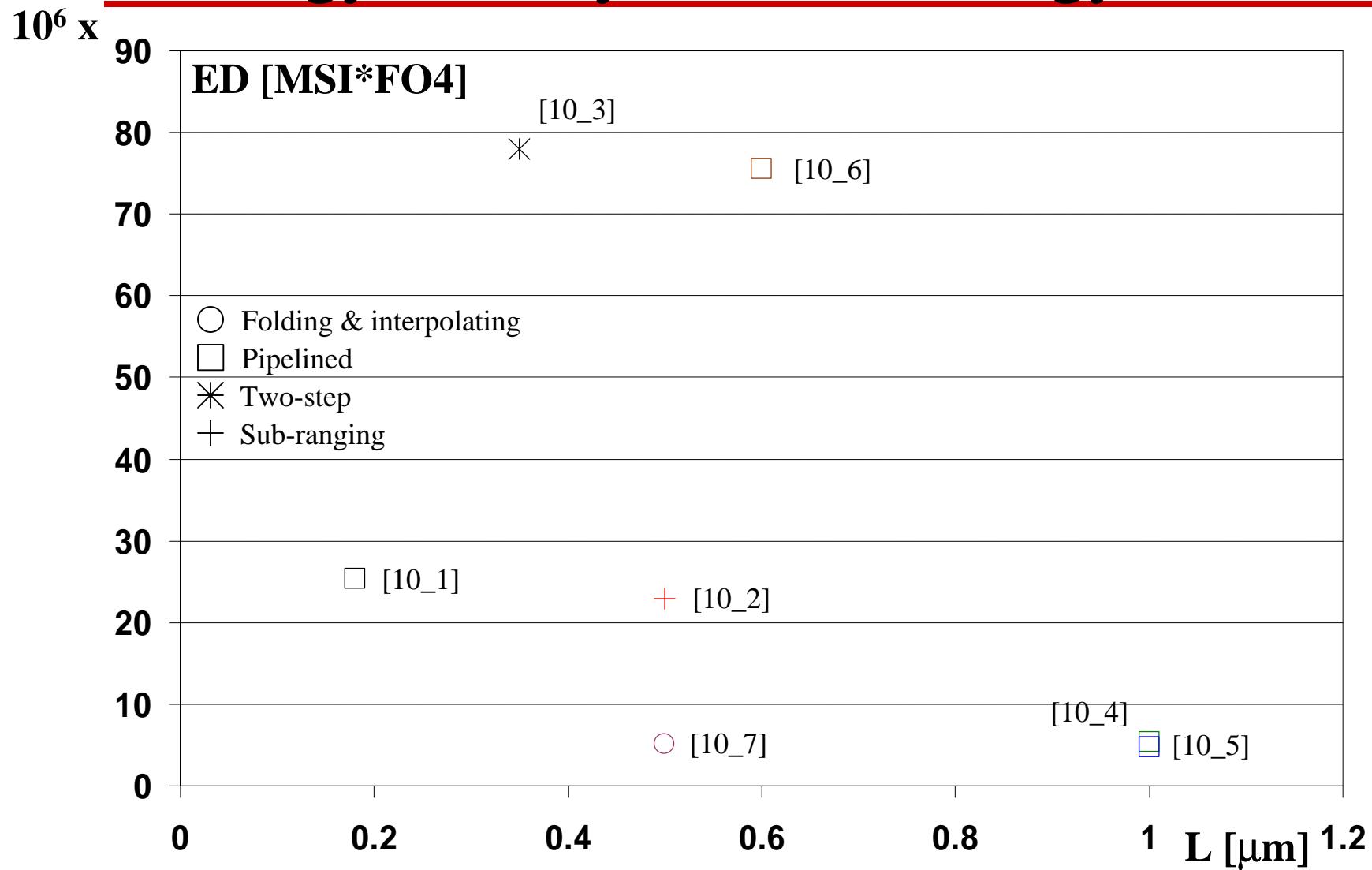

# Figure of merit vs. technology

---

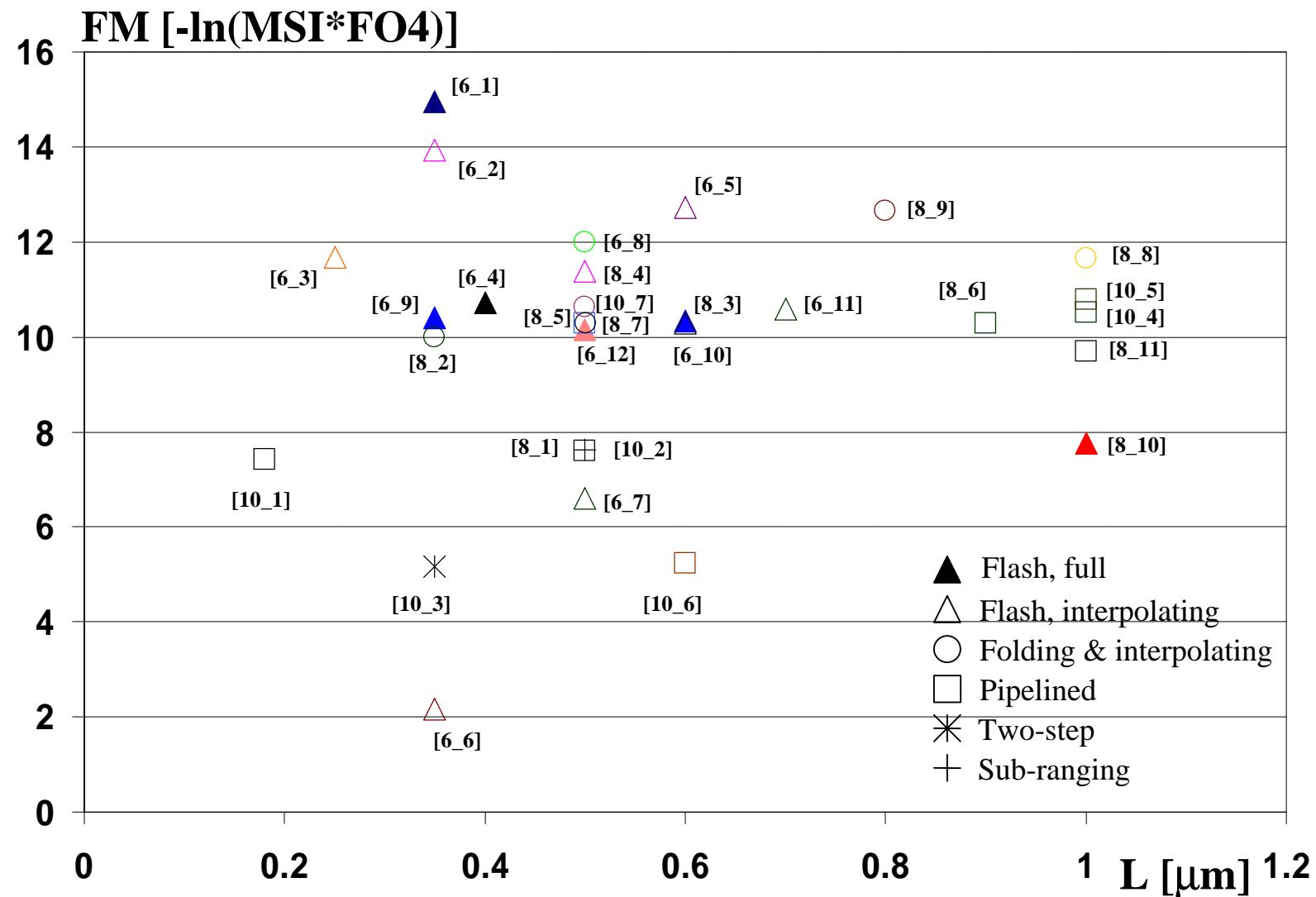

# Limiting factors

---

- Timing errors
  1. Sampling clock jitter
  2. Limited rise/fall time of sampling clock
  3. Skew of clock & input signal at different places on the chip  
(1ps = 100-200 μm on a die)
  4. Signal-dependent delay
- Distortion errors
  1. Sampling comparators' aperture time
  2. Distortion in the linear part of the input amplifier
  3. Changes in the reference voltage values & comparator offsets, also kickback
  4. Delays of analog signal and clock signal

# Timing Error performance limitations

---

- Definition A:

$$SNR = -20 \log_{10}(2pf_{in} e_{t\_rms})$$

$$e_{t\_rms} < \frac{10^{-(6.02 ENOB + 1.76) / 20}}{2pf_{in}}$$

- Definition B:

$$2pf_{in} A \Delta t < 1LSB = \frac{2A}{2^N}$$

$$e_{t\_rms} < \frac{1}{3p 2^N f_{in}}$$

For max fin=1GHz

N	A: $\epsilon_{trms}$ [ps]	B: $\epsilon_{trms}$ [ps]	C: $\epsilon_{trms}$ [ps]
2	33	27	53
4	8	7	27
6	2	2	14
8	0.5	0.4	7
10	0.1	0.1	3

- Definition C:

$$e_{t\_rms} < \frac{1}{3p 2^{LENOB/2} f_{in}}$$

Taking into account both transmitter and receiver noise  
and budgeting 50% for other noise

# Conclusion

---

- Future – very high speed ADCs
  - Digitally corrected interpolated Flash
  - Time-Interleaved pipelined ADC with channel mismatch calibration
- Big problem – timing errors
  - Most of all jitter – after all it is Gaussian noise limit
  - Jitter is less of a problem for digital data communications
- Spectrum allocation limitations for wireless
  - Most of ADCs need not be very, very high speed

# References

---

## 6 bit Converters

- [6\_1] M. Choi and A. Abidi “ A 6b 1.3GSample/s A/D Converter in 0.35 $\mu$ m CMOS,” ISSCC 2001, paper 8.1
- [6\_2] G. Geelen “ A 6b 1.1GSample/s CMOS A/D Converter,” ISSCC 2001, paper 8.2
- [6\_3] K. Nagaraj et al. “ Dual Mode A/D Converter,” JSSC 2000, December, vol. 35, no. 12, pp. 1760-68
- [6\_4] Y. Tamba and K. Yamakido “ A CMOS 6b 500MSample/s ADC for a Hard Disk Drive Read Channel,” ISSCC 1999, paper 18.5
- [6\_5] K. Yoon et al. “ A 6b 500MSample/s CMOS Flash ADC with a Background Interpolated Auto-Zeroing Technique,” ISSCC 1999, paper 18.6
- [6\_6] B. Song et al. “ A 1V 50MHz Current-Interpolating CMOS ADC,” VLSI Symposium 1999, paper 8.3
- [6\_7] K. Nagaraj et al. “ Efficient 6-b A/D Converter Using a 1-bit Folding Front End,” JSSC 1999, August, vol. 34, no. 8, pp. 1056-62
- [6\_8] M. P. Flynn and B. Sheahan “ A 400MSample/s 6b CMOS Folding and Interpolating ADC,” ISSCC 1998, paper 9.7
- [6\_9] S. Tsukamoto et al. “ A CMOS 6b 400MSample/s ADC with Error Correction,” ISSCC 1998, paper 9.8
- [6\_10] J. Spalding and D. Dalton “ A 200MSample/s 6b Flash ADC in 0.6um CMOS,” ISSCC 1996, paper 19.5
- [6\_11] R. Roovers and M. S. J. Steyaert “ A 175Ms/s, 6 b, 160 mW, 3.3 V CMOS A/D Converter,” JSSC 1996, July, vol. 31, no. 7, pp. 938-44
- [6\_12] S. Tsukamoto et al. “ A CMOS 6-bit, 200Msample/s, 3 V-Supply A/D Converter for a PRML Read Channel LSI,” JSSC 1996, November, vol.31, no. 11, pp. 1831-36

## 8 bit Converters

- [8\_1] J. Ming and S. H. Lewis “ An 8b 80MSample/s Pipelined ADC with Background Calibration,” ISSCC 2000, paper 2.5
  - [8\_2] K. Yoon et al. “ An 8-bit 125Ms/s CMOS Folding ADC for Gigabit Ethernet LSI,” VLSI Symposium 2000, paper 16.2
  - [8\_3] Y. Wang and B. Razavi “ An 8-bit 150-MHz CMOS A/D Converter,” JSSC 2000, March, vol. 35, no. 3, pp. 308-17
  - [8\_4] M. Choe et al. “ An 8b 100MSample/s CMOS Pipelined Folding ADC,” VLSI Symposium 1999, paper 8.4
-

# References ...

---

- [8\_5] W. Bright “ 8b 75MSample/s 70mW Parallel Pipelined ADC Incorporating Double Sampling,” ISSCC 1998, paper 9.5
- [8\_6] K. Nagaraj et al. “ A 250-mW, 8-b, 52-Msample/s, Parallel-Pipelined A/D Converter with Reduced Number of Amplifiers,” JSSC 1997, March, vol. 32, no. 3, pp. 312-20
- [8\_7] A. G. W. Venes and R. J. van de Plassche “An 80MHz 80mW 8b CMOS Folding A/D Converter with Distributed T/H Preprocessing,” ISSCC 1996, paper 19.4
- [8\_8] M. P. Flynn and D. J. Allstot “ CMOS Folding ADCs with Current-Mode Interpolation,” ISSCC 1995, paper 16.2
- [8\_9] B. Nauta and A. G. W. Venes “A 70MSample/s 110mW 8b CMOS Folding Interpolating A/D Converter,” ISSCC 1995, paper 16.3
- [8\_10] M. Pelgrom et al. “ A 25-Ms/s 8-bit CMOS A/D Converter for Embedded Application,” JSSC 1994, August, vol. 29, no. 8, pp. 879-86
- [8\_11] C. Conroy et al. “ An 8-bit 85MS/s Parallel-Pipeline A/D Converter in 1-um CMOS,” JSSC 1993, April, vol. 28, no. 4, pp. 447-54

## 10 bit Converters

- [10\_1] Y. Park et al. “ A 10b 100MSample/s CMOS Piplined ADC with 1.8V Power Supply,” ISSCC 2001, paper 8.3
- [10\_2] B. Brandt and J. Lutsky “ A 75mW 10b 20MSample/s CMOS Subranging ADC with 59dB SNDR,” ISSCC 1999, paper 18.4
- [10\_3] H. van der Ploeg and R. Remmers “ A 3.3V 10b 25MSample/s Two-Step ADC in 0.35um CMOS,” ISSCC 1999, paper 18.2
- [10\_4] K. Dyer et al. “ Analog Background Calibration of a 10b 40MSample/s Parallel Pipelined ADC,” ISSCC 1998, paper 9.3
- [10\_5] D. Fu et al. “ Digital Background Calibration of a 10b 40MSample/s Parallel Pipelined ADC,” ISSCC 1998, paper 9.2
- [10\_6] A. M. Abo and P. R. Gray “A 1.5V, 10-bit, 14MS/s CMOS Pipeline Analog-to-Digital Converter,” VLSI Symposium 1998, paper 14.2
- [10\_7] K. Bult et al. “ A 170mW 10b 50MSample/s CMOS ADC in 1mm<sup>2</sup>,” ISSCC 1997, paper 8.3