

USING THE L6204, A BIPOLAR STEPPER AND DC MOTOR DRIVER IN BCD TECHNOLOGY


by E Balboni

Containing two H-bridge drivers, the L6204 is a compact and simple solution for driving two-phase bipolar stepper motors and in applications where two DC motors must be driven.

The L6204 is a DMOS dual full bridge driver mainly designed to drive bipolar stepper motors. All the inputs are TTL/CMOS compatible and each bridge can be enabled by its own dedicated input. The windings current can be regulated by sensing the voltage drop across two low value resistors at the low end of both the bridge: this is the feedback for the current controller. To feed

the gates of the upper DMOS, a peak to peak rectifier charges a capacitor in series with the Power Supply voltage at the optimum DC level defined by an on-board square wave oscillator. The L6204, with 0.5 A drive capability without external heatsink up to 70°C, is packaged in a 20 leads PowerDip with four heat transfer pins. The Block diagram of the device is shown in fig.1.

Figure 1: Block diagram of the L6204 single chip dual full bridge driver.

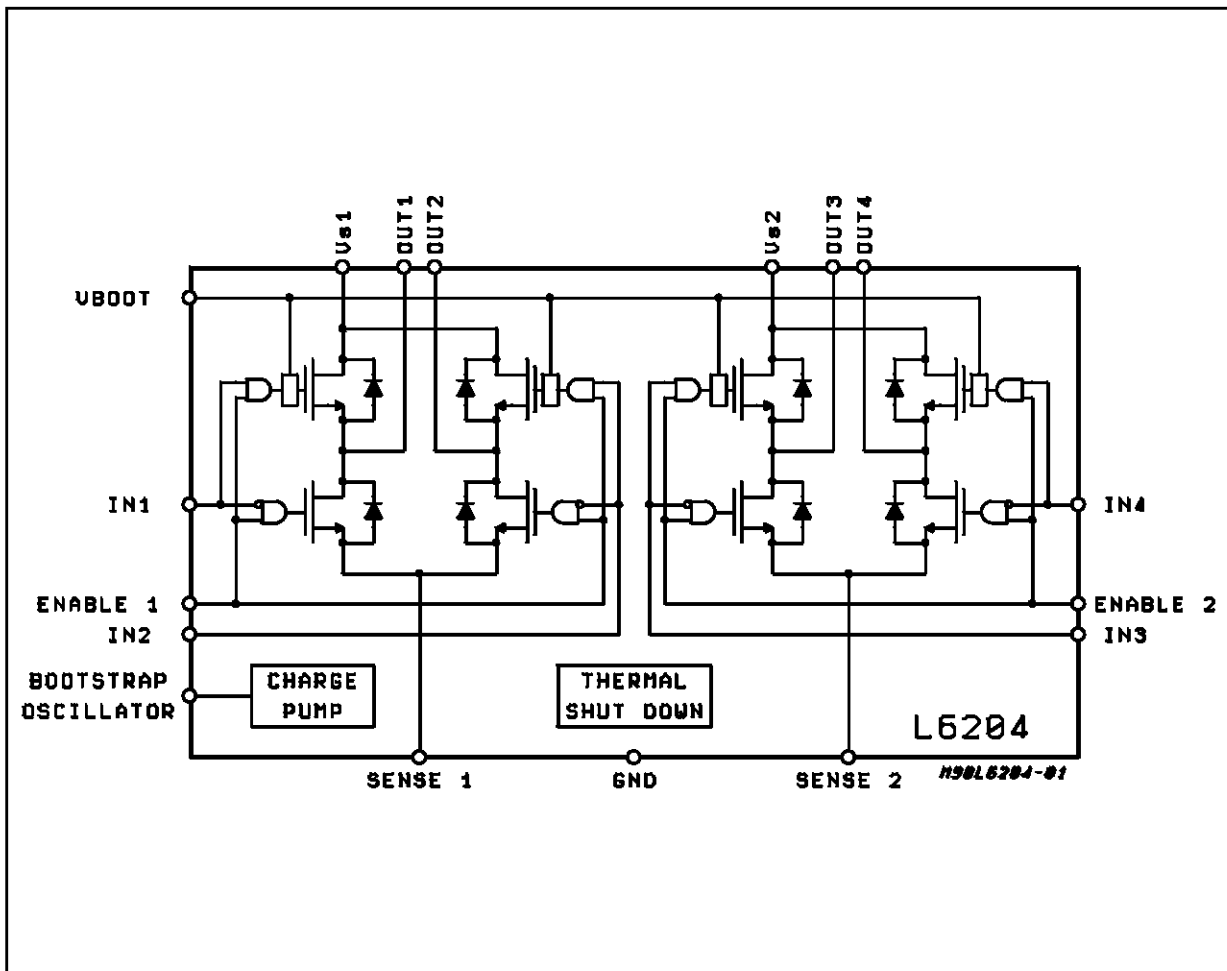

stead of two. This configuration is shown in fig.2 to drive the load Z1. A more complex circuit, in wich one paralleled L6204 drives a DC motor, is shown in fig.3B; in this example the two chopper of the L6506 are used to implement two functions: 1) Current Control during speed variation at $I_p \text{ max} = 0.8\text{A}$ and 2) Current Control during brake and/or direction change at higher current level that depends from the brake repetition (it

must be in the Max Ratings limit). The divider R6R7 defines the brake current intensity as V_{17}/R_s while the product $(I_p \text{ max.}) \times (R_s)$ is the limit of the reference voltage V_{16} for speed control. The Enable function is driven via the L6506. Since during the brake time the Enable of the L6506 is chopped, the motor current ricirculates via the Supply; because of this a suitable large capacitor must be connected in parallel to C2.

Figure 3A: Bidirectional DC motor drive. The L6204 can drive two motors.


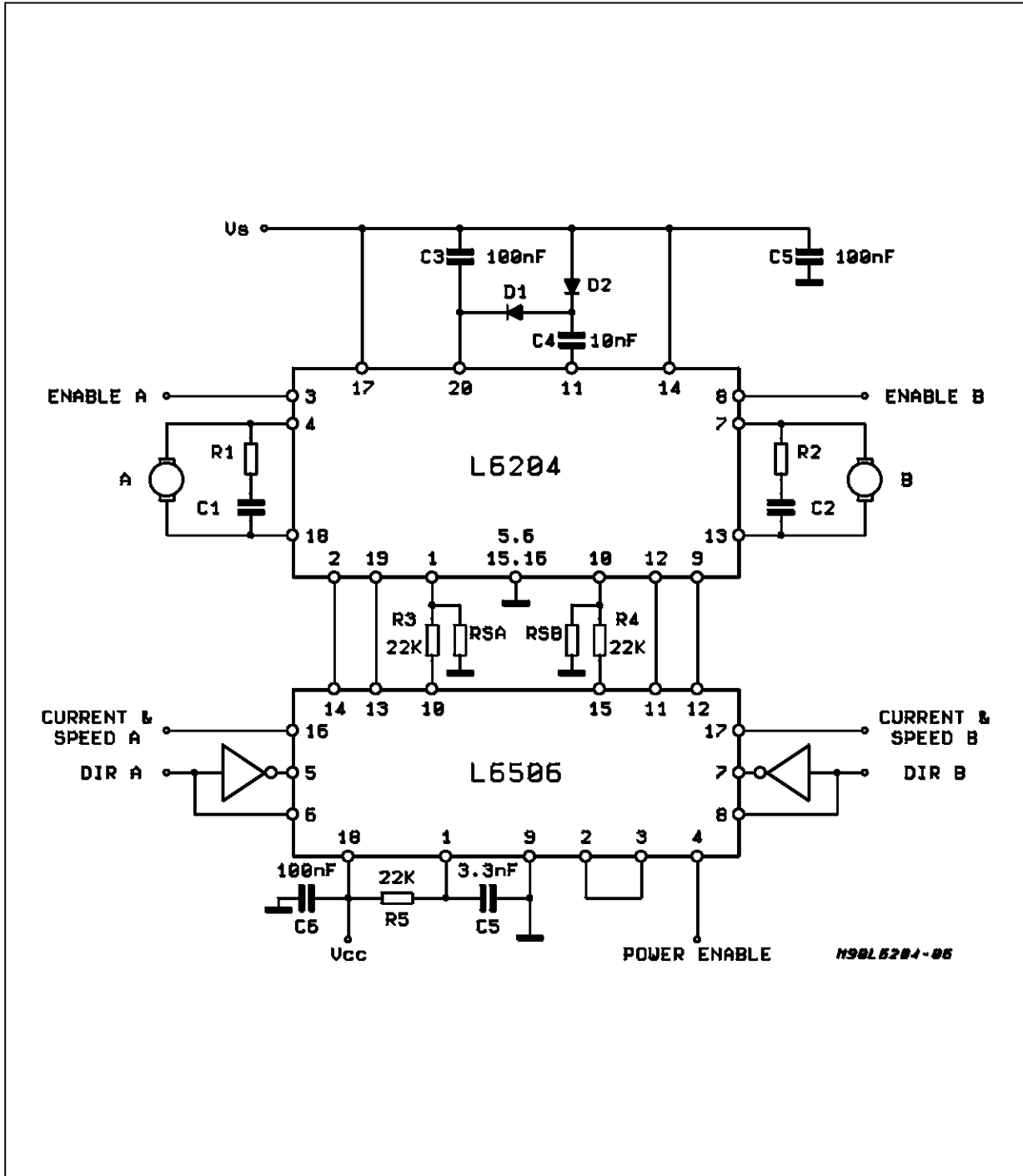


Figure 4: Bipolar stepping motor drive: phase sequence generation and current peak control are achieved by means of the controller L297.

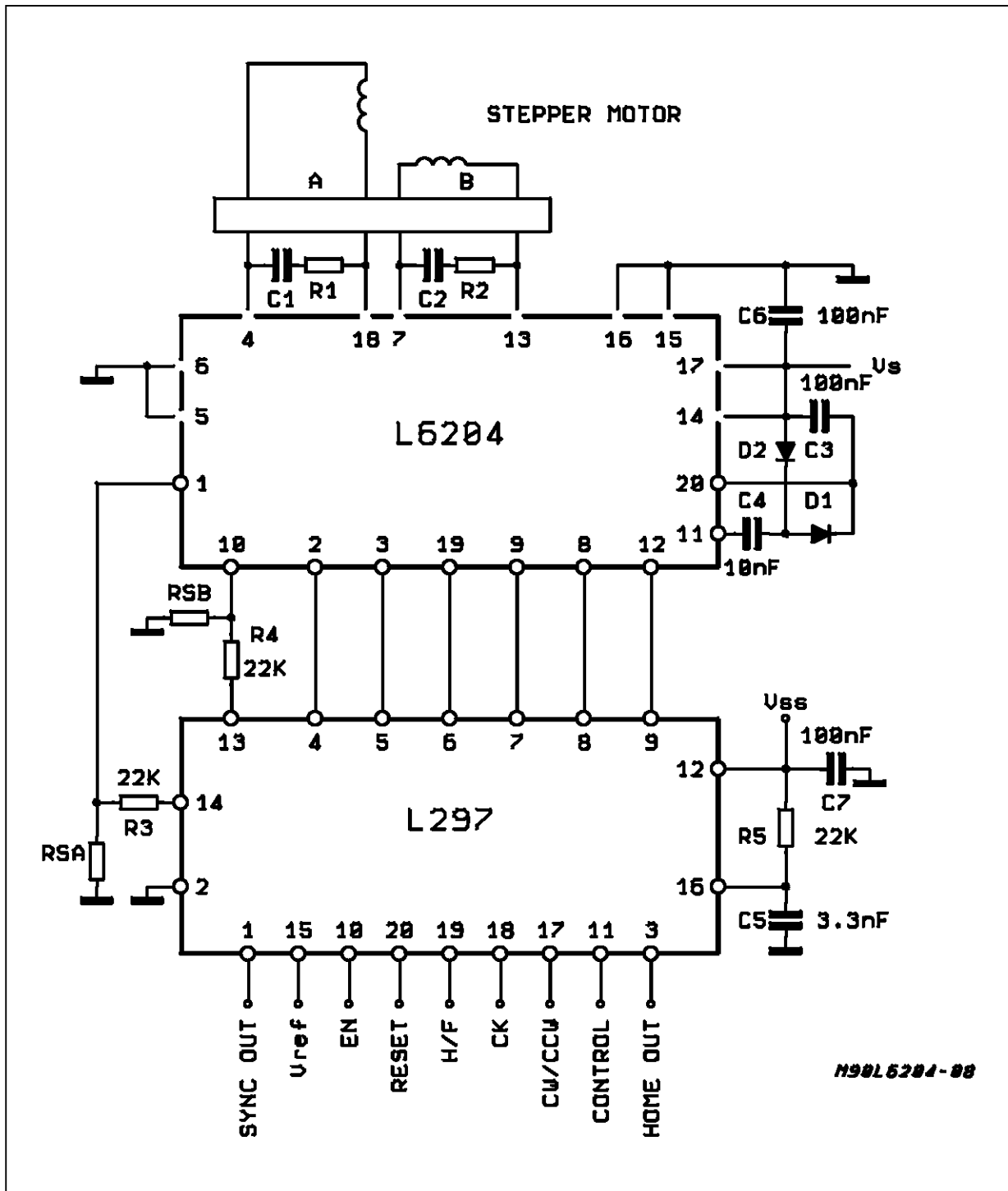


This last is obtained from the oscillator the frequency of which is fixed by the ratio $1/0.69 R5C5$ about ($R5 \geq 10Kohm$). The peak of the chopped current is given by the ratio of the reference voltage at pin.15 and the value of the sensing resis-

tors Rs. When the four phase signals needed at the inputs of the L6204 are generated in any other way than by the L297 (for example, via μ Processor), the motor driver needs one interface to control the peak current. One possible solution is shown in fig.5.

APPLICATION NOTE


Figure 5: The L6506 can be used to control the peak current in the windings of a bipolar stepper motor. The power is supplied by the L6204.

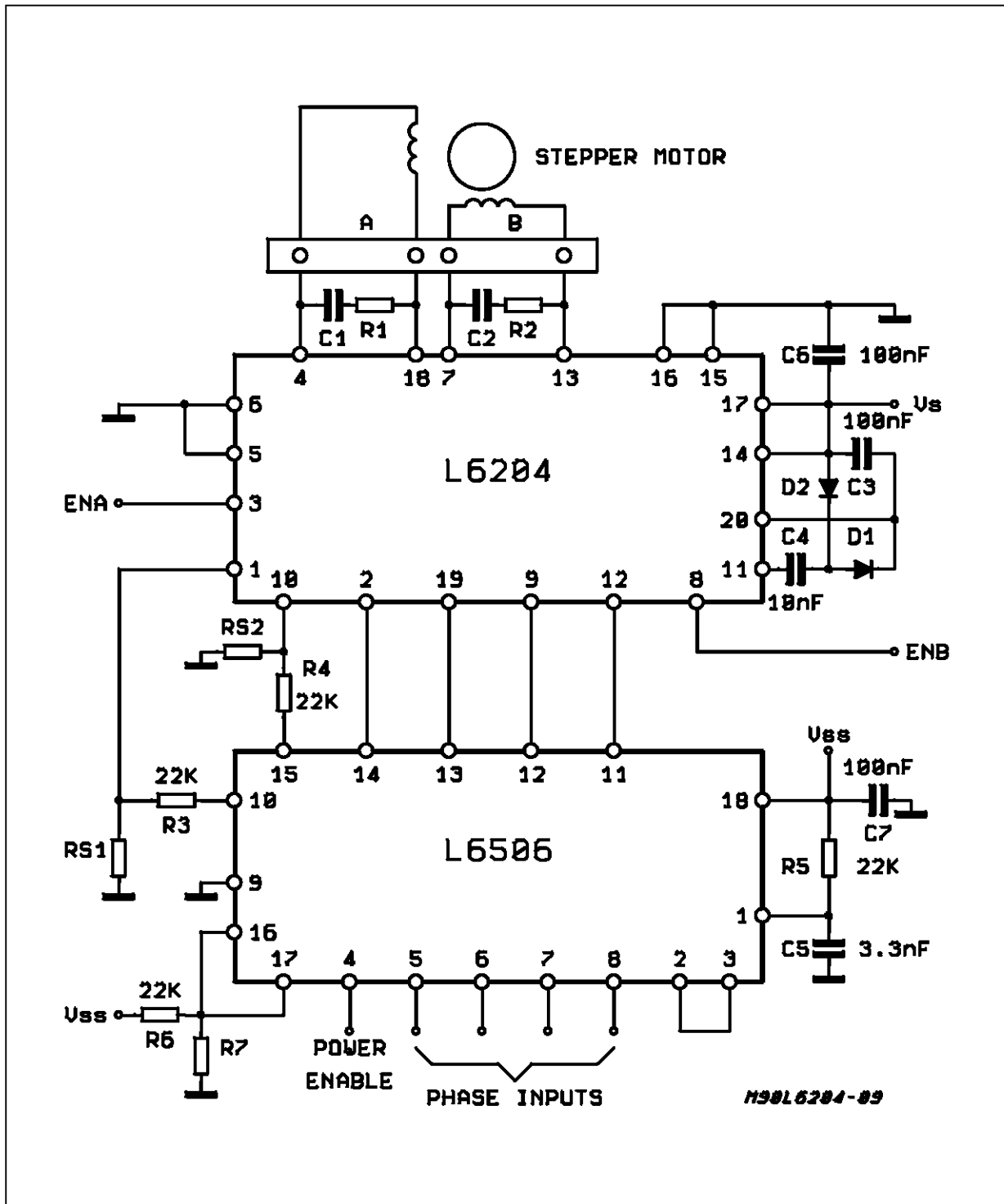

The motor can be driven in the Full-Step or in Half-Step Mode. The chopped current I_p is controlled at the value V_{ref}/R_s where V_{ref} is the output voltage of the divider R6 R7. The pins 16 and 17 (reference input voltage of the controller)

can be driven with two different signals. This arrangement allows to keep constant the motor current and the torque during the Half-Step Mode revolution of the stepper. This behavior is well explained by the fig. 6.

Figure 6: Characteristics of the Half - Step Mode drive with constant torque control. It should be noted that the resultant current is constant while the current in the windings alternates between one-phase-on and two-phase-on with a ratio of $\sqrt{2}$.

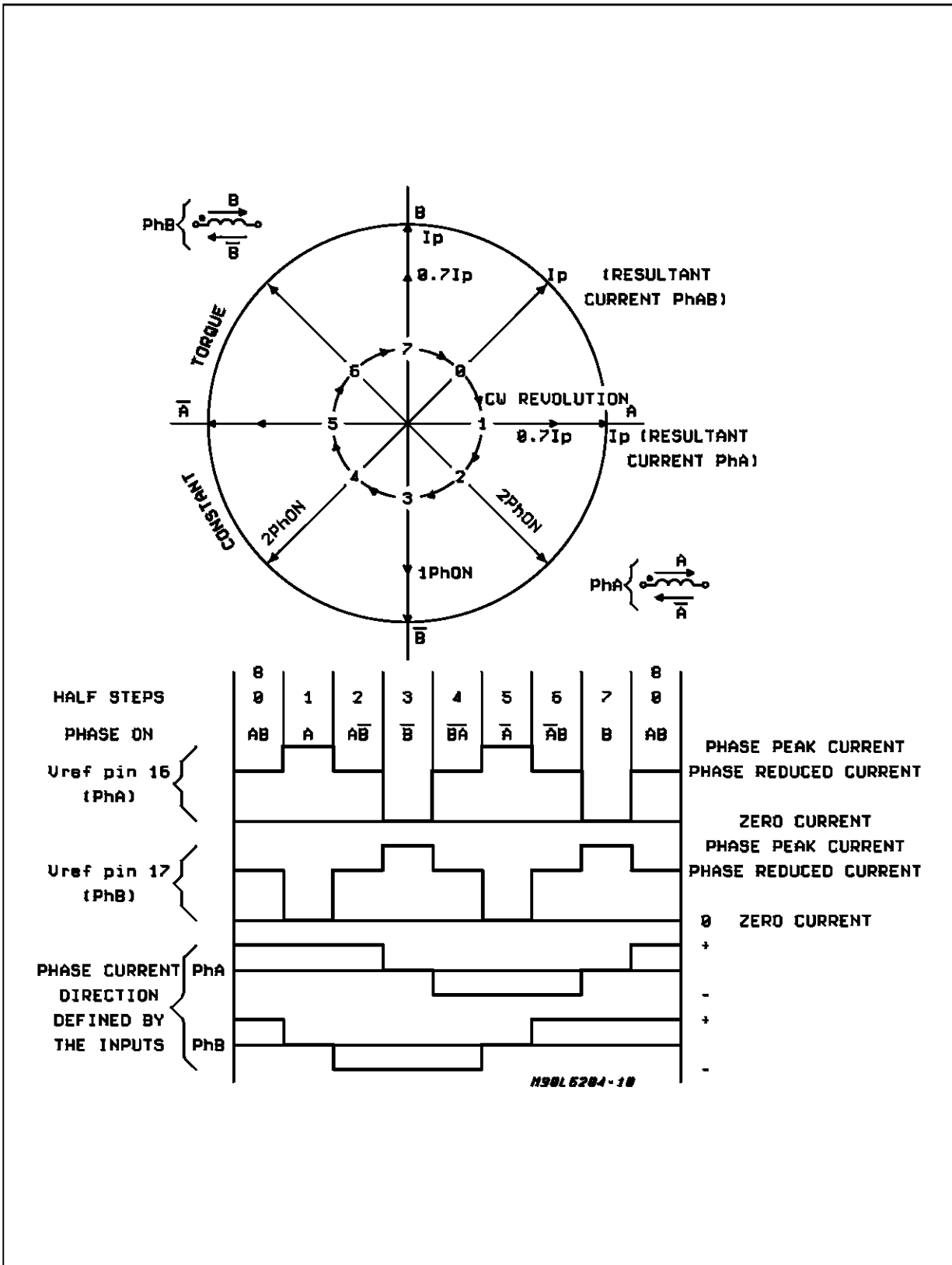

APPLICATION NOTE

Information furnished is believed to be accurate and reliable. However, SGS-THOMSON Microelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of SGS-THOMSON Microelectronics. Specifications mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. SGS-THOMSON Microelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of SGS-THOMSON Microelectronics.

© 1995 SGS-THOMSON Microelectronics - All Rights Reserved

SGS-THOMSON Microelectronics GROUP OF COMPANIES

Australia - Brazil - France - Germany - Hong Kong - Italy - Japan - Korea - Malaysia - Malta - Morocco - The Netherlands - Singapore - Spain - Sweden - Switzerland - Taiwan - Thailand - United Kingdom - U.S.A.