



# PHILIPS

Philips Semiconductors

---

Connectivity

Oct 2001

## Application Note

### Interfacing ISP1161 to Intel StrongARM® SA1110 Processor

Rev. 3.0

**Revision History:**

Rev.	Date	Descriptions	Author
1.0	Aug 18, 2000	First draft	Socol Constantin
2.0	May 29, 2001	Updates after actual implementation	Ng Chee Yu
3.0a	June 7, 2001	Revised chapters and added Appendix A	Jason Ong
3.0b	Aug 2001	Changed to Philips template	Yuk-lin Ong
3.0c	Oct 8, 2001	Updated schematic	Jason Ong

We welcome your feedback. Send it to [apic@philips.com](mailto:apic@philips.com).

---

---

## Interfacing ISP1161 to Intel StrongARM SA1110

---

---

### Table of Contents

1. Overview.....	3
2. ISP1161 Interface Signals to a RISC Processor Bus.....	3
3. Intel StrongARM SA-1110 processor.....	4
4. Considerations in Timing Diagrams and WAIT States.....	4
5. Using interrupts.....	6
6. Suspend/Resume.....	6
7. Schematic Diagram.....	7
Appendix A –Hardware Installation.....	9
Appendix B –Software Installation.....	11

---

---

## Interfacing ISP1161 to Intel StrongARM SA1110

---

---

### 1. Overview

The unique design of Philips ISP1161 makes it possible to use it as a host controller (with two downstream ports) as well as a device controller (with one upstream port); these ports may be accessed independently. In this way, a simultaneous connection as a host controller and a device controller can be achieved.

When ISP1161 is integrated into a personal digital assistant (PDA) or handheld personal computer (HPC), in most configurations this means connecting it to the external bus interface of a RISC processor. This application note deals with the critical issues in ISP1161's embedded design, using the Intel StrongARM SA-1110 processor as a concrete example.

The actual implementation of the SA1110-ISP1161 uses an Intel StrongArm-1110 Hardware Development Platform, a Philips ISP1161 evaluation kit, and a Philips ISP1161 Bridging Board for SA1110.

### 2. ISP1161 Interface Signals to a RISC Processor Bus

The processor bus interface of ISP1161 was designed for a simple direct connection with a RISC processor. The data transfer can be done in PIO or DMA mode. The estimated maximum data transfer rate on the generic processor bus of the ISP1161—based on an ISP1161 internal clock frequency value equal to 48 MHz—is about 14 MB/s. To achieve the maximum data transfer rate on the host processor bus, the ISP1161 contains a Ping-Pong structured RAM which allows alternative access from the RISC processor or from the internal host/device controller. The “Ping-Pong” memory is allocated separately for the host and the device controllers. The host controller uses 2-KB of “Ping” memory and 2-KB of “Pong” in its allocated memory and the device controller uses 1.5 KB for each of the “Ping” memory and “Pong” in its own memory.

The main ISP1161 signals you should take into consideration for connecting to a StrongARM SA1110 processor will be:

- A 16-bit data bus: D0-D15 for ISP1161. ISP1161 is “little endian” compatible.
- Two address lines A0 and A1 necessary for complete addressing of the ISP1161 internal registers:
  - A0 = 0 and A1 = 0 selects the Data Port of the Host Controller
  - A0 = 1 and A1 = 0 selects the Command Port of the Host Controller
  - A0 = 0 and A1 = 1 selects the Data Port of the Device Controller
  - A0 = 1 and A1 = 1 selects the Command Port of the Device Controller
- One CS\_N line used for selection of the ISP1161 in a certain address range of the host system. This input signal is active LOW.
- RD\_N and WR\_N are common read and write signals. These signals are active LOW.
- Two interrupt lines: INT1 (used by the host controller) and INT2 (used by the device controller). Both have programmable level/edge and polarity (active HIGH or LOW).
- The RESET signal is active LOW.

---



---

## Interfacing ISP1161 to Intel StrongARM SA1110

---



---

### 3. Intel StrongARM SA-1110 processor

The main features of the Intel StrongARM SA1110 processor of special interest for connecting to the ISP1161 are highlighted as follows:

The “Memory and PCMCIA Control Module” of the Intel StrongARM processor is responsible for generating all signals for interfacing with the ISP1161. The following features are useful for a direct connection of ISP1161:

- The “Memory Control Module” generates all the necessary signals to control different types of external devices:
  - DRAM (up to 4 banks of FPM, EDO, and SDRAM)
  - static memory (up to 3 banks of ROM, Flash, SRAM, SMAROM – selected by nCS0, nCS1 and nCS2 signals)
  - static memory and variable latency I/O devices (up to 3 banks of ROM, Flash, SMROM, and SRAM-like variable latency I/O devices, selected by nCS3, nCS4 and nCS5 signals).

Additional wait-states can be inserted by programming the internal registers of SA1110, if necessary.

- The data bus size of these memory areas can be set as 16-bit or 32-bit wide. The 16-bit wide data bus size is used by the ISP1161.
- The memory access is defined as “little endian” or “big endian” types, according to the value of the “big endian bit” in the control register. By default, at power-on or after a reset the SA1110 processor uses the “little endian” memory access scheme, which corresponds to ISP1161 requirement.

### 4. Considerations in Timing Diagrams and WAIT States

The following is a short study of the timing diagrams of the main bus cycles of ISP1161 and Intel SA1110:

The timing diagram of the external bus cycle of the Intel StrongARM SA1110 processor is determined by the “memory clock”, which is equal to two CPU clock cycles. Timing during RD/WR accesses is determined by the settings of the MSC0, MSC1 and MSC2 registers which correspond to the chip select pairs nCS(5,4), nCS(3,2) and nCS(1,0) respectively. All timing fields are specified as numbers of memory clock cycles. Each register contains two identical configuration fields – corresponding to each nCS within one of the pairs mentioned earlier. By programming the MSC0, MSC1 and MSC2 registers it is possible to modify the assert time of each beat of a burst RD/WR, the de-assert time between each beat of a burst RD/WR, and the hold-off time after a write to subsequent accesses.

According to ISP1161 datasheet specifications, a read operation requires the following timing parameters (the write operation is similar), defined in Figure 1:

- tRL = 33 nsec (RD\_N low pulse width – minimal value required by ISP1161),
- tRHRL = 110 nsec (RD\_N HIGH to next RD\_N LOW – minimal value required by ISP1161) and
- tRHDZ = 3 nsec (RD\_N hold time, minimal value that can be expected from ISP1161).
- tRC = 143 nsec (will obviously result as a sum of tRL and tRHRL)
- tSHSL = 300 nsec (first RD\_N/WR\_N after CMD).

Consider the access of one of the internal registers of the ISP1161 (for example the Control Register of the HC) for a detailed analysis of the timing diagram. An access of one of the internal registers of ISP1161 will require two phases: first writing the address (index) of the selected register into the Command Port and then the data transfer access (RD/WR) may take place. Note: the index of each register is different in case of a RD or a WR operation.

The following timing diagram describes the two phases of accessing the ISP1161:

## Interfacing ISP1161 to Intel StrongARM SA1110

- The first phase is accessing the Command (control) Port of ISP1161, to write the address (index) of the data port that will be accessed. In this phase CS\_N is active, the data lines D0-D15 contain the desired address and then the WR\_N pulse will be activated and will latch the data. Note the value of tSHSL that represents the minimum time required between occurrence of the first phase and the occurrence of the second phase. One example of the HC "Control Register" a value of 01H will be transferred during a RD operation and 81H during a WR operation.
- The second phase shown in the same diagram consists of the access (read or write) to the data port selected by the address latched in the previous phase. Two timing diagrams are combined again in this second phase: one for Read access and one for Write access. A series of RD\_N and WR\_N pulses are shown in the diagram to define the timing requirements between two consecutive accesses to the ISP1161: tRHRL, tWHWL, tRC, tWC, tRLDV, as specified in the datasheet.

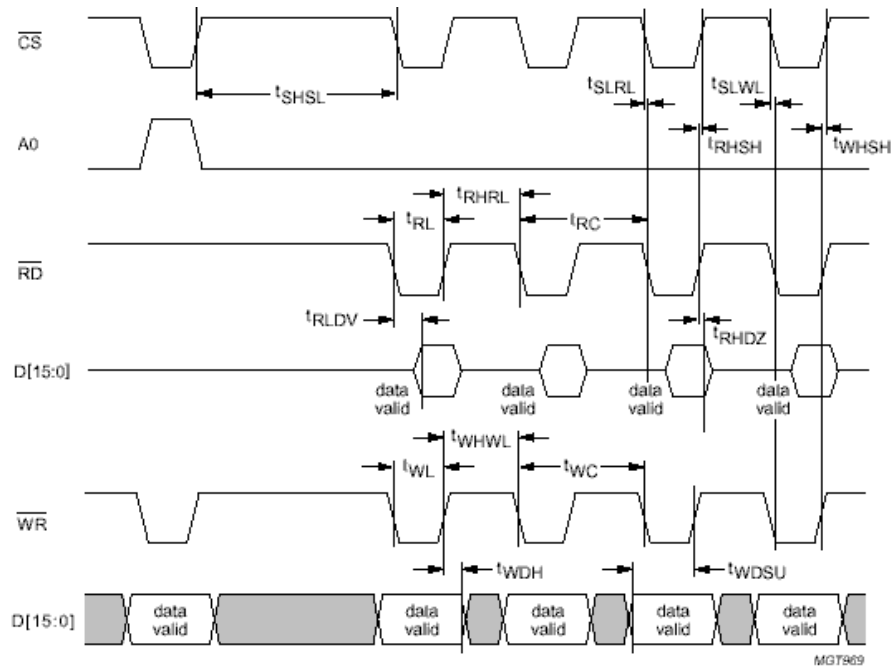


Figure 1. Parallel I/O Interface Timing (16-bit Read/Write)

---

---

## Interfacing ISP1161 to Intel StrongARM SA1110

---

---

### 5. Using interrupts

ISP1161 will generate two interrupts on INT1 and INT2 pins, allocated for the Host and the Device controller, respectively. These interrupts will occur depending on the setting of the following registers: *Interrupt Register*, *Interrupt Enable Register* and the *Hardware Configuration Register*. These registers are separately programmed for host controller and for device controller operation.

Connect the ISP1161 interrupts INT1 and INT2 to one of the 28 GPIO lines of the SA1110 processor. Each GPIO line of the SA1110 can be programmed to detect a rising or falling edge and to generate an interrupt. The type of edge detection is programmed through the GPIO rising-edge detect register GREER and GPIO falling-edge detect register GFER. The state of the edge detect can be determined by reading the edge-detect status register GEDR.

Both INT1 and INT2 of the ISP1161 are programmable as active on level or edge and HIGH or LOW—as specified in the *Hardware Configuration Registers* for each of the Host and Device controllers, separately. You must match the settings of the ISP1161 interrupt lines INT1 and INT2 with the settings of the GREER and GFER registers of SA1110, used for programming the type of edge detection.

You can use ISP1161's INT1 and INT2 output signals to “wake up” the host system's processor—in this case the SA1110—from the idle or sleep modes. The GPIO pins are defined as category 3 signals and are actively sampled by the SA1110 even during sleep mode. The sleep mode of SA1110 offers the greatest power savings. In this mode the internal sleep state machine of the SA1110 is running off the 32.768 kHz crystal oscillator and watches for a preprogrammed event to occur, which will initiate the wake-up sequence. The VDDX I/O voltage supply of SA1110 must be present during sleep mode to enable this wake-up method.

### 6. Suspend/Resume

You can make ISP1161 enter different functional states (Reset, Resume, Operational and Suspend) by programming the *Control Register* of the Host Controller or the *Mode Register* of the Device Controller.

Another way to “wake-up” ISP1161 from Suspend mode is to use the input signals H\_WAKEUP (for the Host Controller) and D\_WAKEUP (for the Device controller). These signals may be connected to any available GP I/O lines of the SA1110.

Monitoring the H\_SUSPEND pin (for Host status) and D\_SUSPEND pin (for Device status) can determine the actual status of the ISP1161, without having to access the internal status registers. Connecting these signals to any available GP I/O port of the SA1110 is an easy way to determine the status of the ISP1161.

ISP1161 may “wake up” when its CS\_N input signal becomes active, if this is desired, by programming a “1” in bit 3 of the *Hardware Configuration Register* of the Device Controller. Alternatively, if the same bit is programmed to a value of “0”, asserting the CS\_N signal does not cause ISP1161 to wake up.

---

---

## Interfacing ISP1161 to Intel StrongARM SA1110

---

---

### 7. Schematic Diagram

The following schematic diagram shows the connection of the ISP1161 to a StrongARM SA1110 processor, in a minimal hardware configuration.

In this example schematic, ISP1161 is simply selected by nCS5. To correctly access the ISP1161, it is assumed that the memory space selected by nCS5 is programmed for 16 bit accesses and “little endian”.

Interrupts INT1 and INT2 are arbitrarily connected to IRQ2 and IRQ3 lines of SA1110.

The RESET input signal of ISP1161 is generated in the schematics by the RSTOUT signal generated by the SA1110 processor, when its RESET\_IN signal is active. The RSTOUT signal is also asserted for “soft reset” events (sleep and watchdog). Connecting the RESET input of 1161 to RESET\_IN of SA1110 may be a better solution if INT1 and INT2 are used to “wake up” SA1110.


Pins H\_PSW1 and H\_PSW2 are connected to lines 4 and 5 of the same I/O port; this connection creates an alternative way to determine the power status of each downstream port.

Input signals H\_OC1\_N and H\_OC2\_N are used by the ISP1161 to detect an overcurrent on the downstream ports. As separate overcurrent detection and protection circuits are implemented for each downstream port in ISP1161, detection of an overcurrent on one of the downstream ports will power down that port only. Connecting the voltages of the two downstream ports VBUS\_DN1 and VBUS\_DN2 to H\_OC1\_N and H\_OC2\_N pins enables detection of the current value by sensing the voltage drop on Q1 and Q2 which are PMOS transistors with very low switch-on resistance  $R_{ds(on)}$ . Selection between Q1 and Q2 depends on the desired maximum current value and this determines the value of  $R_{ds(on)}$ . For example, if the allowed maximum current is about 0.5 A, a voltage drop of 75 mV will trigger the overcurrent circuitry and an approximate value of  $R_{ds(on)} = 150 \text{ m}\Omega$  will result. Connecting the 1161 input pins H\_OC1\_N and H\_OC2\_N to +5V will disable the internal overcurrent protection of ISP1161; an external overcurrent protection circuit may also be used.

Selection of the number of downstream ports can be done in this configuration by programming the respective GPIO output of the SA1110 to a certain value. This will determine the desired LOW or HIGH level on ISP1161's NDP\_SEL input signal, and one or two downstream ports will be selected accordingly.

Detection of a connection on the upstream port is achieved by connecting VBUS\_UP to pin D\_VBUS of the ISP1161. R12 and C20 will act as a low-pass filter that eliminates the possibility of sensing false voltage drop due to load current variations or noise on VBUS\_UP. It is recommended, if possible, to implement a hybrid power solution, by using VBUS\_UP to power the ISP1161 and an external power source for the rest of the system.

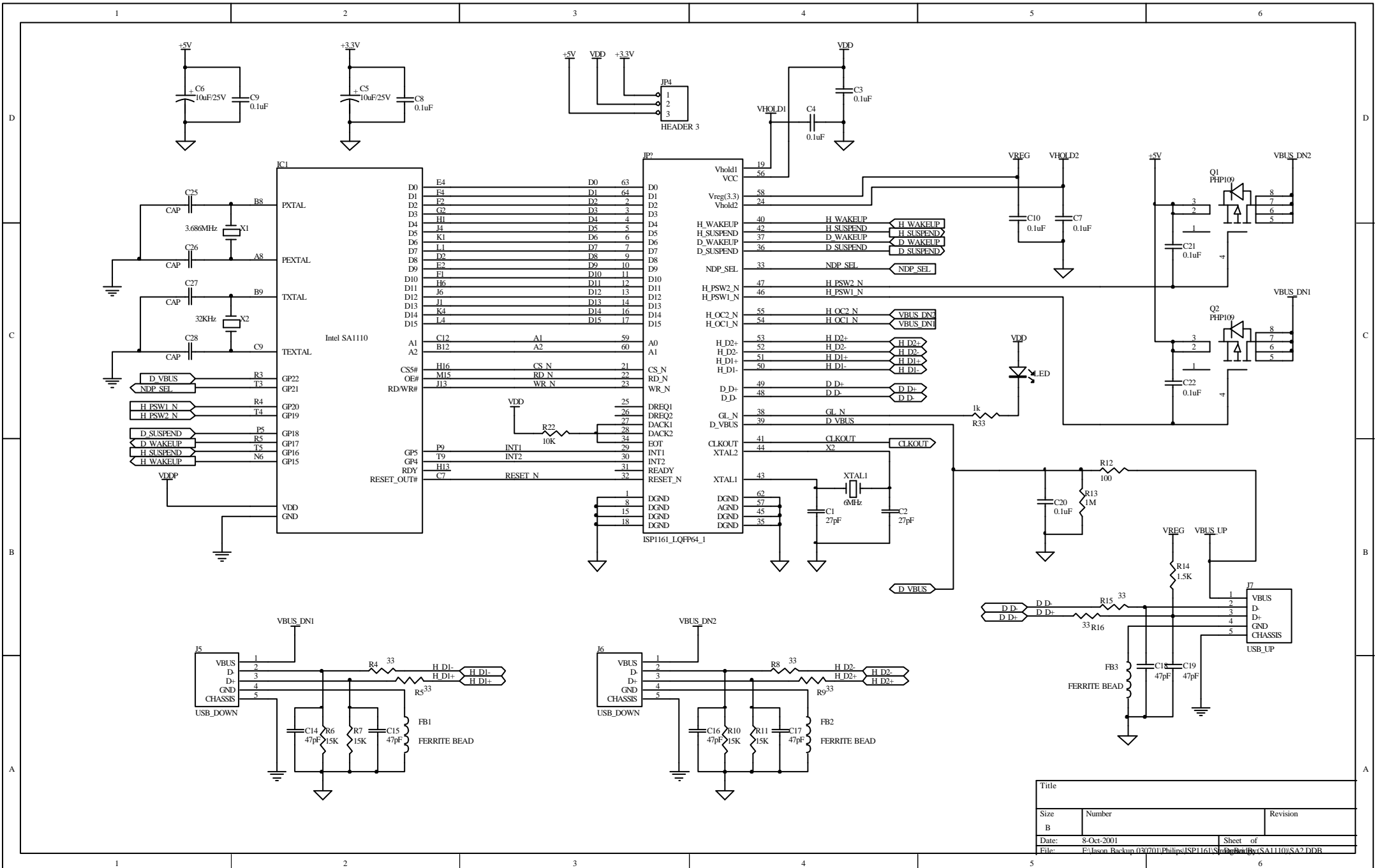The GL\_N output signal indicates, through an LED, the status of the USB device and helps in troubleshooting the USB connection.



Title		
Size	Number	Revision
B		
Date:	8-Oct-2001	Sheet of
File:	F:\Jason Backup 03\701\Philips\ISP116\US...By\SA1110\SA2_DDR	



---

## Interfacing ISP1161 to Intel StrongARM SA1110

---

### Appendix A –Hardware Installation

The installation of the ISP1161 to Intel StrongARM SA1110 is very simple. The procedure is as follows:

**Step 1:** Plug the ISP1161 Evaluation Board to the StrongBridge Board.

**Step 2:** Plug the StrongARM Development Kit to the StrongBridge Board.

**Step 3:** Plug the StrongARM Companion Chip Development Kit to the StrongARM Development Kit Board.  
The ISP1161 interface to Intel StrongARM SA1110 Evaluation Kit is ready for testing!

For a clearer graphical installation, please see the following figures:



Figure 3. ISP1161 Evaluation Board

Figure 4. ISP1161 Evaluation Board with StrongBridge Board



---

## Interfacing ISP1161 to Intel StrongARM SA1110

---



Figure 5. ISP1161 Evaluation, StrongBridge and StrongARM Development Kit



Figure 6. ISP1161 Evaluation, StrongBridge, StrongARM Development Kit and StrongARM Companion Chip Development Kit

 


Figure 7. Side View of ISP1161 interface to Intel StrongARM SA1110 Evaluation Kit

---

---

## Interfacing ISP1161 to Intel StrongARM SA1110

---

---

### Appendix B –Software Installation

#### Host Requirements

To develop on the WinCE platform:

1. Install Platform Builder in a PC running on Windows NT 4.0 or Windows 2000.  
The current version for Platform Builder is 3.0
2. After the destination location has been chosen, the CESH Update Screen appears.  
Determine if this is a new install or update of Microsoft Windows CE Platform Builder:
  - For new installs, choose: "Use Ethernet".
  - For updates, choose: "Do not change Current CESH settings".

#### Network Requirements

To use the Ethernet boot application to download the Windows CE image or to do Ethernet debugging, the host and target systems must choose **one** of the network configurations listed below:

- A network HUB with a DHCP server
- A 10BASE-T unshielded twisted pair (UTP) "cross-over" Ethernet cable to go between the host and SA-1110 Development Board (provided with the SA-1110 Development Board kit). The amount of network traffic often present on a corporate network HUB can impede the downloading efforts. To avoid network traffic, it is recommended that you use this 10BASE-T UTP "crossover" Ethernet cable.